
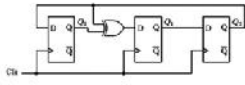


Frequency Response of RC Circuits

Peter Mathys
ECEN 1400

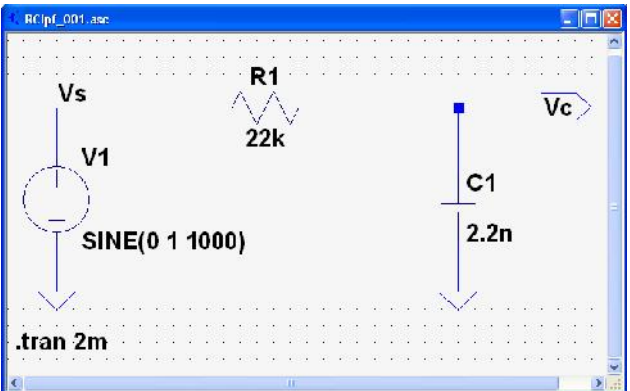



RC Circuit 1



Vs is source voltage (sine, 1000 Hz, amplitude 1 V).
Vc is voltage across capacitor.



$$|X_C| = \frac{1}{2\pi fC} = \frac{1}{1.382 \times 10^{-5}} = 72.34 \text{ k}\Omega$$

Input and Output Signals: f=1kHz

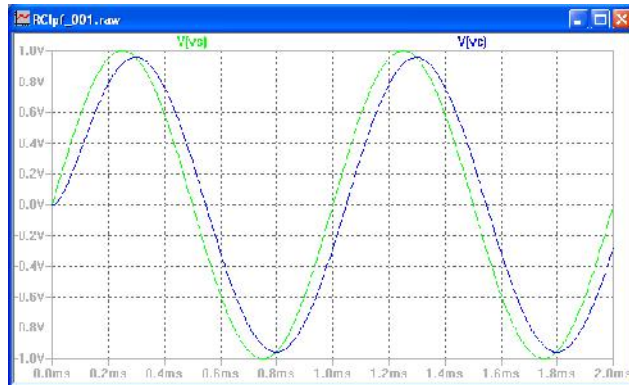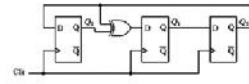



Output signal (blue) has almost same amplitude as input signal (green).

Input and Output Signals f=3.2 kHz

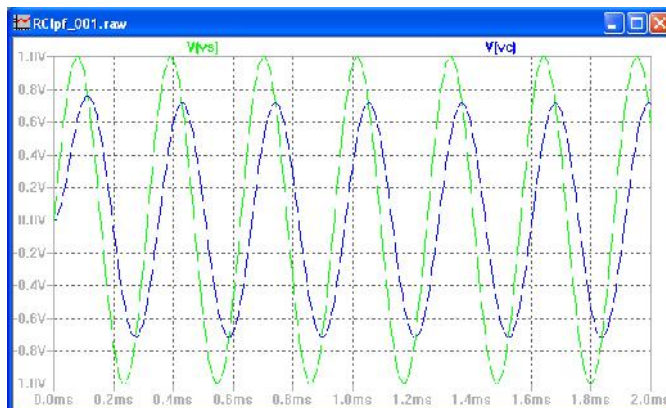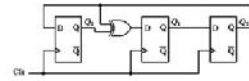

Now output signal (blue) is only about 0.7 times the input signal (green).
In this case $X_C = 22.6 \text{ k}\Omega$ and $R1 = 22 \text{ k}\Omega$


Input and Output Signals f=10 kHz

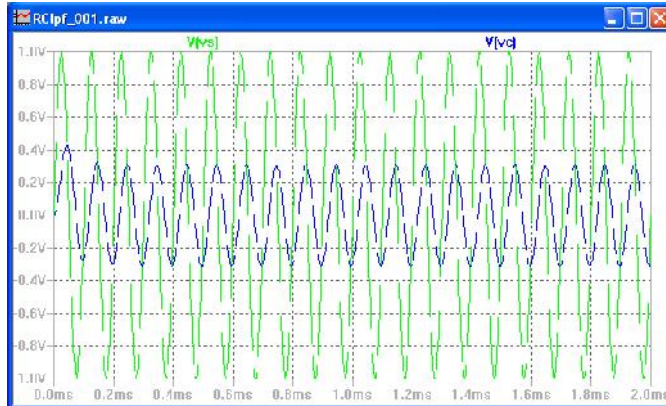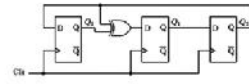

Output signal (blue) is now about 0.3 times the input signal (green).
In this case $X_C = 7.23 \text{ k}\Omega$, $R_1 = 22 \text{ k}\Omega$

Thus, RC Circuit 1 passes low frequencies and attenuates high frequencies. The circuit is called a RC LPF (lowpass filter).

Sinusoidal Parameters


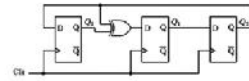


- A sinusoidal waveform

$$s(t) = A \cdot \cos(2\pi f t + \theta)$$
 is characterized by its amplitude A , its frequency f and its phase θ .
- A delayed (by t_d) sinusoidal waveform is


$$s(t) = A \cdot \cos(2\pi f (t - t_d))$$
- Thus $\theta = -2\pi f t_d$ (in radians) or $t_d = -\theta / (2\pi f)$ (in seconds), i.e., a delayed sinusoid corresponds to a phase shift of the sinusoid.

Zoom-In for Phase Change

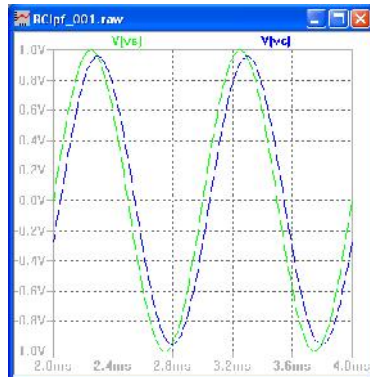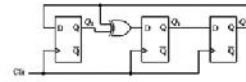

1 kHz: Phase shift $\theta = -17^\circ$


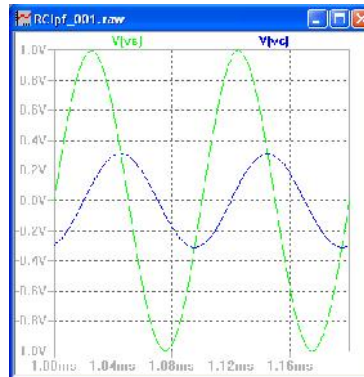
At 1 kHz $v_C(t)$ is almost equal to $v_S(t)$ in amplitude and phase.



10 kHz: Phase shift $\theta = -72^\circ$

$v_C(t)$ is delayed by about 0.02 ms (1/5 of period of 0.1 ms) from $v_S(t)$.

Analysis Using Phasors

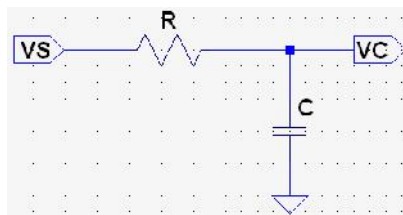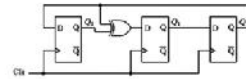

\underline{V}_S (VS) is input phasor
 \underline{V}_C (VC) is output phasor
 $Z_C = 1/(j2\pi fC)$ is capacitor impedance


Using voltage division:

$$\underline{V}_C = \frac{\frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} \underline{V}_S = \frac{1}{1 + j2\pi fRC} \underline{V}_S$$

Define: $H(f) = \frac{V_C}{V_S} = \frac{1}{1 + j2\pi fRC}$

System Function

Complex Number z

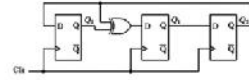

$$z = a + j b \quad \text{Cartesian representation}$$

$$z = r e^{j\theta} \quad \text{Polar representation}$$

Using Euler's formula:

$$j = \sqrt{-1}$$


$$z = r e^{j\theta} = r \cos \theta + j r \sin \theta$$

$$\Rightarrow \boxed{\begin{aligned} a &= r \cos \theta, & b &= r \sin \theta \\ r &= \sqrt{a^2 + b^2}, & \theta &= \tan^{-1} \left(\frac{b}{a} \right) \end{aligned}}$$

Conversion between Cartesian (a,b) and polar (r,θ) format


$a = \text{Re}\{z\}$: Real part of z , $b = \text{Im}\{z\}$: Imaginary part of z
 $r = |z|$: Magnitude of z , $\theta = \arg(z)$: Angle or Phase of z

System Function $H(f)$

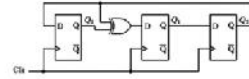

- The system function $H(f)$ is a complex-valued function of frequency f .
- For a given system, $H(f)$ is obtained by measuring the system output \underline{V}_O in response to a sinusoidal input \underline{V}_S and then taking the ratio $H(f) = \underline{V}_O / \underline{V}_S$ where \underline{V}_O and \underline{V}_S are phasors.
- In polar representation, $|H(f)|$ is called the **magnitude of the frequency response**.
- Also in polar representation, $\arg(H(f))$ is called the **phase of the frequency response**.

RC LPF Frequency Response

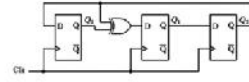

For the RC LPF:



$$H(f) = \frac{1}{1+j2\pi fRC} = \frac{1}{r e^{j\theta}} = \frac{1}{r} e^{-j\theta}$$

$$\text{with } r = \sqrt{1 + (2\pi fRC)^2}, \quad \theta = \tan^{-1}(2\pi fRC)$$


$$\Rightarrow |H(f)| = \frac{1}{\sqrt{1+(2\pi fRC)^2}}$$

$$\arg(H(f)) = -\tan^{-1}(2\pi fRC)$$

Plot of Frequency Response

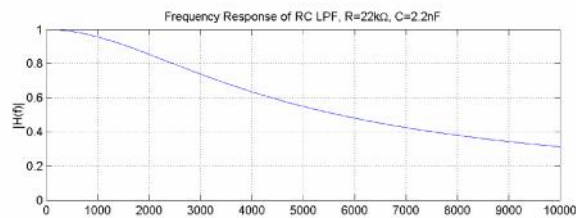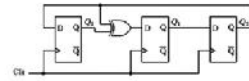


Magnitude $|H(f)|$ of RC LPF frequency response.

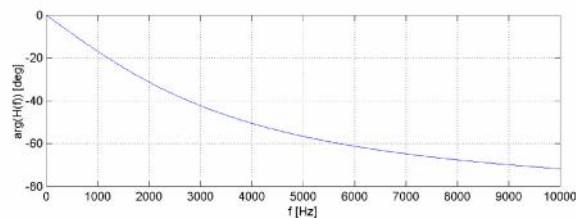

Phase $\arg(H(f))$ of RC LPF frequency response in degrees.

Matlab Script for Plots

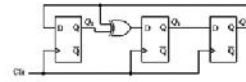


```

1  %RClpf_001  Frequency Response of RC LPF
2
3  R = 22e3;           %Resistor
4  C = 2.2e-9;        %Capacitor
5  f1 = 0; f2 = 10e3; N = 500;
6
7  ff = linspace(f1,f2,N); %Frequency axis
8  Hf = 1./(1+j*2*pi*ff*R*C); %H(f)
9
10 subplot(211)
11 plot(ff,abs(Hf)),grid %Magnitude of H(f)
12 ylim([0 1])
13 ylabel('|H(f)|')
14 title('Frequency Response of RC LPF, R=22k\Omega, C=2.2nF')
15 subplot(212)
16 plot(ff,(180/pi)*angle(Hf)),grid %Phase of H(f)
17 xlabel('f [Hz]'),ylabel('arg(H(f)) [deg]')

```

Cutoff Frequency f_L

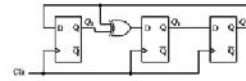

- Note that


$$|H(f)| = \frac{1}{\sqrt{1 + (2\pi fRC)^2}} \approx \begin{cases} 1, & f < \frac{1}{2\pi RC}, \\ \frac{1}{2\pi fRC}, & f > \frac{1}{2\pi RC}. \end{cases}$$

- And

$$|H(f_L)| = \frac{1}{\sqrt{2}} \approx 0.707, \quad \text{where } f_L = \frac{1}{2\pi RC}$$



- The frequency f_L at which $2\pi f_L RC = 1$ is called the **cutoff frequency** of the lowpass filter.

-3 dB Frequency f_L

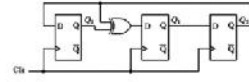


- $|H(f)|$ is often expressed in decibels as $20 \log_{10}(|H(f)|)$ dB
- At the cutoff frequency f_L
 $20 \log_{10}(|H(f_L)|) = -20 \log_{10}(\sqrt{2}) = -10 \log_{10}(2) \approx -3$ dB
- Thus f_L is also called the **-3 dB frequency** of the lowpass filter.

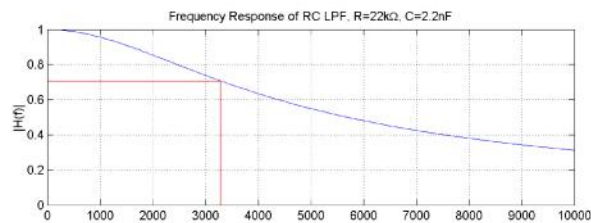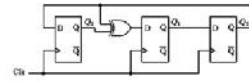RC LPF Frequency Response with -3 dB Frequency Shown





$$|H(f_L)| = 0.707$$

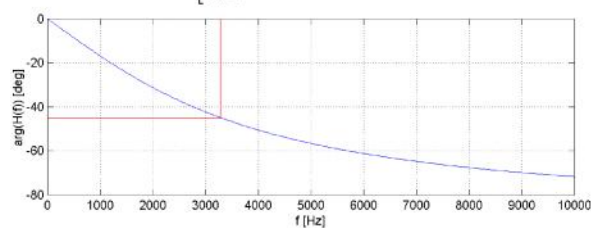

$$\arg(H(f_L)) = -45 \text{ deg}$$



RC Highpass Filter (HPF)

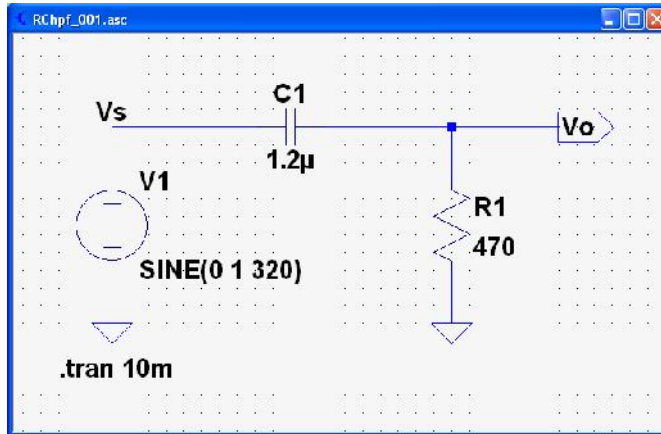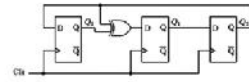

For a HPF the roles of the capacitor and the resistor are interchanged.

Here the input is a sine with frequency 320 Hz and the output is taken across the 470 Ω resistor



Input and Output Signals: f = 320 Hz

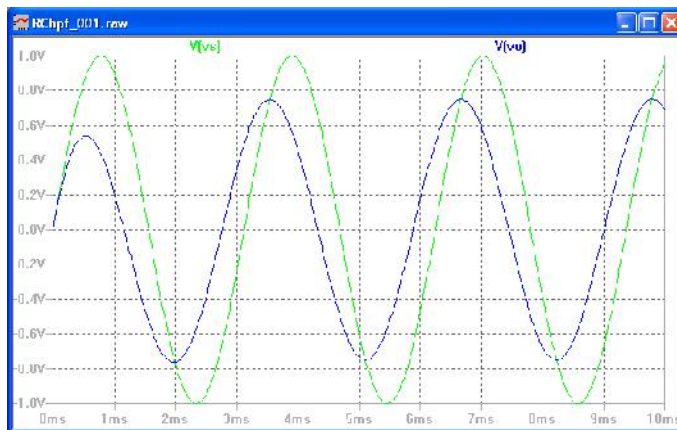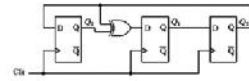

At 320 Hz,
 $|XC|=414.5 \Omega$,
 $|H(f)|=0.75$, and
 $\arg(H(f))=+41 \text{ deg}$

Note that for the HPF the output voltage leads compared to the input voltage. For a LPF the opposite is true, i.e., the output voltage lags compared to the input voltage.

HPF Analysis Using Phasors

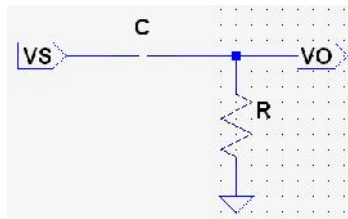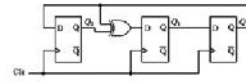


\underline{V}_S (VS) is input phasor
 \underline{V}_O (VO) is output phasor
 $Z_C = 1/(j2\pi fC)$ is capacitor impedance

Using voltage division:

$$\underline{V}_O = \frac{R}{\frac{1}{j2\pi fC} + R} \underline{V}_S = \frac{j2\pi fRC}{1 + j2\pi fRC} \underline{V}_S$$

System Function: $H(f) = \frac{\underline{V}_O}{\underline{V}_S} = \frac{j2\pi fRC}{1 + j2\pi fRC}$

RC HPF Frequency Response

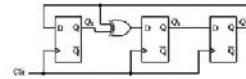

$$|H(f)| = \frac{2\pi fRC}{\sqrt{1 + (2\pi fRC)^2}} \quad \text{Magnitude of } H(f)$$

$$\arg(H(f)) = \frac{\pi}{2} - \tan^{-1}(2\pi fRC) \quad \text{Phase of } H(f)$$

$$|H(f)| = \frac{2\pi fRC}{\sqrt{1 + (2\pi fRC)^2}} \approx \begin{cases} 2\pi fRC, & f < \frac{1}{2\pi RC} \\ 1, & f > \frac{1}{2\pi RC} \end{cases}$$

Cutoff frequency f_H :

$$|H(f_H)| = \frac{1}{\sqrt{2}} \approx 0.707 \quad \text{for } f_H = \frac{1}{2\pi RC}$$

RC HPF Frequency Response with -3 dB Frequency Shown

