



BUILD
A
**“FUZZBOX” FOR
UNDER \$3**

DEFINITELY NOT RECOMMENDED FOR USE
BY MUSICAL PURISTS, THE FUZZBOX IS
INTENDED TO GIVE ROCK-'N'-ROLL
MUSIC THAT BIG, BRASSY SOUND

By **CRAIG ANDERTON**, W82JQC

AS YOU LISTEN to rock-'n'-roll by the big-time performers, do you often wonder how they can get that fuzzy, raspy, piercing sound from an electric guitar while nonprofessional groups sound distinctively small-time? The answer lies in the use of an electronic gadget called a "Fuzzbox"—and you can build one for about \$3 in a matter of minutes!

Most commercial "fuzz"-producing de-

vices are transistorized and must be powered by a battery or external line power. But this *batteryless* Fuzzbox gives the same nerve-shattering sound produced by transistorized commercial units selling for \$25 and up.

How It Works. The utter simplicity of the Fuzzbox is shown in Fig. 1. Its only parts are a s.p.d.t. momentary-
(Continued on page 92)