

---

E40M

RC Filters

# Reading


---

- Reader:
  - The rest of Chapter 7
    - 7.1-7.2 is about log-log plots
    - 7.4 is about filters
- A & L
  - 13.4-13.5
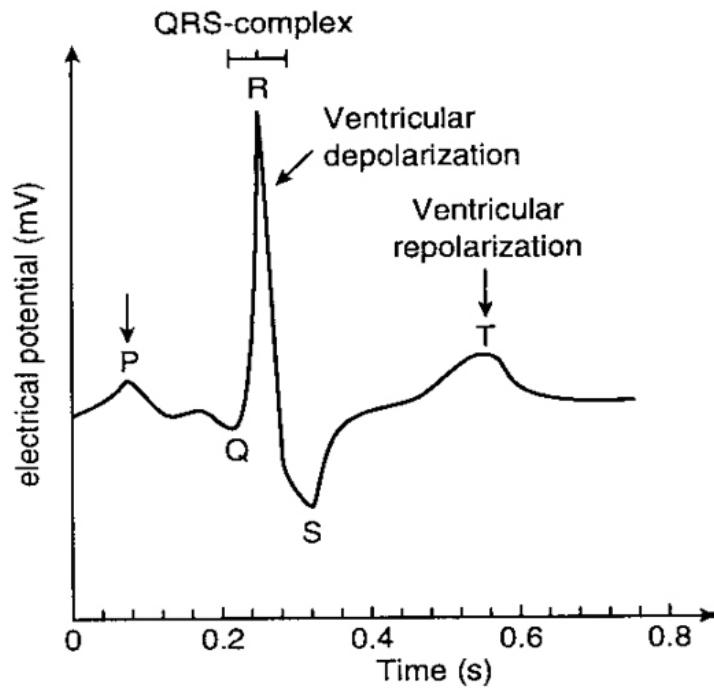
# EKG (Lab 4)

---

- Concepts
  - Amplifiers
  - Impedance
  - Noise
  - Safety
  - Filters
- Components
  - Capacitors
  - Inductors
  - Instrumentation and Operational Amplifiers



In this project we will build an electrocardiogram (ECG or EKG). This is a noninvasive device that measures the electrical activity of the heart using electrodes placed on the skin.

# RC Circuit Analysis Approaches




---

1. For finding voltages and currents as *functions of time*, we solve linear differential equations or run EveryCircuit.
2. For finding the response of circuits to *sinusoidal signals*,\* we use impedances and “frequency domain” analysis

\*superposition can be used to find the response to any periodic signals

# Key Ideas on RC Circuit Frequency Analysis - Review

---

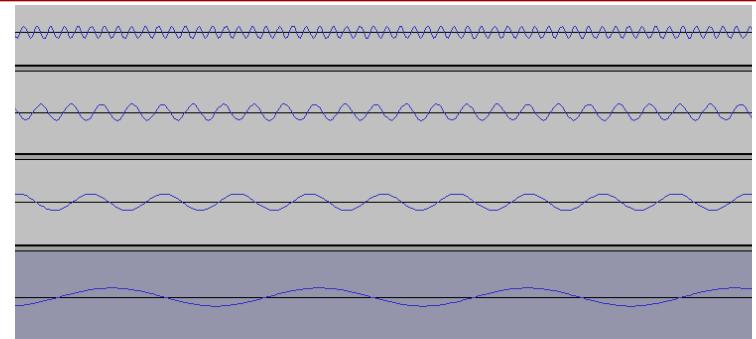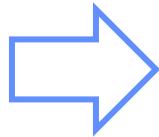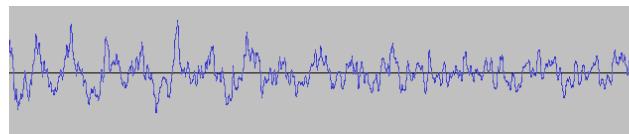

- All voltages and currents are sinusoidal
- So we really just need to figure out
  - What is the amplitude of the resulting sinewave
  - And sometimes we need the phase shift too (but not always)
- These values don't change with time
  - This problem is very similar to solving for DC voltages/currents

# Key Ideas on Impedance - Review

- Impedance is a concept that generalizes resistance:
  - For sine wave input


$$Z = \frac{mag(V)}{mag(i)}$$

Add  $j$  to represent  
90° phase shift

- $Z$  for a resistor is just  $R$ 
  - It does not depend on frequency, it is simply a number.
- What about a capacitor?

$$Z_C = \frac{V}{i} = \frac{V}{CdV/dt} = \frac{V_0 \sin(2\pi F t)}{2\pi F C V_0 \cos(2\pi F t)}$$

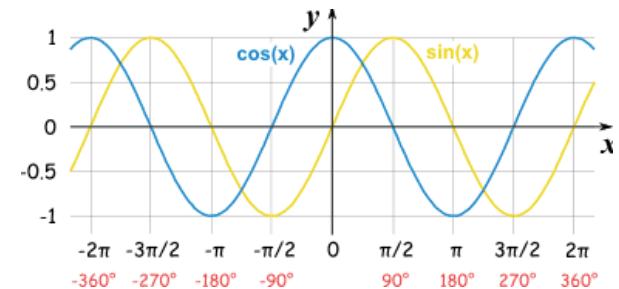
$$Z_C = \frac{V}{i} = \frac{1}{j * 2\pi F C}$$


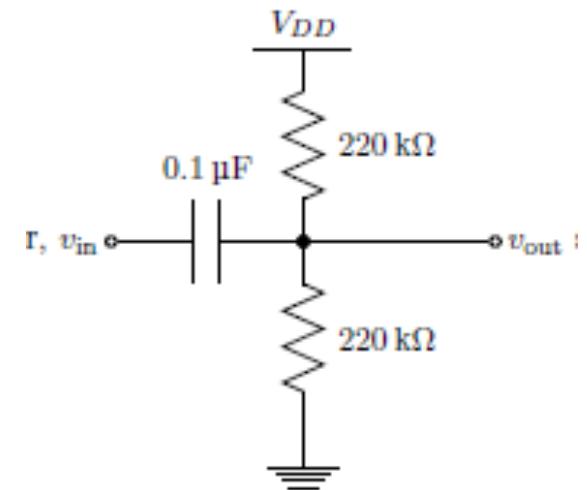
# Analyzing RC Circuits Using Impedance - Review


---

- The circuit used to couple sound into your Arduino is a simple RC circuit.
- This circuit provides a DC voltage of  $V_{dd}/2$  at the output.
- For AC (sound) signals, the capacitor will block low frequencies but pass high frequencies. (High pass filter).
- For AC signals, the two resistors are in parallel, so the equivalent circuit is shown on the next page.




# Analyzing RC Circuits Using Impedance – Review (High Pass Filter)

---

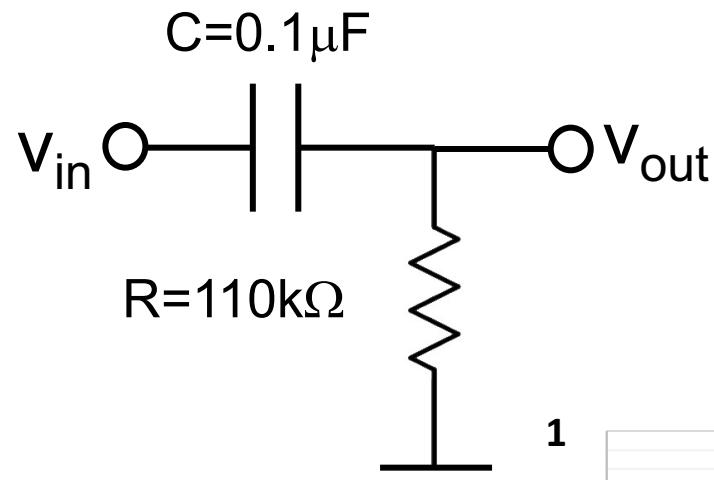

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{R + \frac{1}{j * 2\pi F C}} = \frac{j * 2\pi F R C}{1 + j * 2\pi F R C}$$

RC = 11ms;  $2\pi R C$  about 70ms

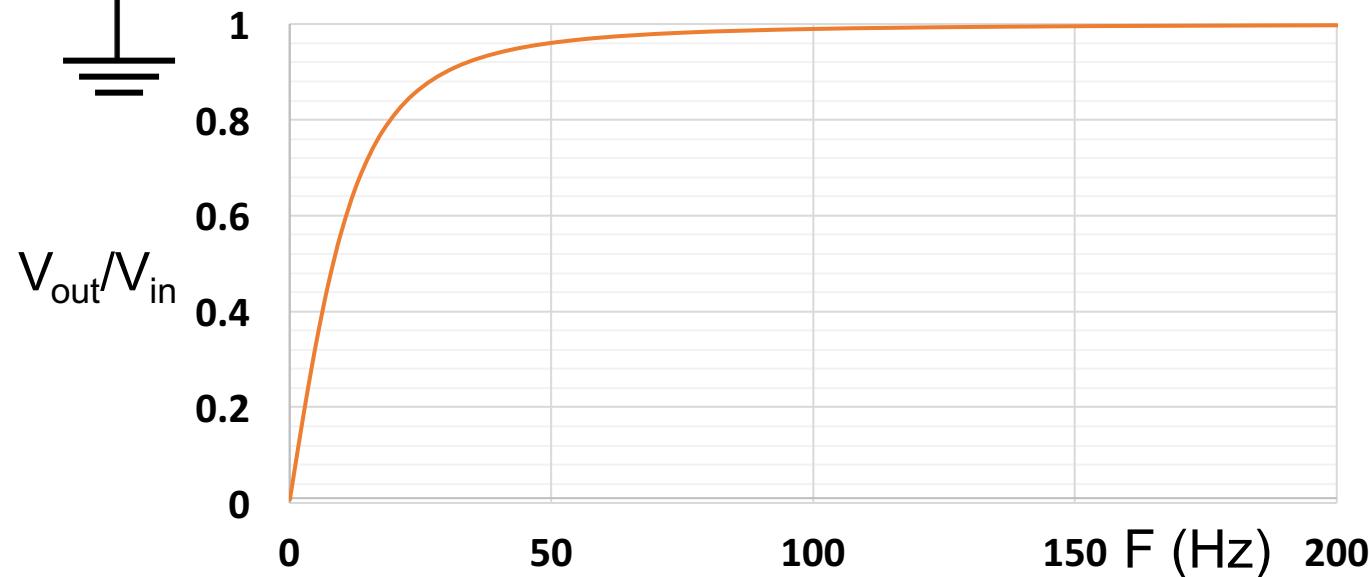

---

# **RC FILTERS**


# RC Circuits Can Make Other Filters

---

- Filters are circuits that change the relative strength of different frequencies
- Named for the frequency range that passes through the filter
  - Low pass filter:
    - Passes low frequencies, attenuates high frequency
  - High pass filter
    - Passes high frequencies, attenuates low frequencies
  - Band pass filter
    - Attenuates high and low frequencies, lets middle frequencies pass

# RC Low Pass Filters

---

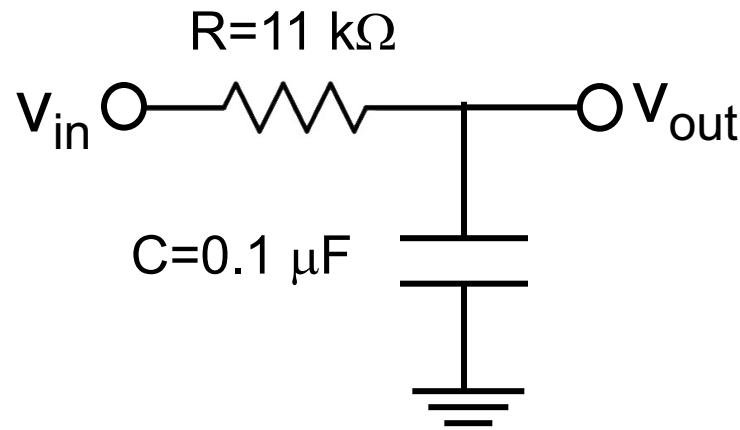

- Let's think about this before we do any math

- Very low frequencies →


$$\begin{aligned} RC &= 11 \times 10^3 \times 0.1 \times 10^{-6} \text{ s} \\ &= 1.1 \text{ ms} \end{aligned}$$

- Very high frequencies →

$$2\pi RC = 6.9 \text{ ms}$$


$$1/(2\pi RC) = 145 \text{ Hz}$$

# RC Low Pass Filters

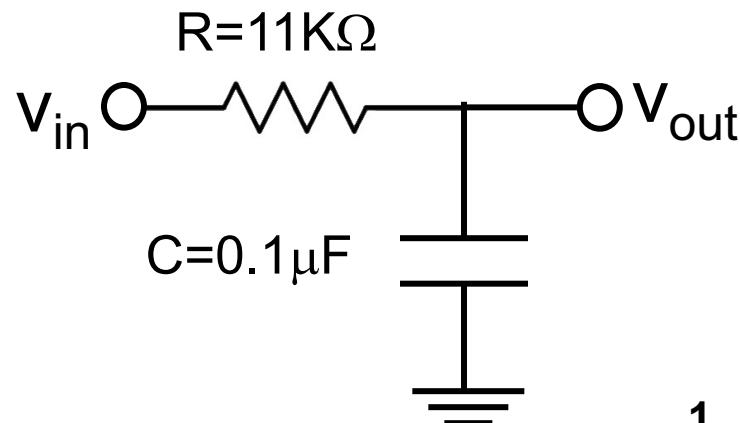

$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j * 2\pi FC}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF/F_c}$$


$$F_c = 1/[2\pi RC]$$

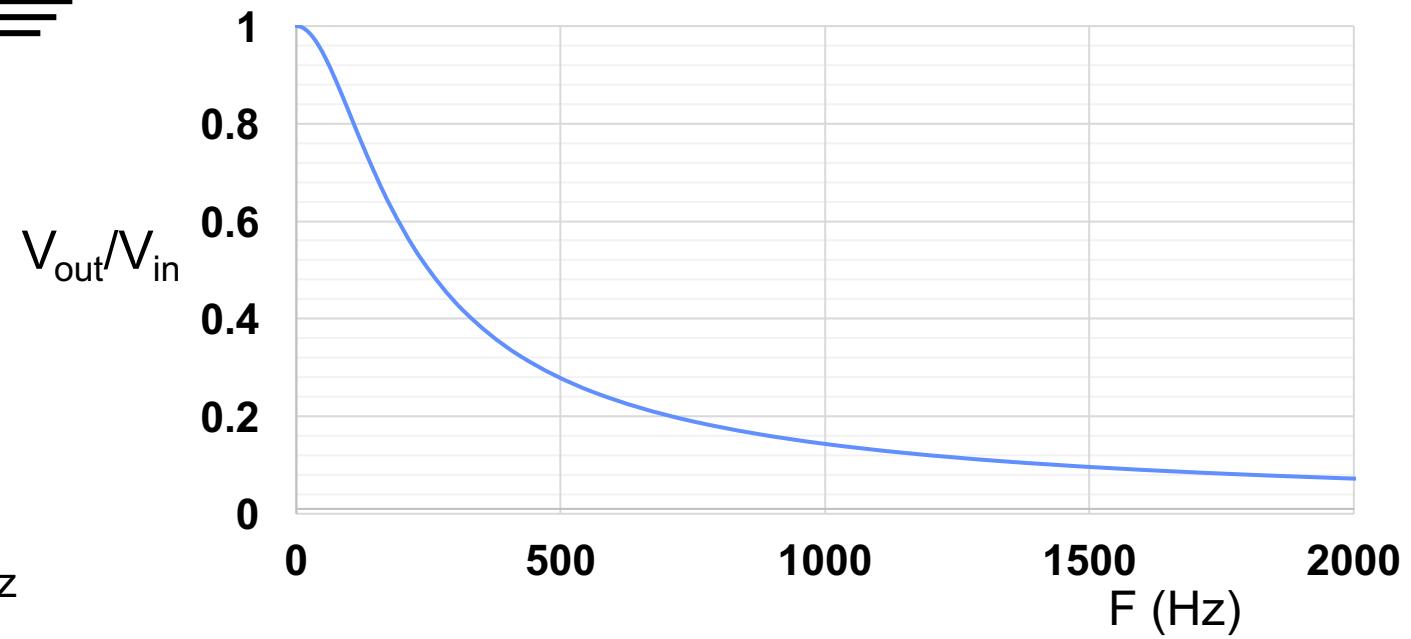


$$RC = 1.1 \text{ ms}$$
$$F_c = 1/[2\pi RC] = 145 \text{ Hz}$$

# RC Filters – Something a Little More Complicated

---

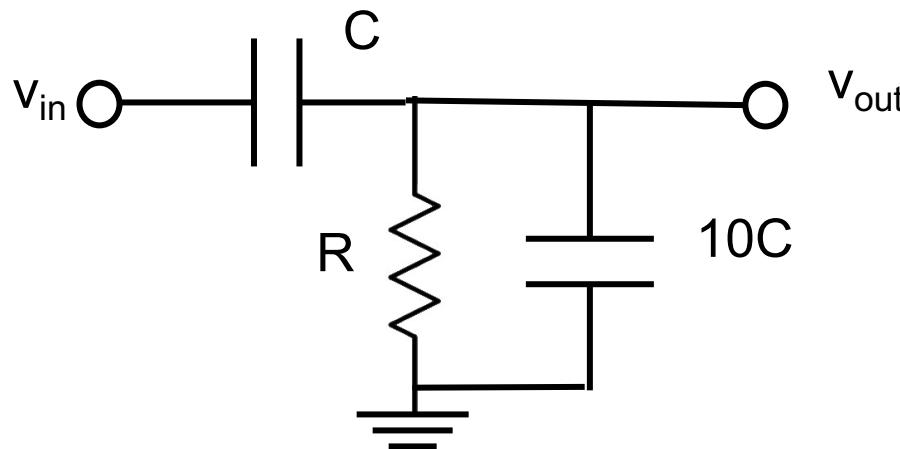


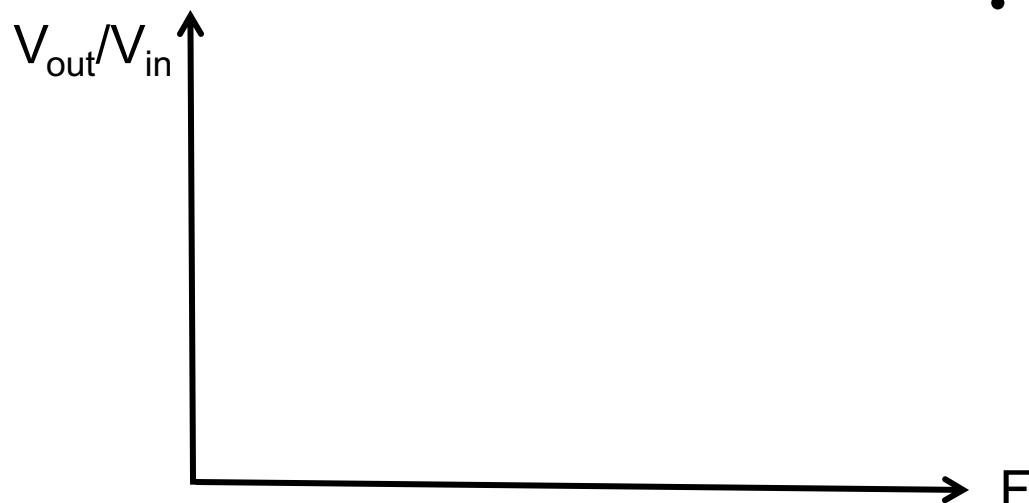- Let's think about this before we do any math
- Very low frequencies →
- Very high frequencies → capacitive divider




# RC Filters – Something More Complicated

---

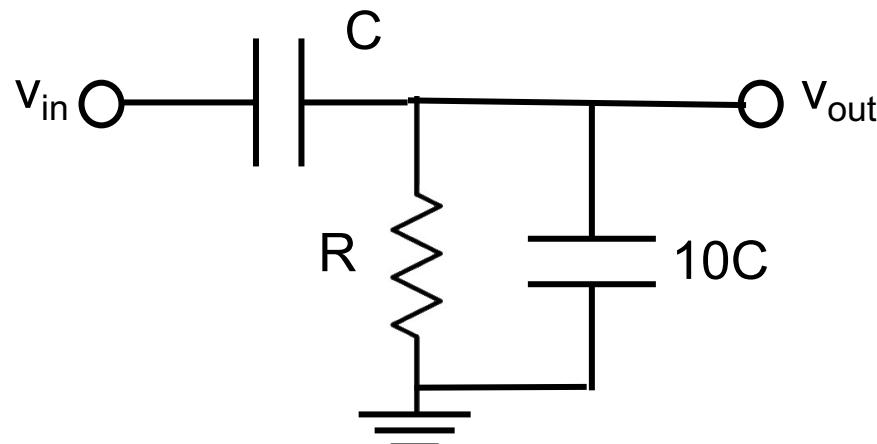

$$Z_1 = \frac{1}{j * 2\pi F C}$$
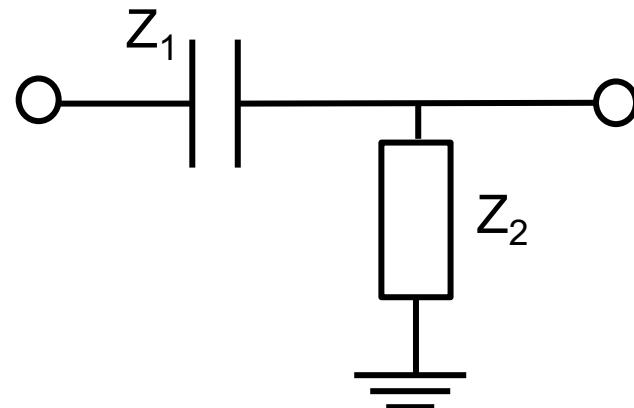
$$Z_2 = \frac{1}{\frac{1}{R} + j * 2\pi F 10C} = \frac{R}{1 + j * 2\pi F 10RC}$$




$$\frac{V_{out}}{V_{in}} = \frac{\frac{R}{1 + j * 2\pi F 10RC}}{\frac{R}{1 + j * 2\pi F 10RC} + \frac{1}{j * 2\pi F C}}$$

$$= \frac{j * 2\pi F R C}{j * 2\pi F R C + (1 + j * 2\pi F 10RC)} = \frac{j * 2\pi F R C}{1 + j * 2\pi F 11RC}$$
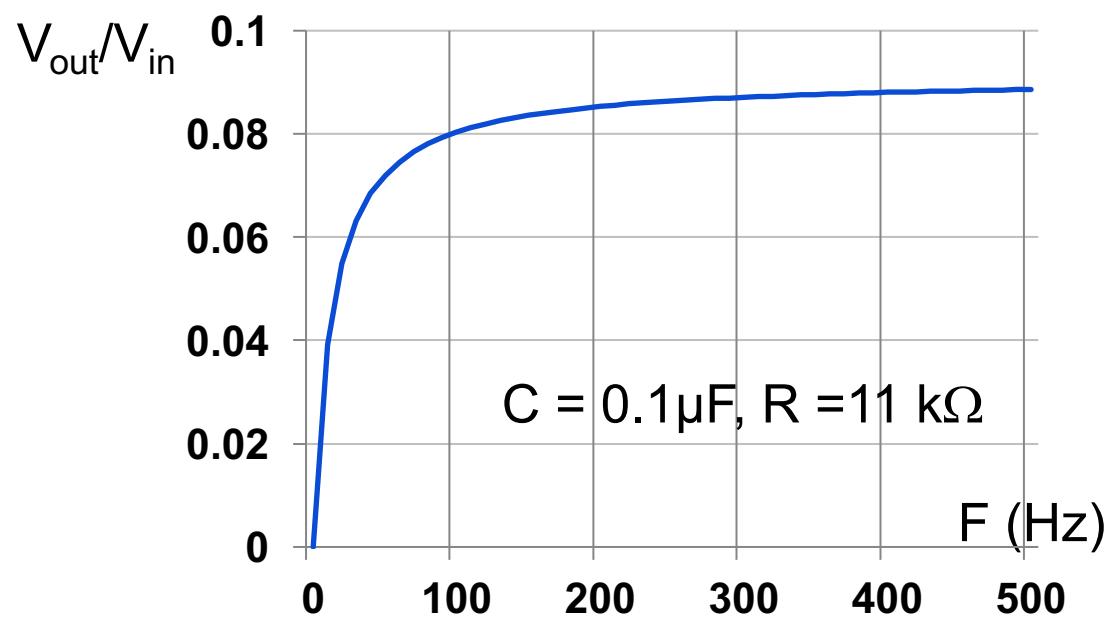
# RC Filters – Something More Complicated


---

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j * 2\pi F R C}{1 + j * 2\pi F R C} \rightarrow \text{Simplify using } F_c = 1 / [2\pi R C] = 13 \text{ Hz}$$



# What If We Combine Low Pass and High Pass Filters?


---

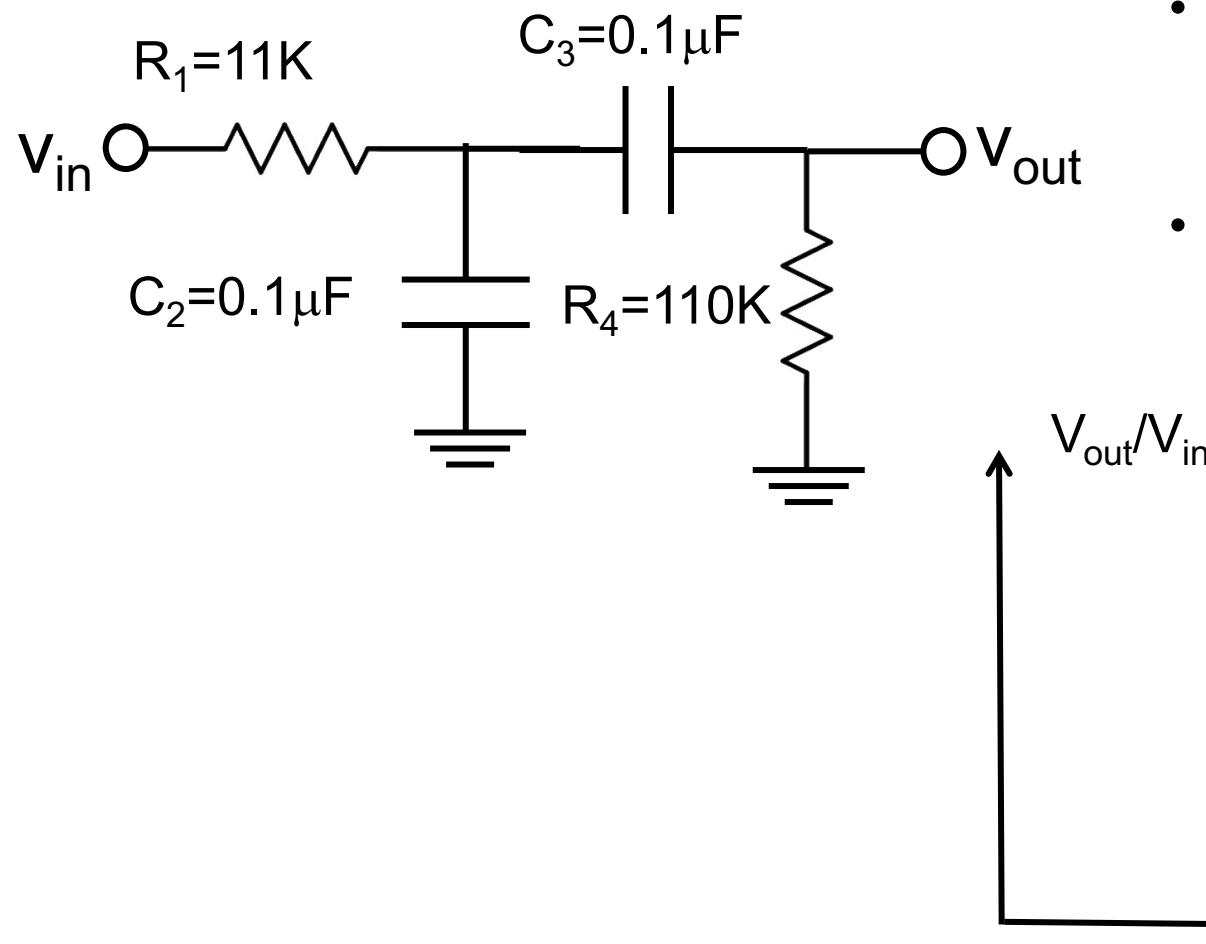

- What do you think it will do?
- We'll use a filter that operates like this in the ECG lab project.

# Analysis Options: Nodal Analysis

---

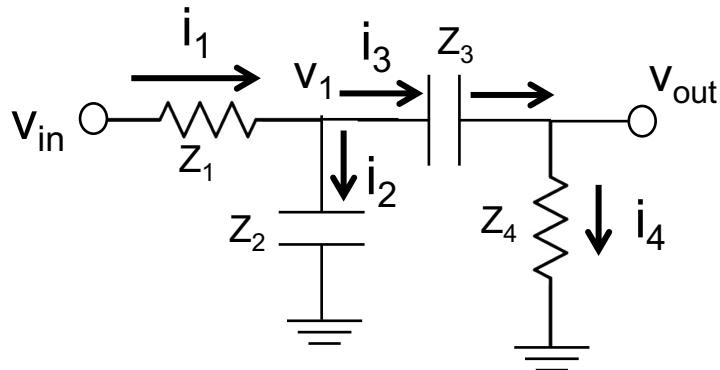


- Let's first solve it using  $Z_1-Z_4$  and nodal analysis

$$i_3 = i_4 \quad \therefore \frac{V_{out} - V_1}{Z_3} = \frac{V_{out}}{Z_4} \quad \therefore V_{out} = V_1 \frac{Z_4}{Z_3 + Z_4}$$

$$i_1 = i_2 + i_3 \quad \therefore \frac{V_1 - V_{in}}{Z_1} = \frac{V_1}{Z_2} + \frac{V_1 - V_{out}}{Z_3}$$

- We have 2 equations in 2 unknowns ( $V_1$  and  $V_{out}$ ). So we could solve this for  $V_{out}/V_{in}$  in terms of the impedances.
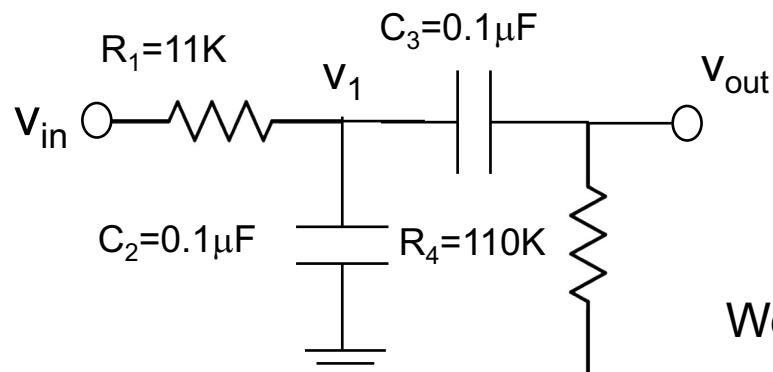
# Analysis Options: Using R, C and Voltage Dividers



For convenience, let  $s = j^*2\pi F$


$$\frac{V_{out}}{V_1} = \frac{R_4}{R_4 + \frac{1}{sC_3}} = \frac{sR_4C_3}{1 + sR_4C_3}$$

We can replace  $R_4$ ,  $C_3$  and  $C_2$  with  $Z_{eqv}$

$$Z_{eqv} = \frac{\frac{1}{sC_3}}{\frac{1}{R_4} + \frac{1}{sC_2}} = \frac{\frac{1}{sC_3}}{\frac{1}{1 + sR_4C_3} + sC_2} = \frac{1 + sR_4C_3}{sC_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}$$

$$\therefore \frac{V_1}{V_{in}} = \frac{\frac{1 + sR_4C_3}{sC_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}}{R_1 + \frac{1 + sR_4C_3}{sC_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}} = \frac{1 + sR_4C_3}{1 + sR_4C_3 + sR_1C_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}$$

# Output Response

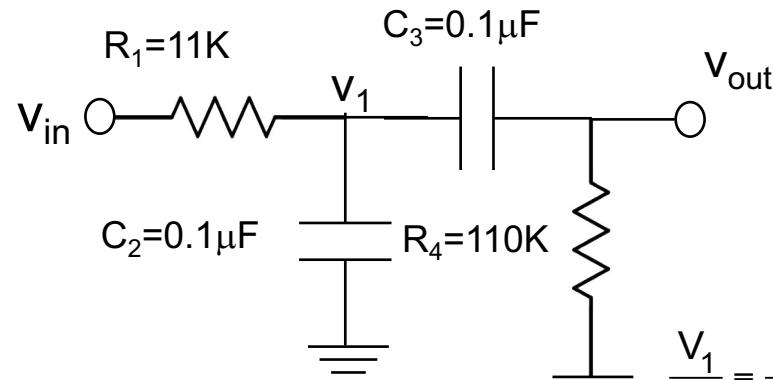


$$\frac{V_{out}}{V_1} = \frac{R_4}{R_4 + \frac{1}{sC_3}} = \frac{sR_4C_3}{1 + sR_4C_3}$$

$$\frac{V_1}{V_{in}} = \frac{\frac{1 + sR_4C_3}{sC_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}}{R_1 + \frac{1 + sR_4C_3}{sC_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}} = \frac{1 + sR_4C_3}{1 + sR_4C_3 + sR_1C_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)}$$


$$\frac{V_{out}}{V_1} \cdot \frac{V_1}{V_{in}} = \frac{sR_4C_3}{1 + sR_4C_3 + sR_1C_2 * \left( \frac{C_3}{C_2} + 1 + sR_4C_3 \right)} = \frac{sR_4C_3}{1 + s(R_4C_3 + R_1C_2 + R_1C_3) + s^2R_1C_2R_4C_3}$$

$$\text{Or, } \frac{V_{out}}{V_{in}} = \frac{j * 2\pi F R_4 C_3}{1 + j * 2\pi F (R_4 C_3 + R_1 C_2 + R_1 C_3) + (j * 2\pi F)^2 R_1 C_2 R_4 C_3}$$


# Output Response

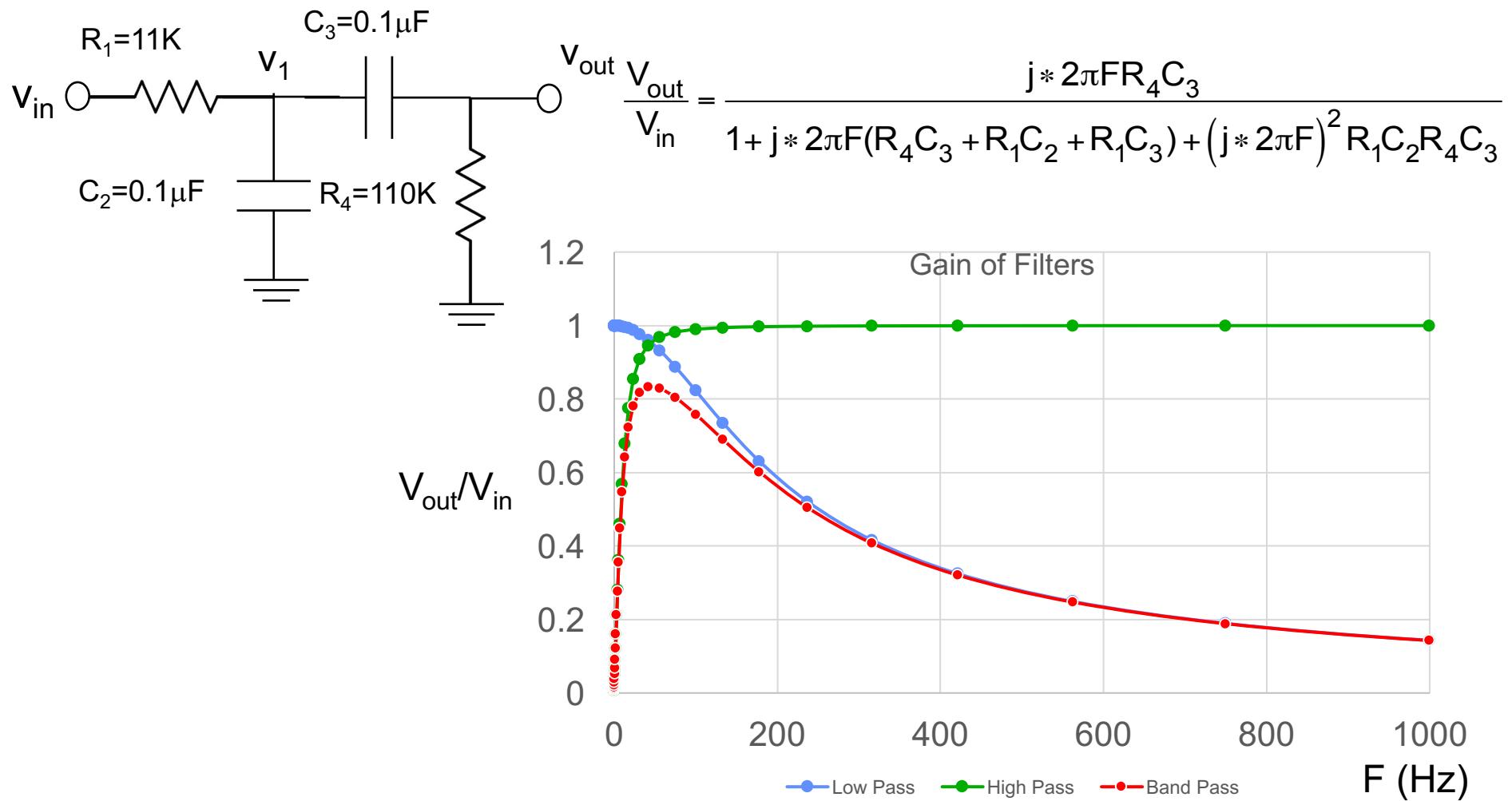

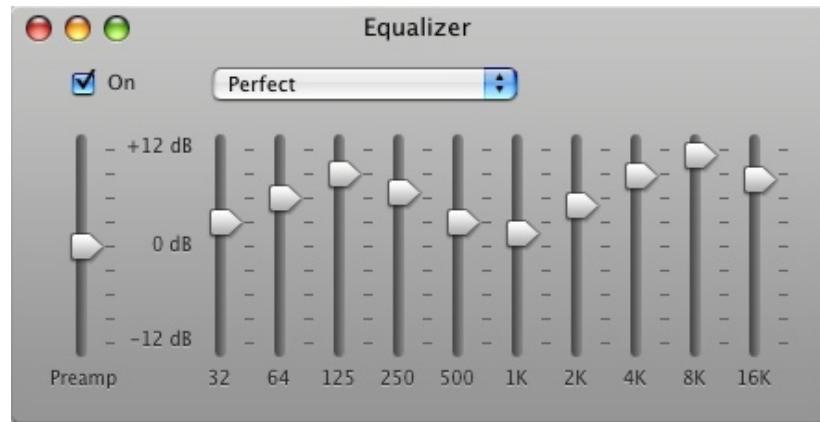
# So What Are The Answers To These Questions?



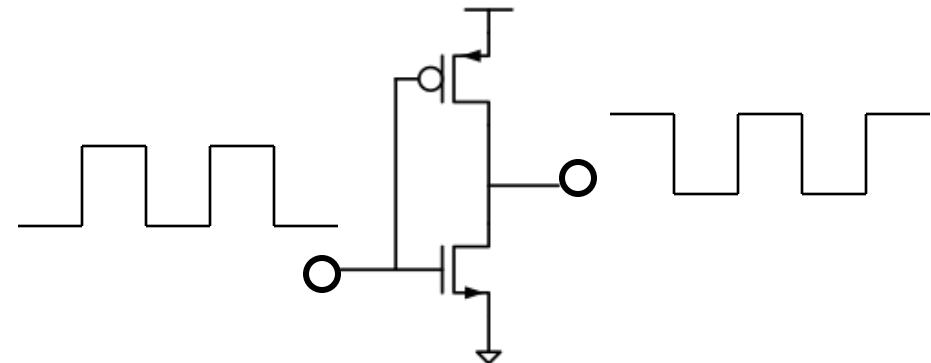How do we design circuits that respond to certain frequencies?



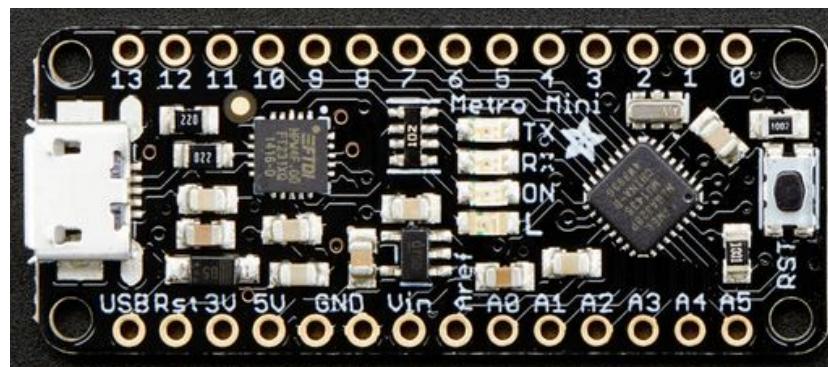What determines how fast CMOS circuits can work?



Why did you put a  $200\ \mu F$  capacitor between Vdd and Gnd on your Arduino?

# Learning Objectives

---

- Become more comfortable using impedance
  - To solve RC circuits
- Understand how to characterize RC circuits
  - Which are low pass, high pass and bandpass filters
- Be able to sketch the frequency dependence of an RC circuit by reasoning about how capacitors behave at low and high frequencies