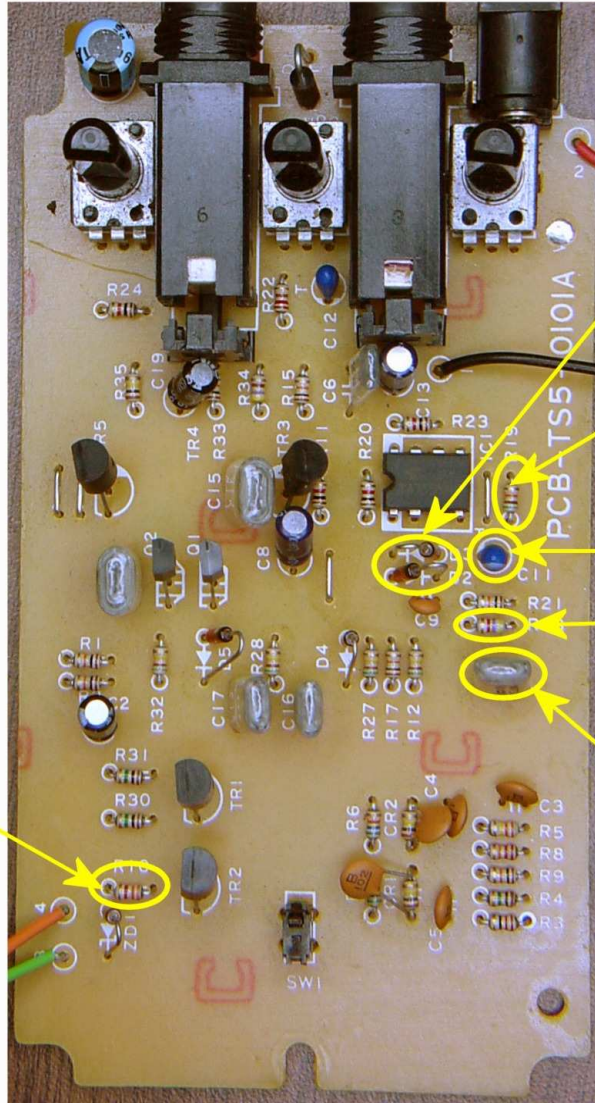


470 ohm to make LED brighter




D2, D3

R19

C11

R18

C10

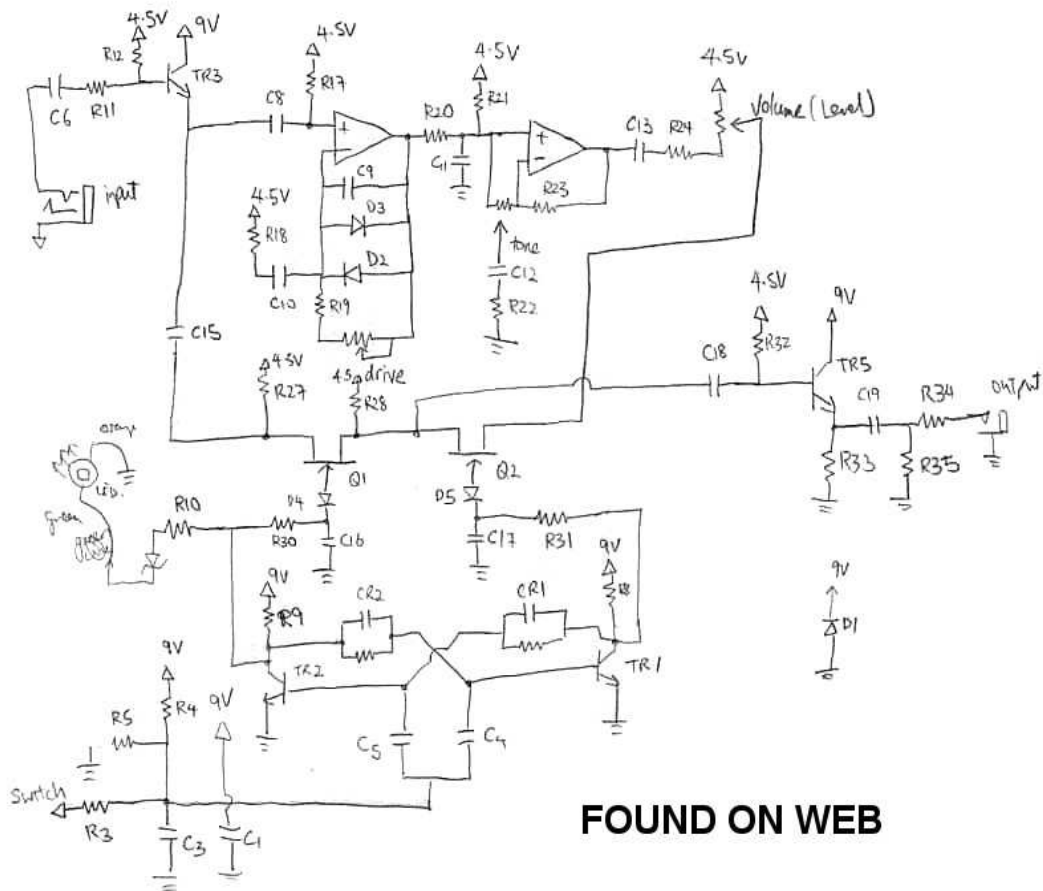

FOUND ON WEB

Ibanez TS-9 TubeScreamer

Circuit Explanation

The signal enters and passes through C1, R1, while going past R2, which helps bias Q1, a transistor buffer. After going through the buffer, the it passes through C2 and into the clipping stage. R4 is biasing the opamp. The signal enters into pin 3.

The signal is boosted through pins 1 and 2 and is controlled by the value the gain pot plus the resistance of R6, in conjunction with R5 and C4. With that said, this means that R6 controls the amount of gain with the gain pot at its minimum. C3 shaves a little bit of highs and keeps the opamp stable.


Since C4 and R5 set what frequencies we are boosting and clipping, changing these values will change that frequency as well as alter the gain a bit. If you go to <http://www.indyguitarist.com/filter.htm> you can input the values of C4 and R5 (resistance and capacitance) and figure out what frequencies you want to clip. As you'll see, adding resistance adds a bit of bass but also makes the gain a bit less.

The combinations of diodes D5 and D6 allow for symmetrical 'soft' clipping.

After leaving this first gain stage, the signal goes through R7 and passes C5. This combination (R7 and C5) form a 'low pass filter' which shaves off highs. R8 helps to bias the next stage which is the tone control.

The signal enters into pin 5. R10 provides enough of a gain boost (or signal boost) to make the tone control an 'active' tone control, meaning it not only cuts highs, it boosts them as well without losing volume or signal. This is an interesting tone control, however – as the tone pot is turned down, it shaves off more highs since it is tied back into the signal after R7. When turned up, it boosts highs since it has a capacitor and resistor (C6 and R9) going to ground, whichs once again controls gain and the frequencies being boosted.

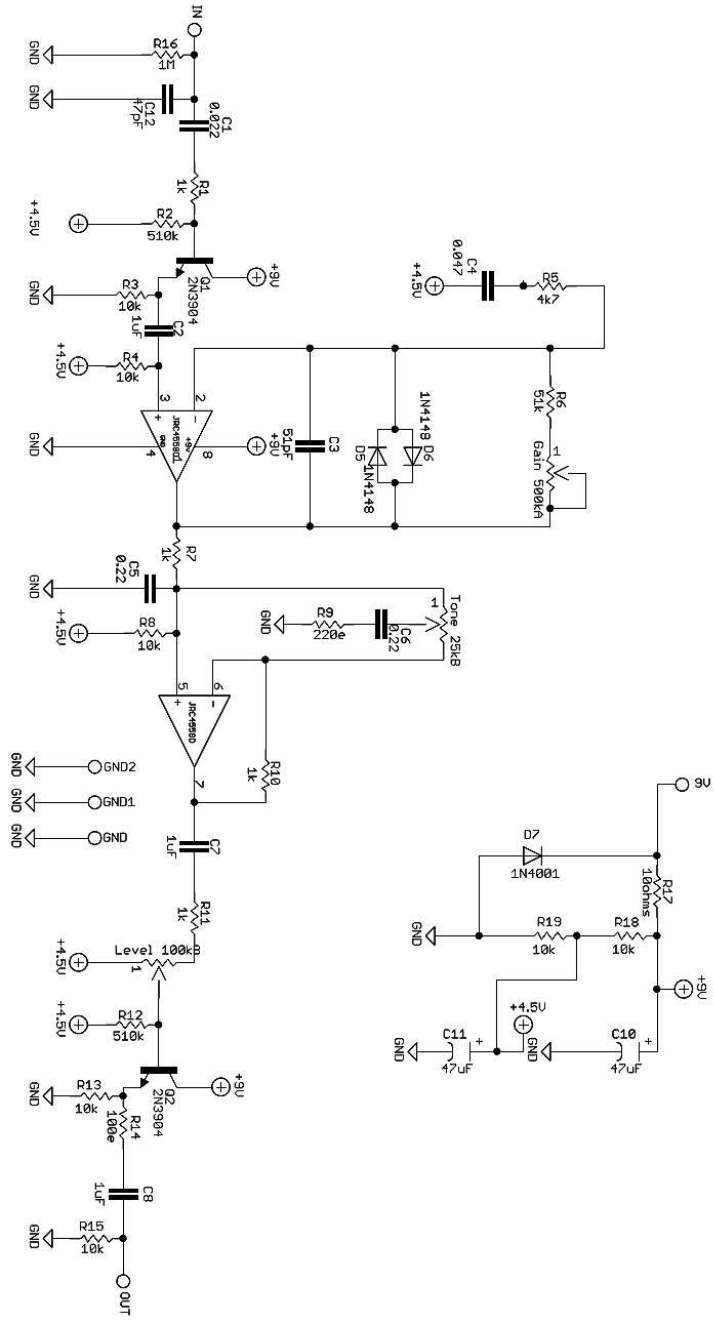The signal leaves and passes through C7 and R11 before going into the volume control. The signal leaves the volume control through lug 2 and goes into the last stage, an output buffer, which is setup just like Q1. The signal leaves this output buffer and goes through R14, C8, and passes R15 and then goes to the output.



BSM (Brent Mason) MOD

A	1K RESISTOR	
B	.22UF x 2 in parallel CAP	
C	10K RES	
D	1N4001	
E	1n4001 + 1n4001 SERIES	
F (2 OF THEM)	1 UF FILM CAPS	
G	.15 uf or .047 + .1 uf in parallel (results in the same thing)	

Ibanez TS-9 316 MOD

Location	Mod value
A	1K RESISTOR
B	.22UF
C	10K RESISTOR
D	LED
E	LED + 4148 in SERIES
F (2 OF THEM)	1 UF FILM CAPS


Ibanez TS-9 standard Mod


Location	Stock value	Mod value	What it affects
B	.047 uf	.1 uf	Adds bottom end. For more, go .22 uf
D		LED & germanium 1n34a in series	Adds fullness, depth, and dynamics
E		1N4001	
A	4.7k	3.3k	The lower the value, the more distortion available.
E		Jrc4558d IC CHIP	Not always needed, will not make a big difference...but there is a lot of hype around this change!
F	1uf elec	1uf film caps	Helps low end to not distort

Ibanez TS-9 Extra's


Location	Mod Value	What it affects
1A	.047uf/.1uf/ .15uf/.47uf/ 1uf	Experiment with value. It will change the frequencies that the tone knob affects.

C	10k	Will allow pedal to clean up when gain knob is turned down
2A	Raise value - .44uf, .1 uf	Raising value will decrease the highs. Alternatively, lessen the value to bring more highs in (.15uf, .1 uf)
B	Raise value for more bass	.1, .22, .44, .1 uf – works in conjunction with # 6 resistor
D,E	Clipping diodes	Experiment—it will shape the tone and overdrive considerably!
A	Gain resistor	Lower value for more gain, and clarity. 2.2k, 1k, works in conjunction with #4.
808-1	100 ohm	These two changes alone is the legendary "ts-808" mod.
808-2	10k ohm	

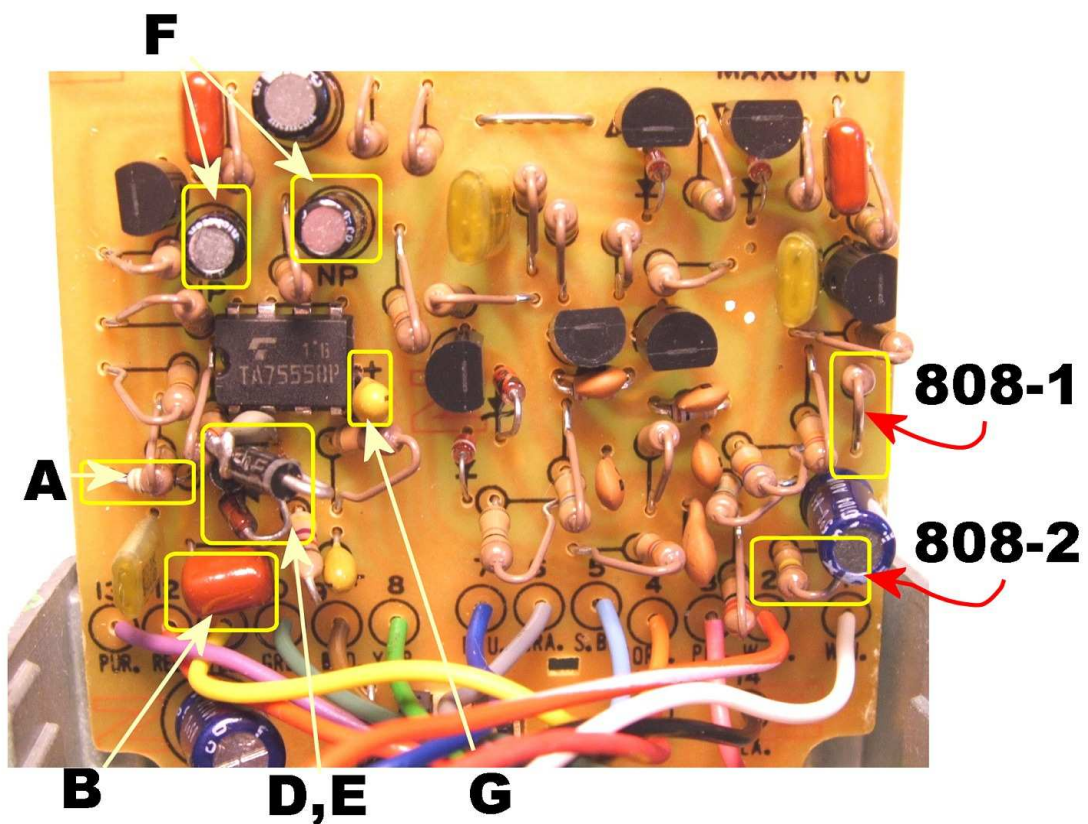

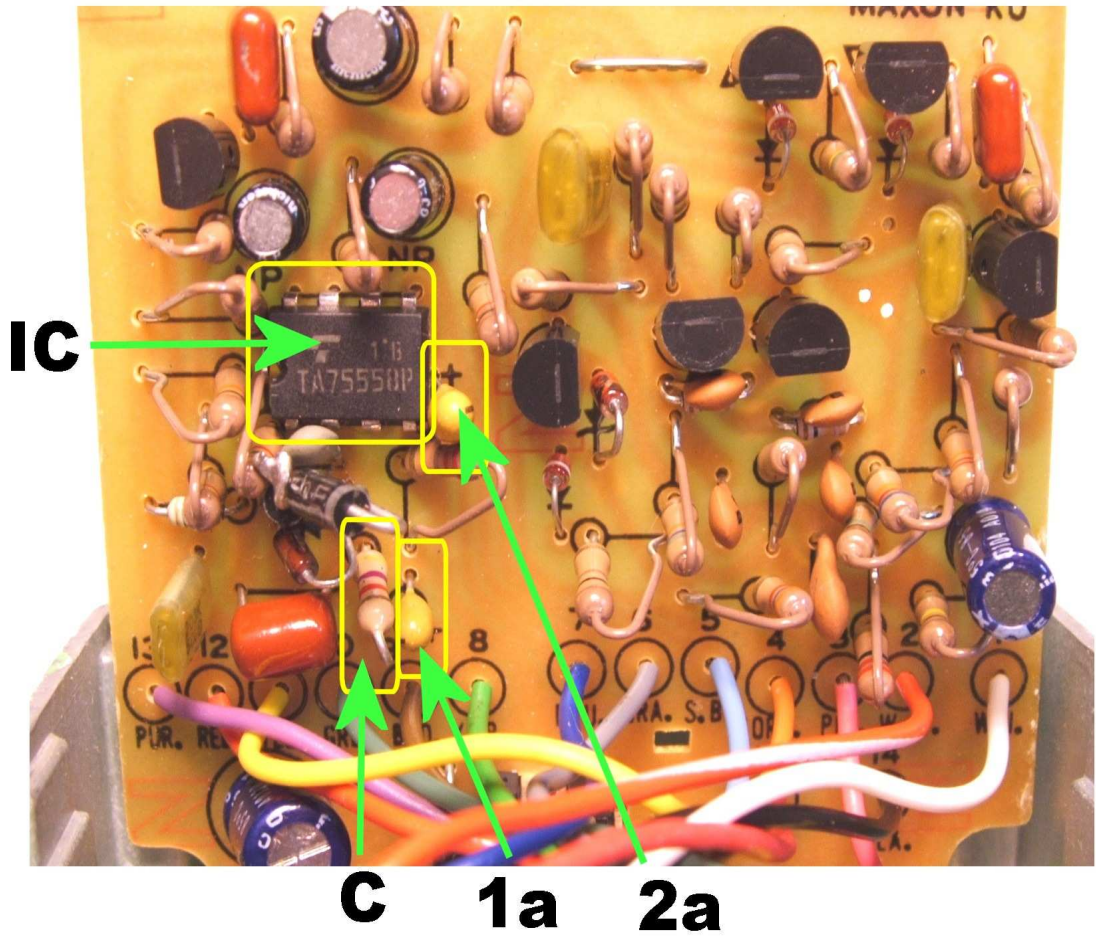

TS-9 Tube Screamer

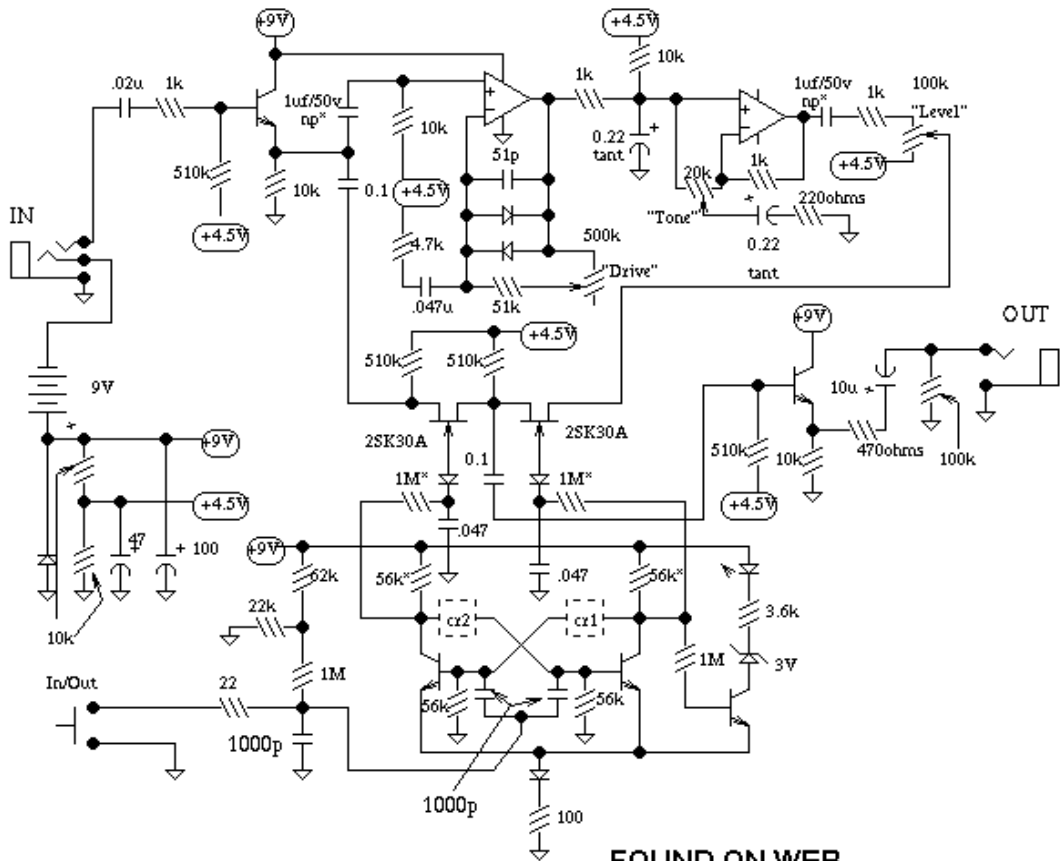

FOUND ON WEB

Opamps are in a dual 8 pin dip, 4558. All transistors 2SC1815. All diodes silicon signal diodes, 1n914 or similar. np* = nonpolarized resistors denoted by * marked as 1M on original might be 22k and those marked as 56K might be 10k. crf1 and crf2 are a special cap and resistor in parallel, the cap is 51p the resistor is 56k.

Schematic with switching circuit

TS-9DX Turbo Tubescreamer

BSM (Brent Mason) MOD

A	1K RESISTOR	
B	.47uf or .22uf + .22uf in parallel (results in the same thing)CAP	
D	1N4001	
E	1n4001 + 1n4001 SERIES	
F (2 OF THEM)	1 UF FILM CAPS	
G	.15 uf or .047 + .1 uf in parallel (results in the same thing)	

Ibanez TS-9 316 MOD

Location	Mod value
A	1K RESISTOR
B	.22UF
D	LED
E	LED + 4148 in SERIES
F (2 OF THEM)	1 UF FILM CAPS

Ibanez TS-9 standard Mod

Location	Stock value	Mod value	What it affects
B	.047 uf	.1 uf	Adds bottom end. For more, go .22 uf
D		LED & germanium 1n34a in series	Adds fullness, depth, and dynamics
E		1N4001	
A	4.7k	3.3k	The lower the value, the more distortion available, as well as the pedal becomes a hair brighter.
E		Burr Brown OPA2604 IC CHIP, rc4558 ic chips, jrc4558 chips	Not always needed, will not make a big difference...but there is a lot of hype around this change!
F	1uf elec	1uf film caps	Helps low end to not distort


Ibanez TS-9 Extra's

Location	Mod Value	What it affects
2A	Raise value - .44uf, .1 uf	Raising value will decrease the highs. Alternatively, lessen the value to bring more highs in (.15uf, .1 uf)
B	Raise value for more bass	.1, .22, .44, .1 uf - works in conjunction with # 6 resistor
D,E	Clipping diodes	Experiment—it will shape the tone and overdrive considerably!
A	Gain resistor	Lower value for more gain, and clarity. 2.2k, 1k, works in conjunction with #4.
808-1	100 ohm	These two changes alone is the legendary "ts-808" mod.
808-2	10k ohm	

*NOTE: The TS9DX has 4 separate modes, so it is possible to make multiple modifications simply by paying close attention to which part shown is affecting which


LOCATION D & E

**Diodes for
+ mode**

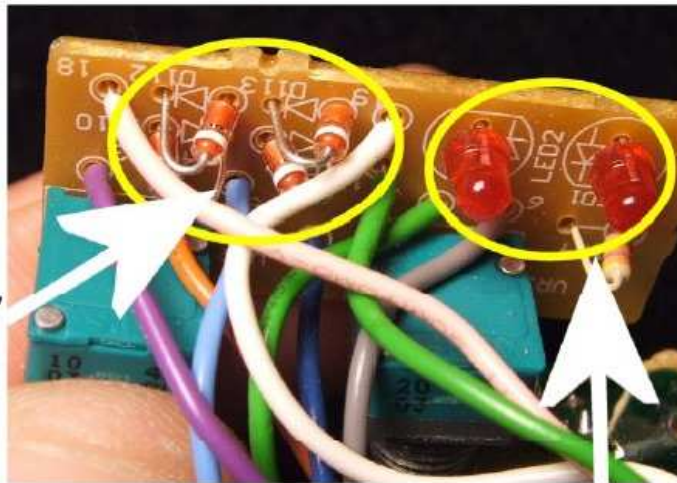


Diodes for Hot Mode

"B" for standard mode

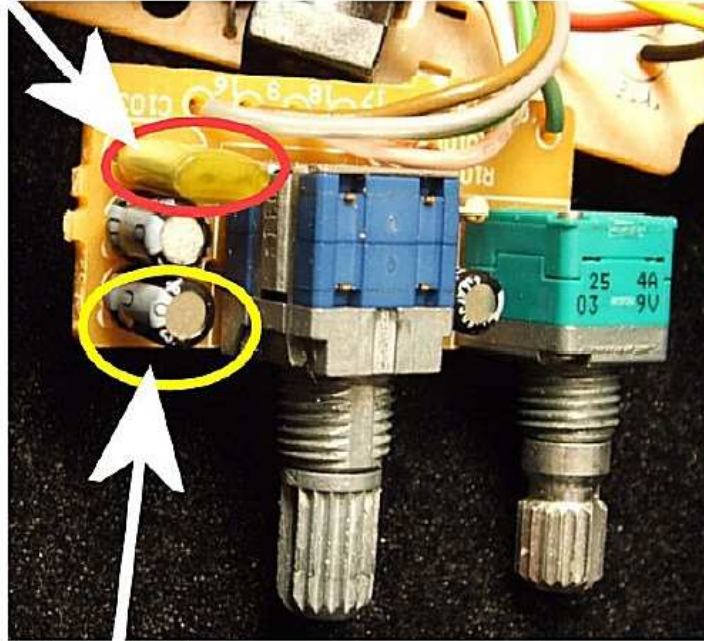

"B" for Hot and + mode

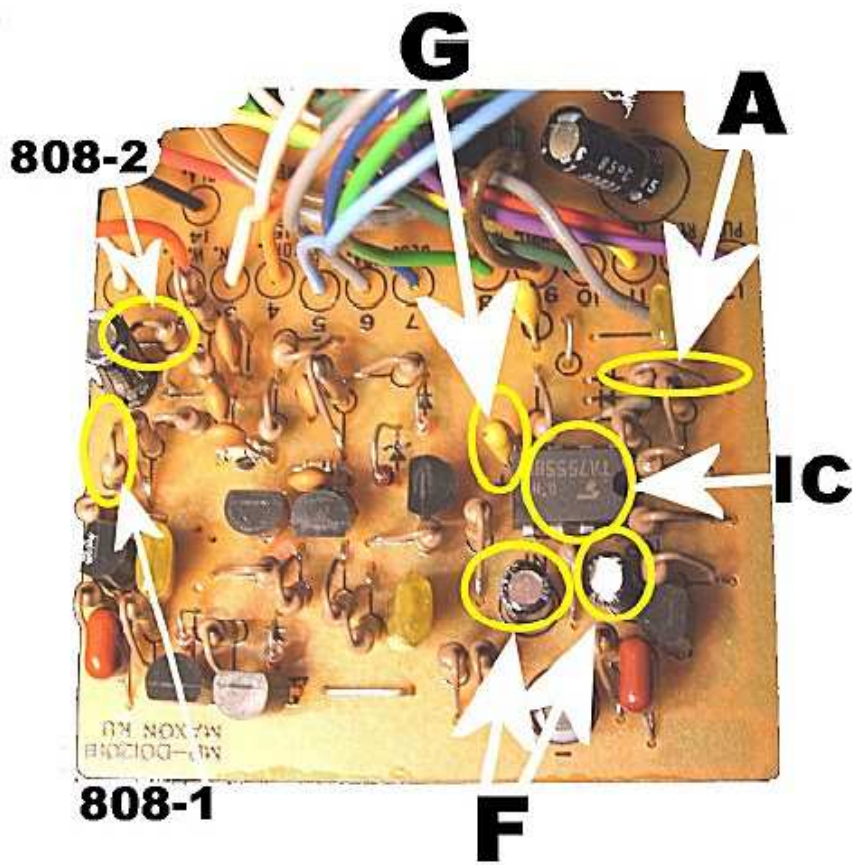

Ibanez SM-9 Mod

Location	Stock value	Mod value
D1		Led + 1n4148
D2		Led
D5		led
C1	.047	.1 uf
C12	.001 uf	Remove, don't jumper


*no pictures available for this one.

Ibanez Smashbox SM-7 Distortion

Location	Mod value	part
D3	1n4001	
D6	1n4001	
D4,	1n4001 x 2 in series	
D5	1n4001 x 2 in series	
C33	.01 uf	Adds distortion
C26	Remove (no jumper)	Adds body to eq
R52	Remove (no jumper)	Adds body to eq


See pic next page

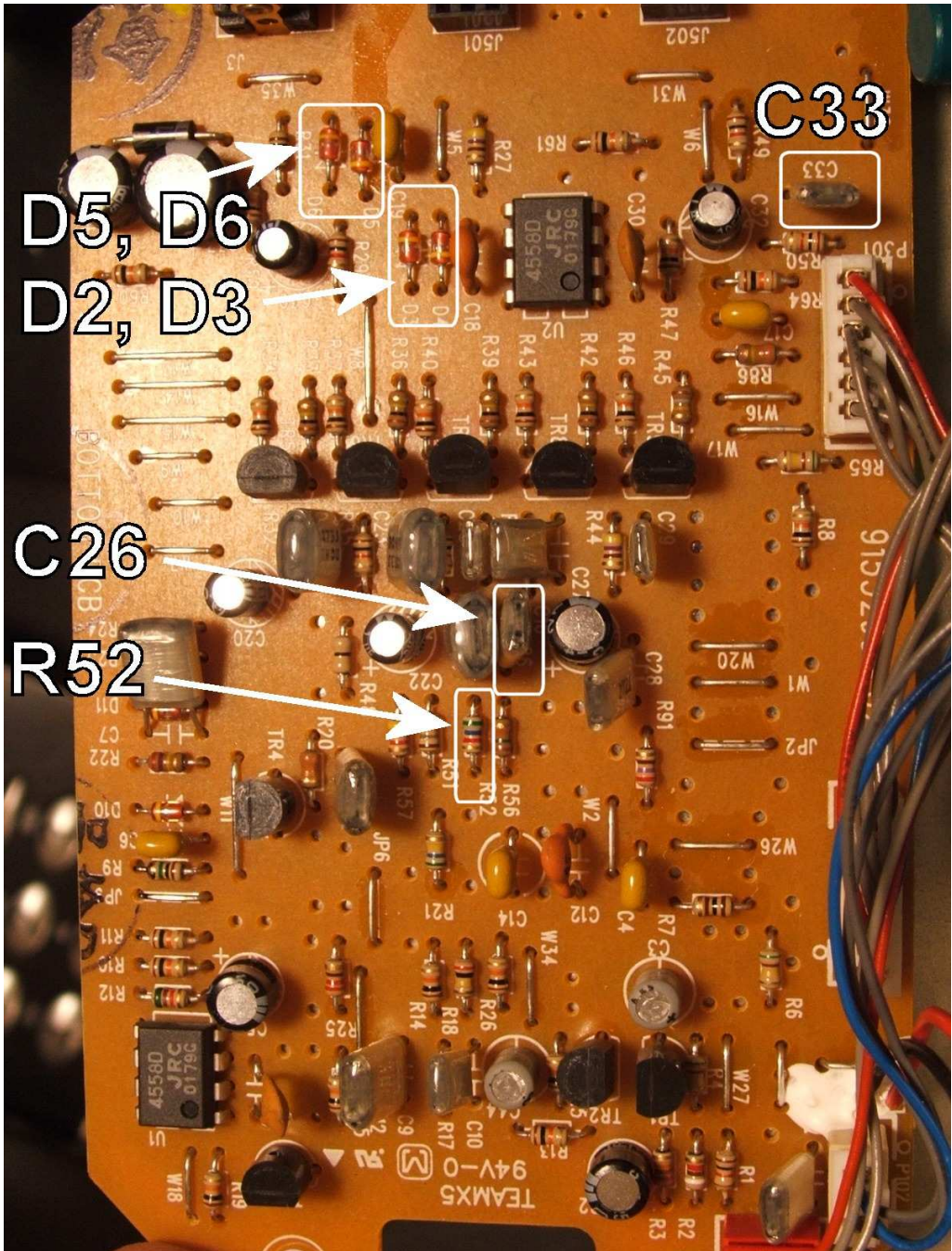See Schematic at <http://www.indyguitarist.com/schematics>



Jacques Tube Blower

Location	Stock value	Mod value	What it effects
R19	4.7k	47k	Richer, smoother mids, better bass response (not muddy bass)
D2	1n914	1n4148 + 1n4148 in series	Thicker clipping, better dynamics and response

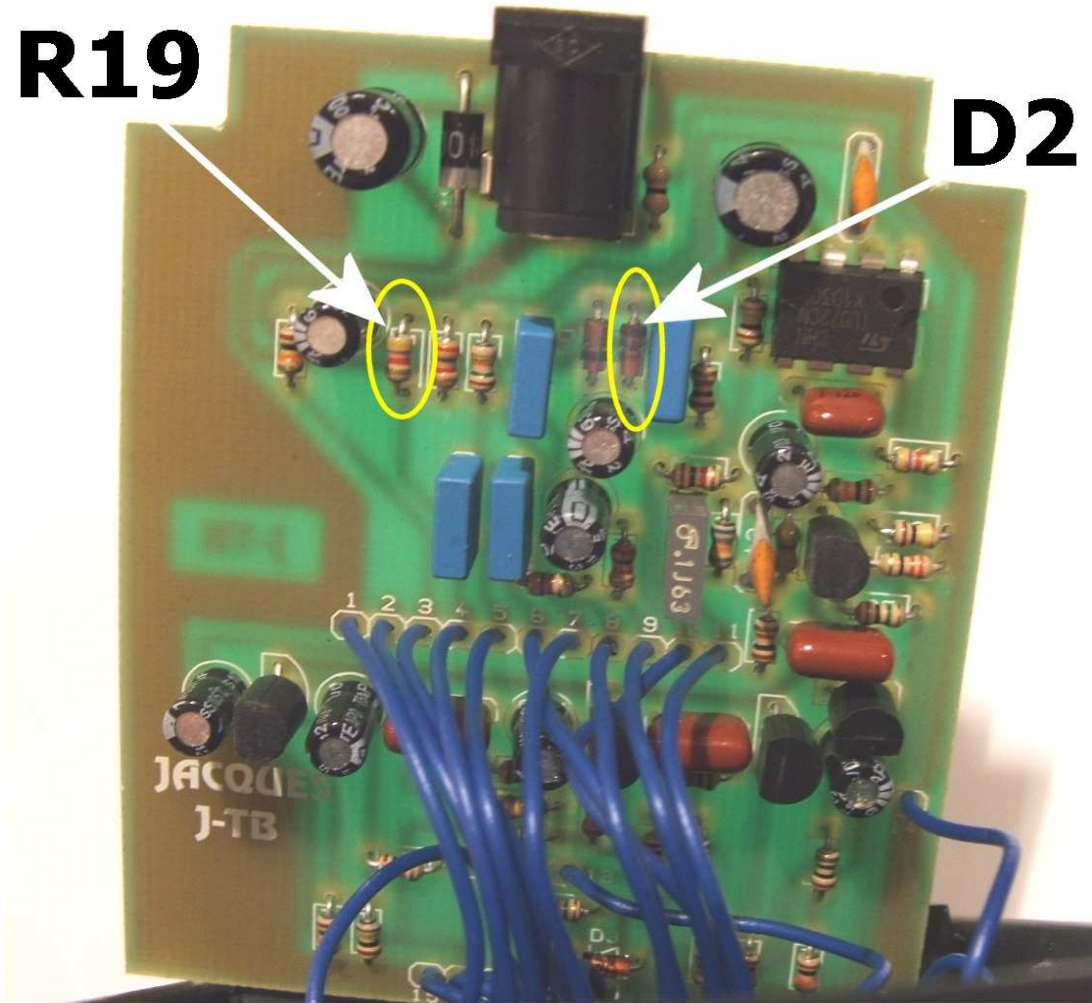


Johnson "Distortion plus EQ"

This pedal is an exact clone of the Boss MT-2 Metalzone, the circuitboards are even the exact same. For this reason, the same mods apply to it...see Boss MT-2 Metalzone mods.



Marshall bb-2 bluesbreaker mod

Location	Stock value	Mod value	What it effects
C12	.0047	.1uf or larger.	Bottom end, adds fullness, the larger the cap, the more lows are produced.
R20	29k	100 ohm	Adds volume, fullness
Led1		1n4001	Makes clipping fuller, thicker, more responsive
Led2		1n4001 + led connected in parallel	Makes clipping fuller, thicker, more responsive
For more bottom end:			
R29	5.6k	100 ohm	Adds more bottom end if you desire
Led1	led	1n4148	


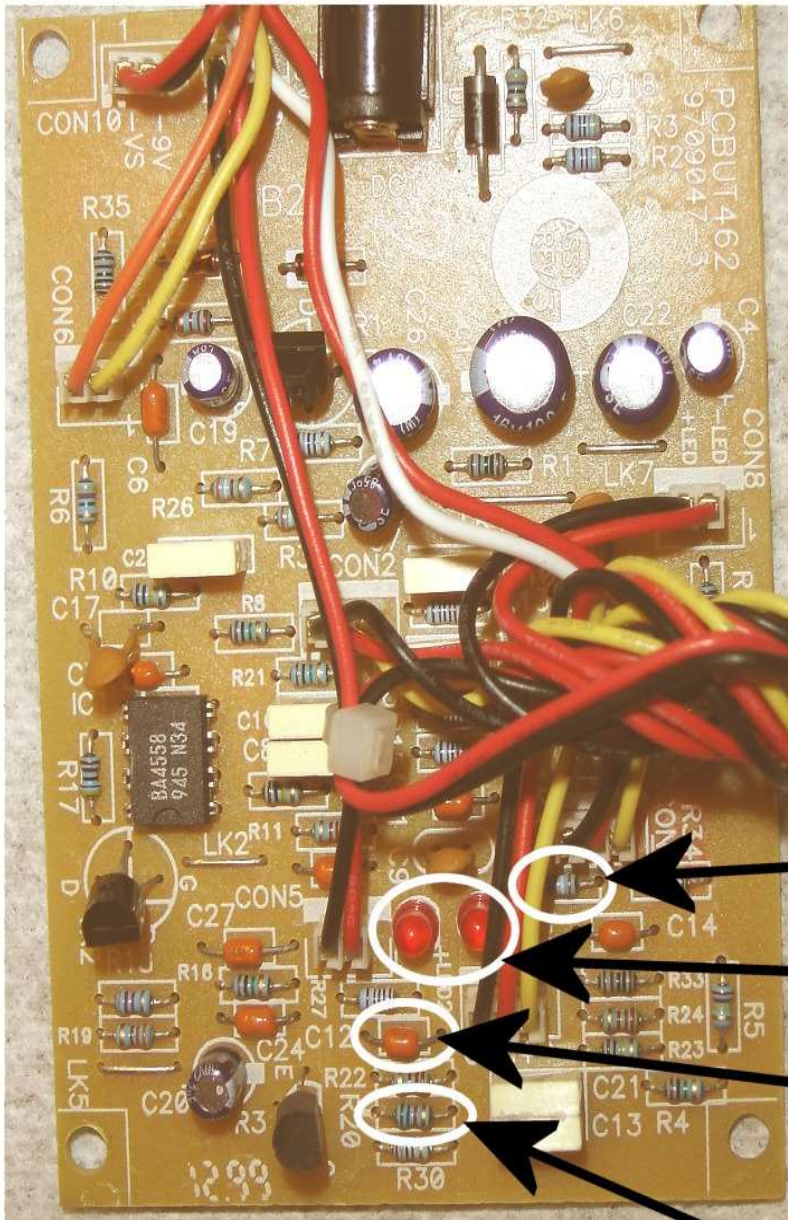


R29

LED 1,2

C12


R20

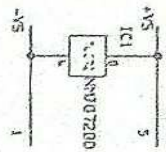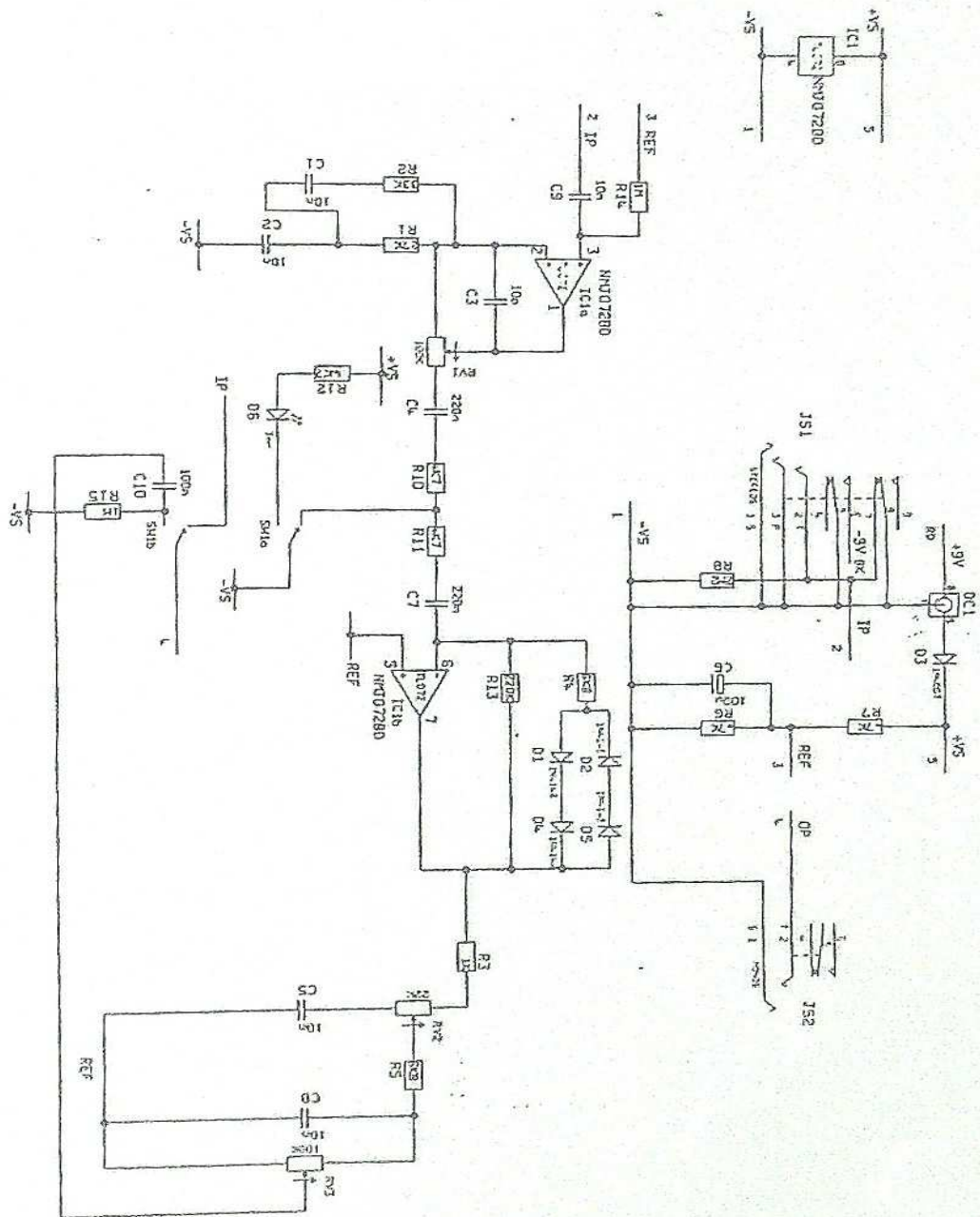


Marshall Guv'nor Plus GV-2

Location	Stock value	Mod value	What it effects
D2	LED	1n4001	Makes clipping more dynamic and responsive, much more pick sensitive.
D4	LED	1n4001 + 1n4001 in series	
C1	.0068uF	.0047uF or .01uF	Change value in small increments, small increments changes mid "q", larger incremental changes change bass
R2	15k	Optional (10k, 6.8k, 4.7k, 2.2k, 1k)	Lower value to add high mids, will change the eq range of the pedal
C8	.1uF	optional	Add value gives more bass. 1uf will make a great bass Overdrive, .068uf will make the pedal a bit cleaner.

C1

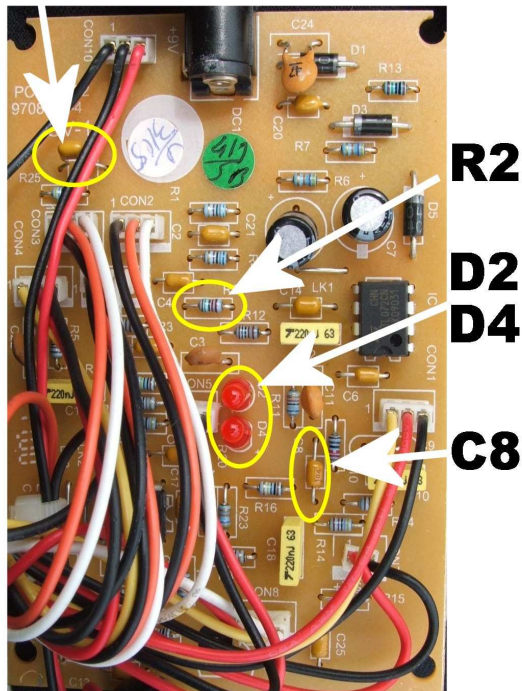

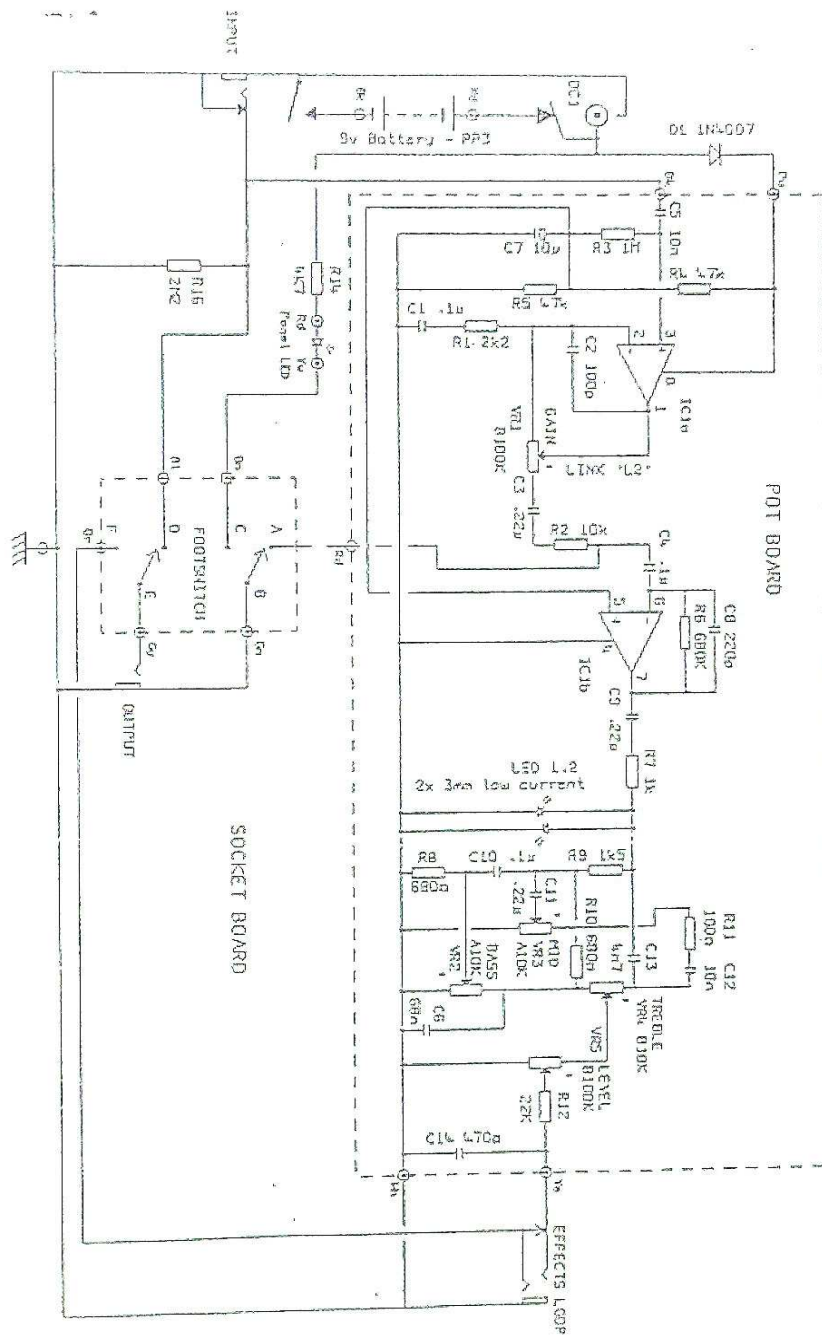Special Thanks to Johan for the Marshall Schematics




Marshall Shredmaster

(original blackbox version)

Location	Stock value	Mod value	What it effects
R9	10k	1k	Increases distortion/treble if desirable
D2	4148	Germanium->1n4001 (in series)	Makes distortion much fuller.
D3	4148	1n4001->4148->1n4001 (in series)	
C5	.001UF	500-800 PF, OR FOR MORE MIDS TRY .0047UF	



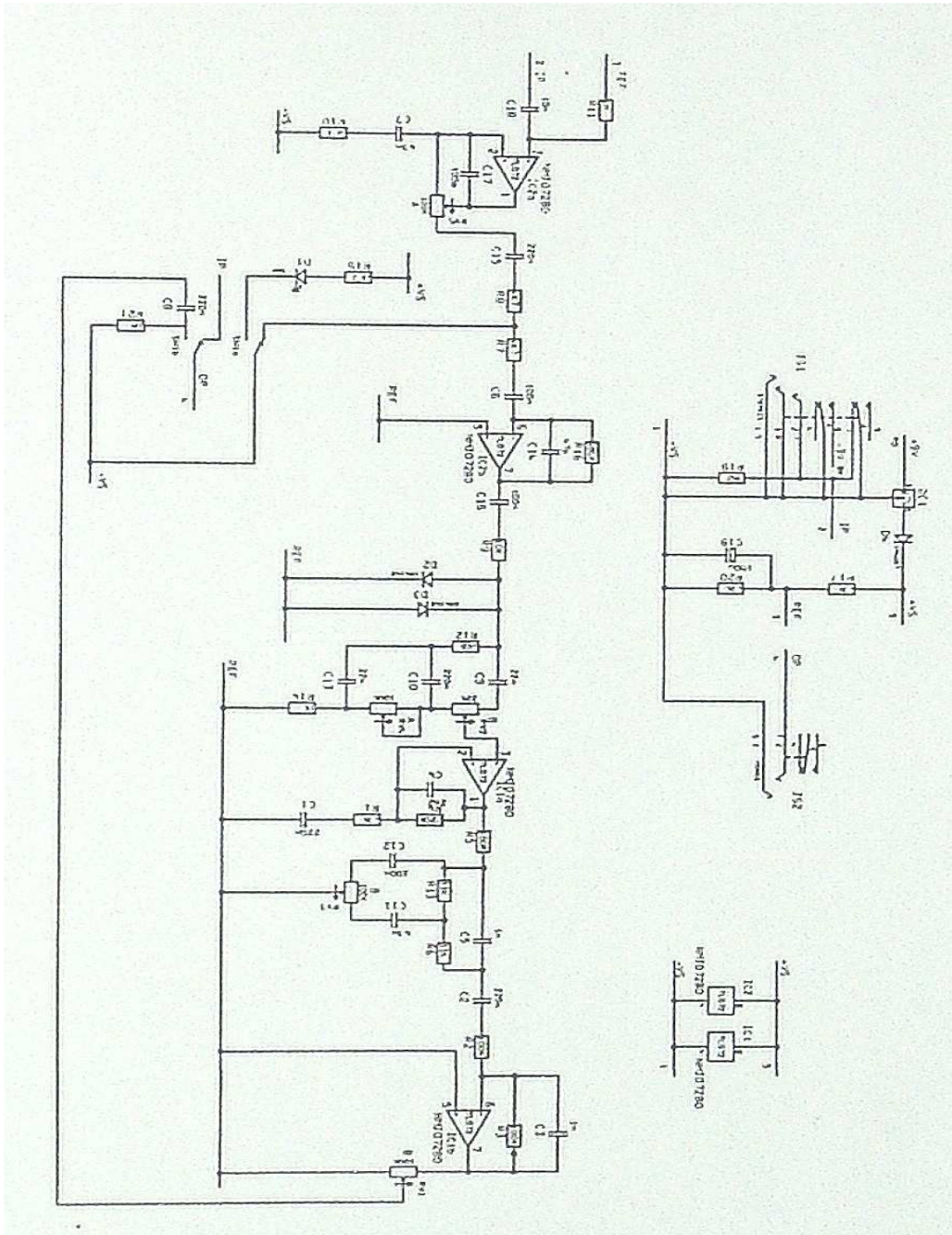

Maxon OD808 TubeScreamer

BSM (Brent Mason) MOD

Location	Mod value
R4	1K RESISTOR
C3	.22UF x 2 in parallel (or .47uf) CAP
D1	1N4001
D2	1n4001 + 1n4001 SERIES
C5	.15 uf or .047 + .1 uf in parallel (results in the same thing)

Maxon OD808 316 MOD

Location	Mod value
R4	1K RESISTOR
C3	.22UF
D1	LED
D2	LED + 4148 in SERIES


Maxon OD808 standard Mod

Location	Stock value	Mod value	What it affects
R4	4.7k	3.3k	The lower the value, the more distortion available.
C3	.047 uf	.1 uf	Adds bottom end. For more, go .22 uf
D1	1N914	LED & germanium 1n34a in series	Adds fullness, depth, and dynamics
D2	1N914	1N4001	
C5	.22uf tantalum	.22uf metal film	

Circuitwise, the od808 is almost an exact tubescreamer clone.


Maxon OD808 Extra's


Location	Mod Value	What it affects
C5	Raise value - .44uf, .1 uf	Raising value will decrease the highs. Alternatively, lessen the value to bring more highs in (.15uf, .1 uf)
C3	Raise value for more bass	.1, .22, .44, .1 uf – works in conjunction with # 6 resistor
D1, D2	Clipping diodes	Experiment—it will shape the tone and overdrive considerably!
R4	Gain resistor	Lower value for more gain, and clarity. 2.2k, 1k, works in conjunction with #4.

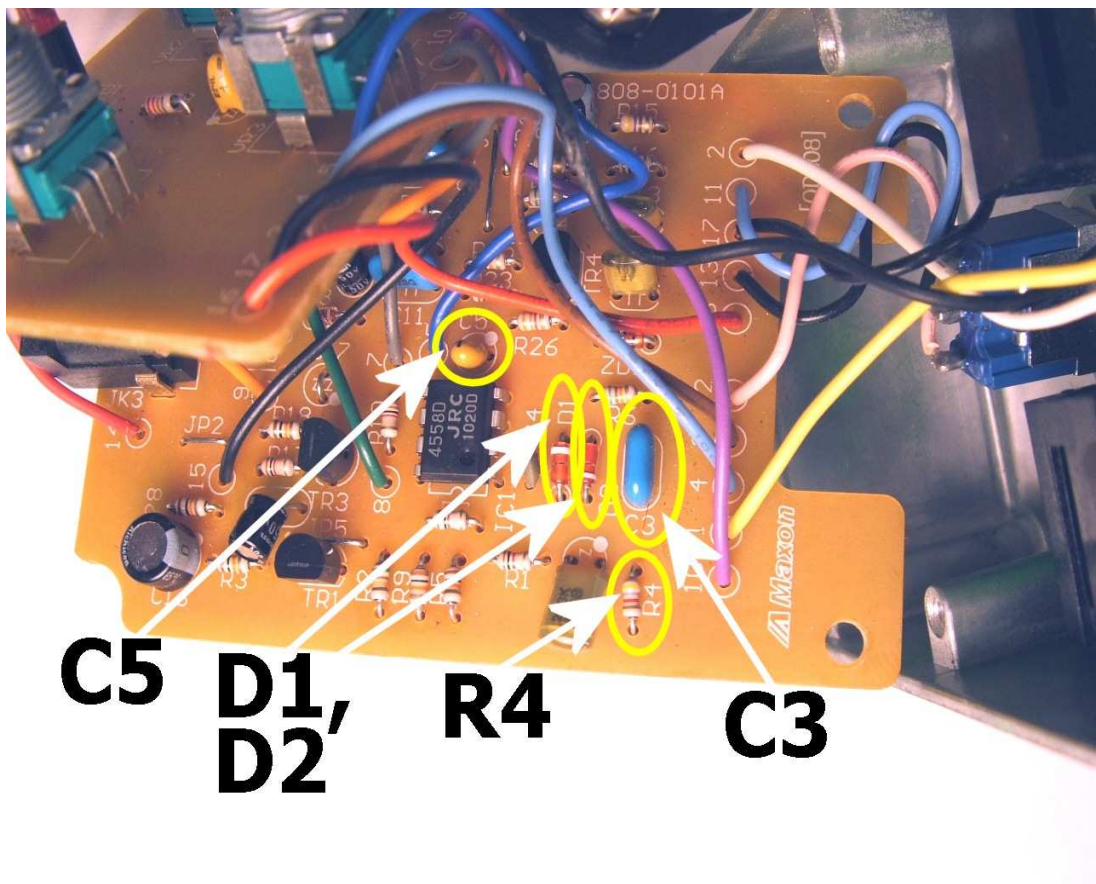

Morley Classic Wah


Location	Mod value
See changes	As shown in picture
Other tips:	<p>Moving the led around will change the tone quite a bit. Feel free to experiment.</p> <p>If you are getting too much range of wah, you can add a 1k resistor in parallel with LDR3 (across from the led).</p>

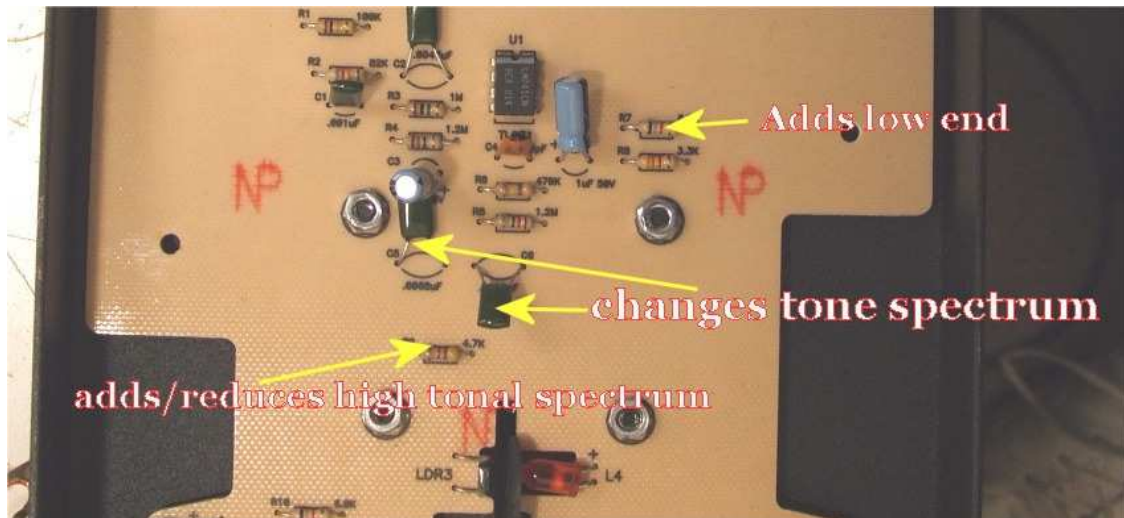

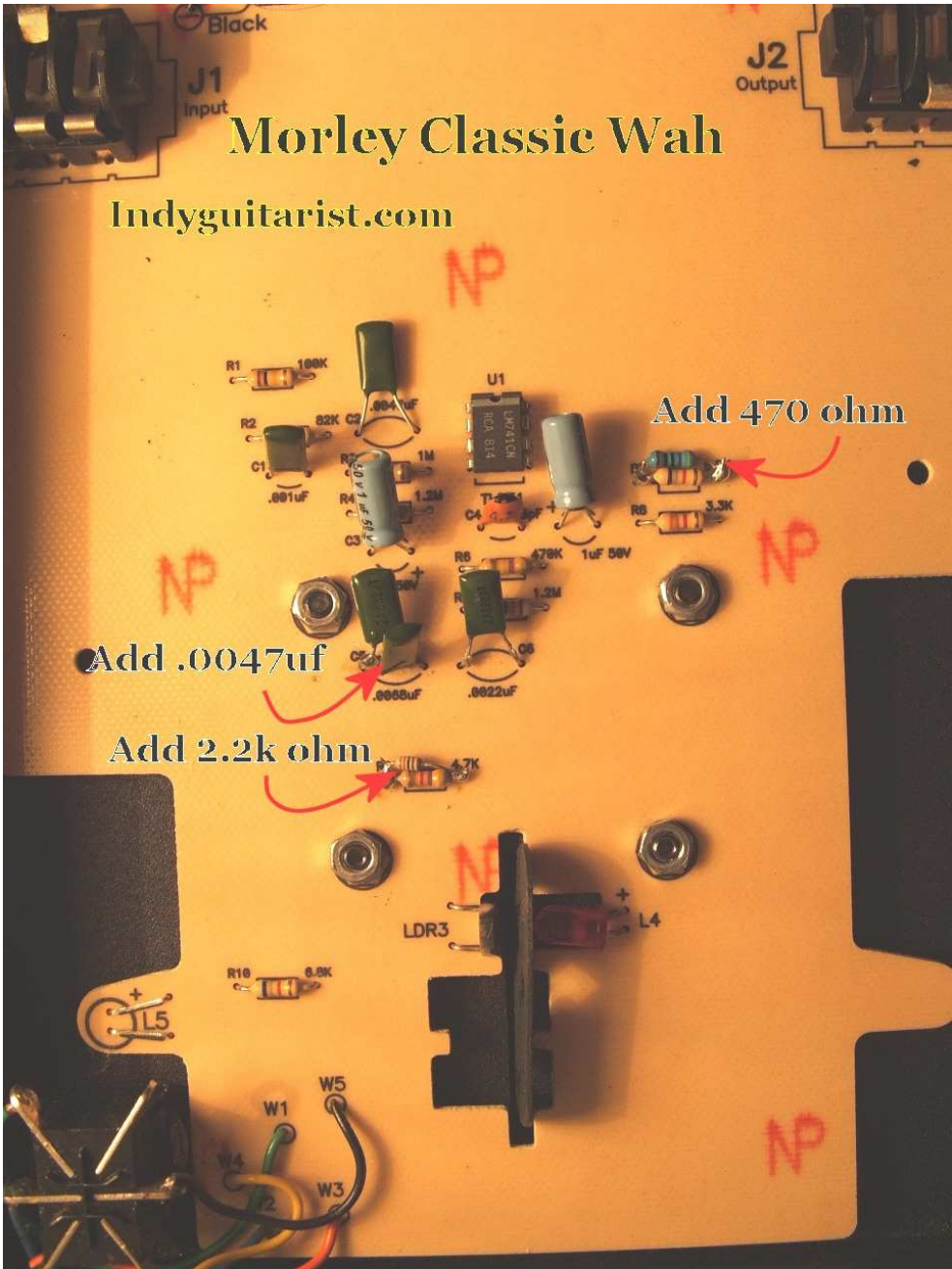

Morley PWOV Power Wah Volume


Location	Mod value	
R7	68K	MORE VOCAL EFFECT
R24	1K	MORE VOCAL EFFECT
C4	1UF	OVERALL FULLER SOUNDING
Other tips:	<p>Moving the led around will change the tone quite a bit. Feel free to experiment.</p> <p>If you are getting too much range of wah, you can add a 1k resistor in parallel with LDR3 (across from the led).</p>	

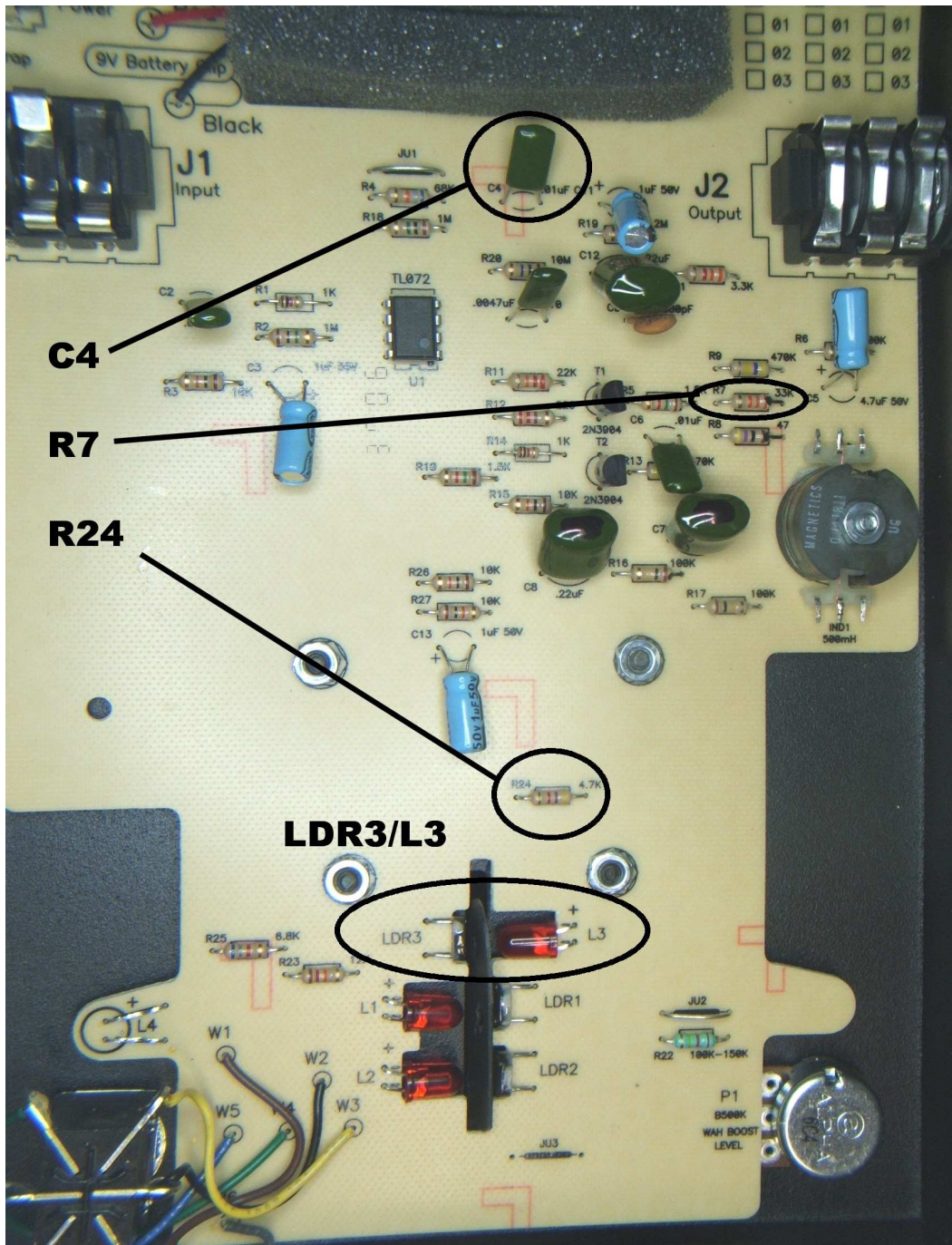


MXR Distortion Plus (newer versions)

Location	Mod value	What it effects
A	.1uf or for more bass try these values: .15uf, .22uf, .47uf. For bass guitar use 1uf	Adds bass
B (DIODE 1)	1n4148	Will make the distortion less fuzzy, and more thick and dynamic.
B (DIODE 2)	1n4148 + 1n4148 connected in series	
C	1uf film cap	Better output tone
H	Replace with 1m pot	2 nd gain control
D,G	Replace with desired value, it is a low pass filter. See http://www.indyguitarist.com/filter for values depending on what frequency you want to remove...for less highs, replace "G" with a larger cap.	

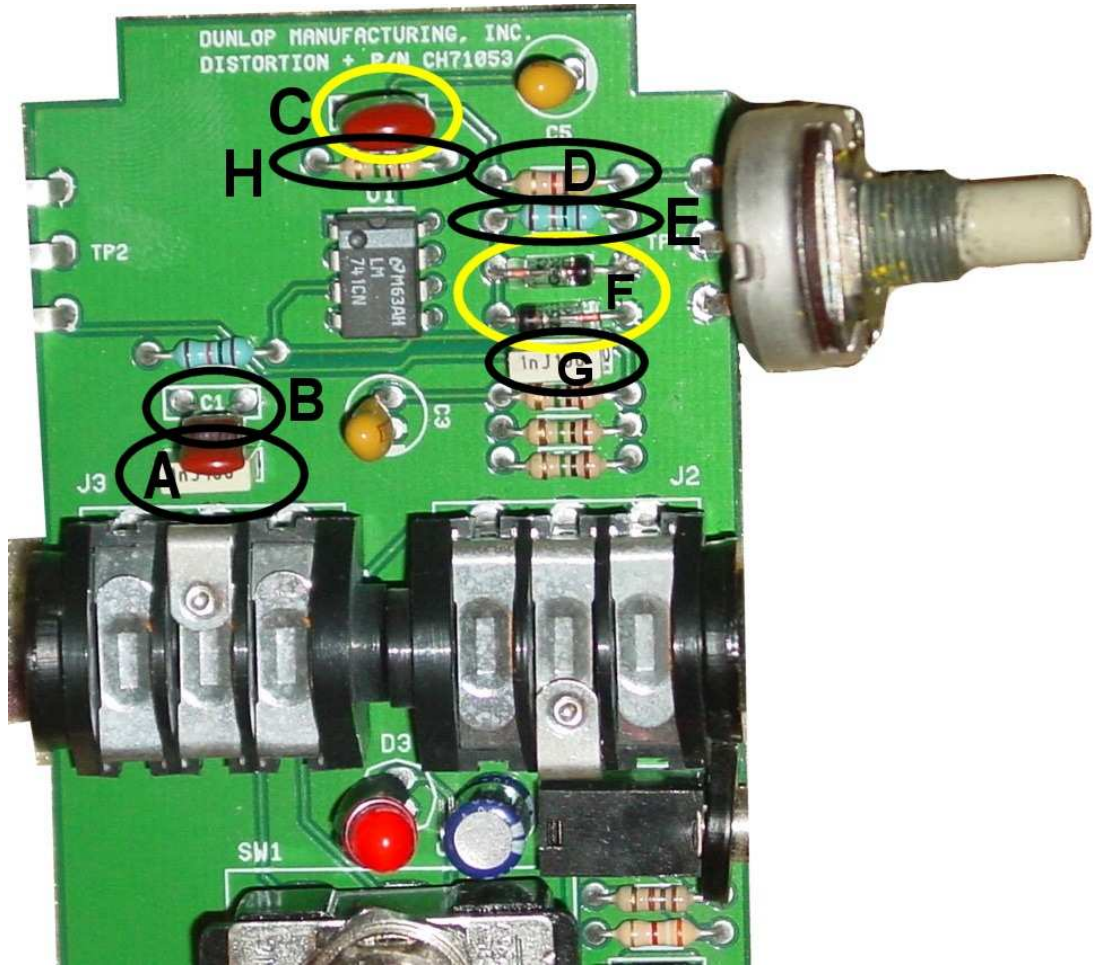***NOTE: It doesn't matter which diode is "diode 1" or "diode 2".**




MXR Distortion +

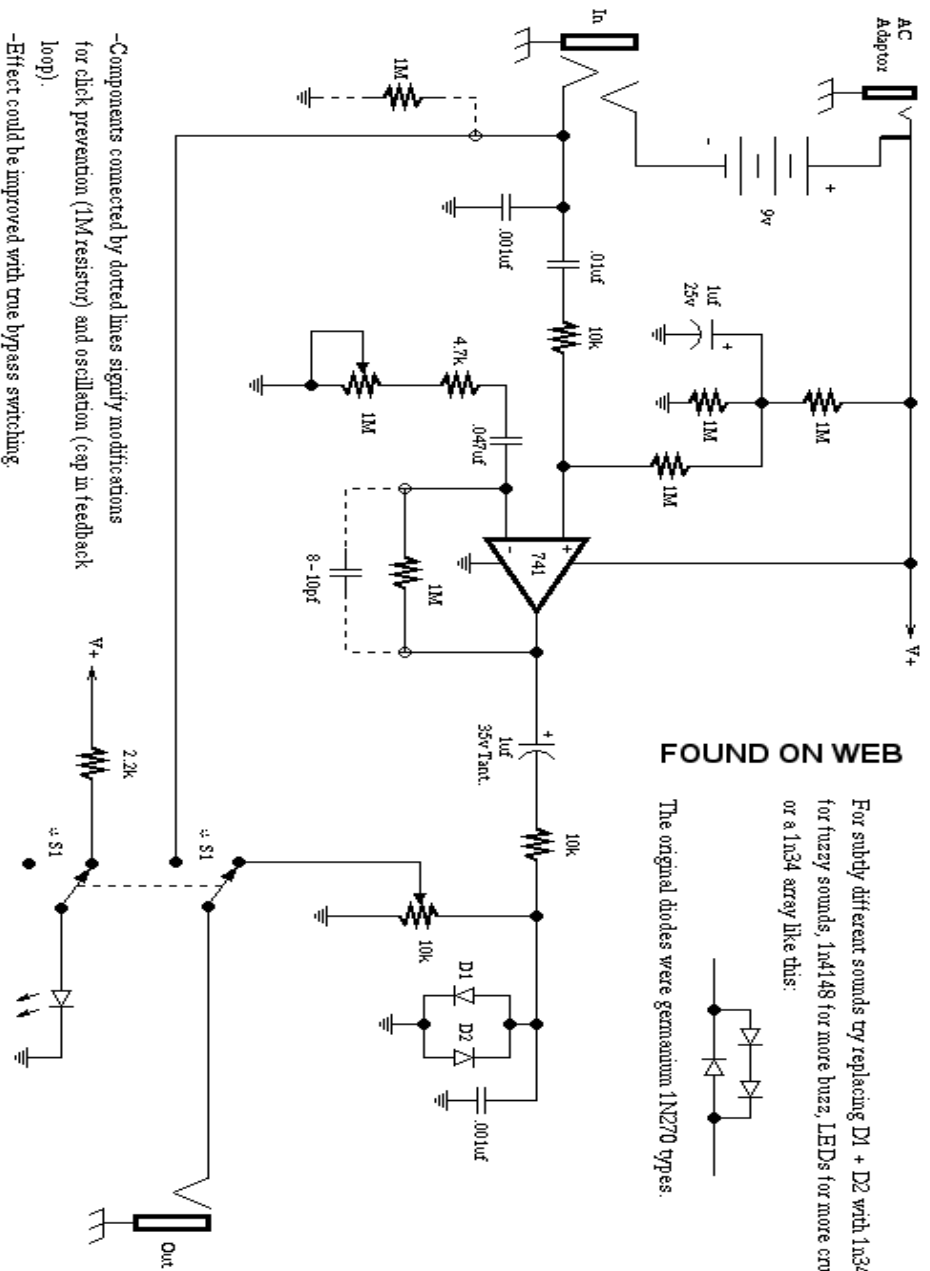

FOUND ON WEB

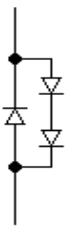For subtle different sounds try replacing D1 + D2 with 1n34's for fuzzy sounds, 1n4148 for more buzz, LEDs for more crunch, or a 1n34 array like this:





The original diodes were germanium 1N270 types.

- Components connected by dotted lines signify modifications for click prevention (1M resistor) and oscillation (cap in feedback loop).
- Effect could be improved with true bypass switching.


MXR Dynacomp – Ross Mod

Location	Mod value	What it effects
R7	Install 2 -- 470k resistors as shown	Connect exactly as shown, to a 1uf cap, that connects to R10
R2	Install 2 -- 220k resistors as shown	Connect exactly as shown, to a 1uf cap, that connects to R10

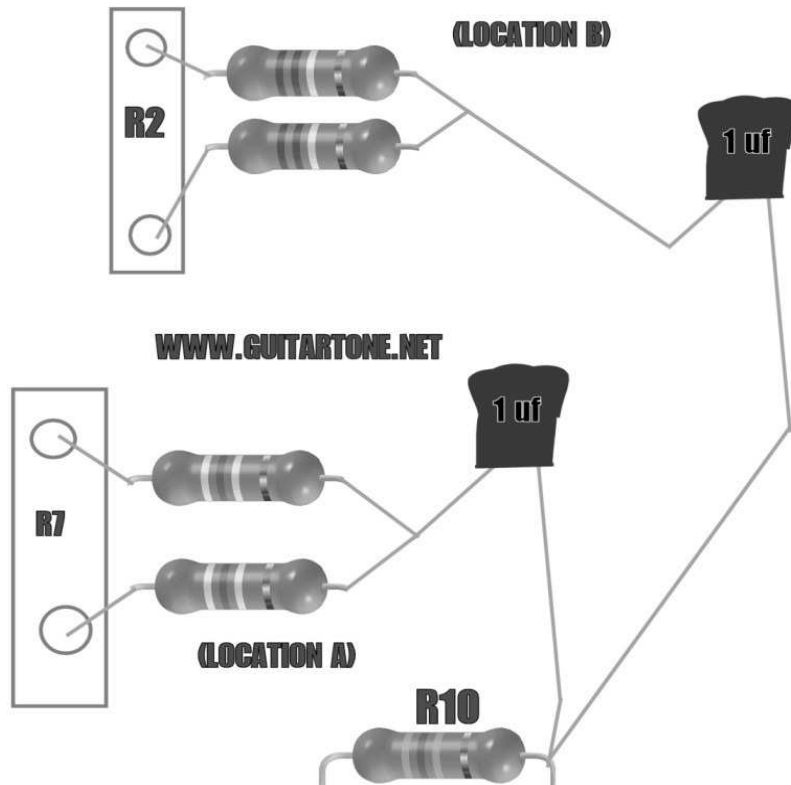

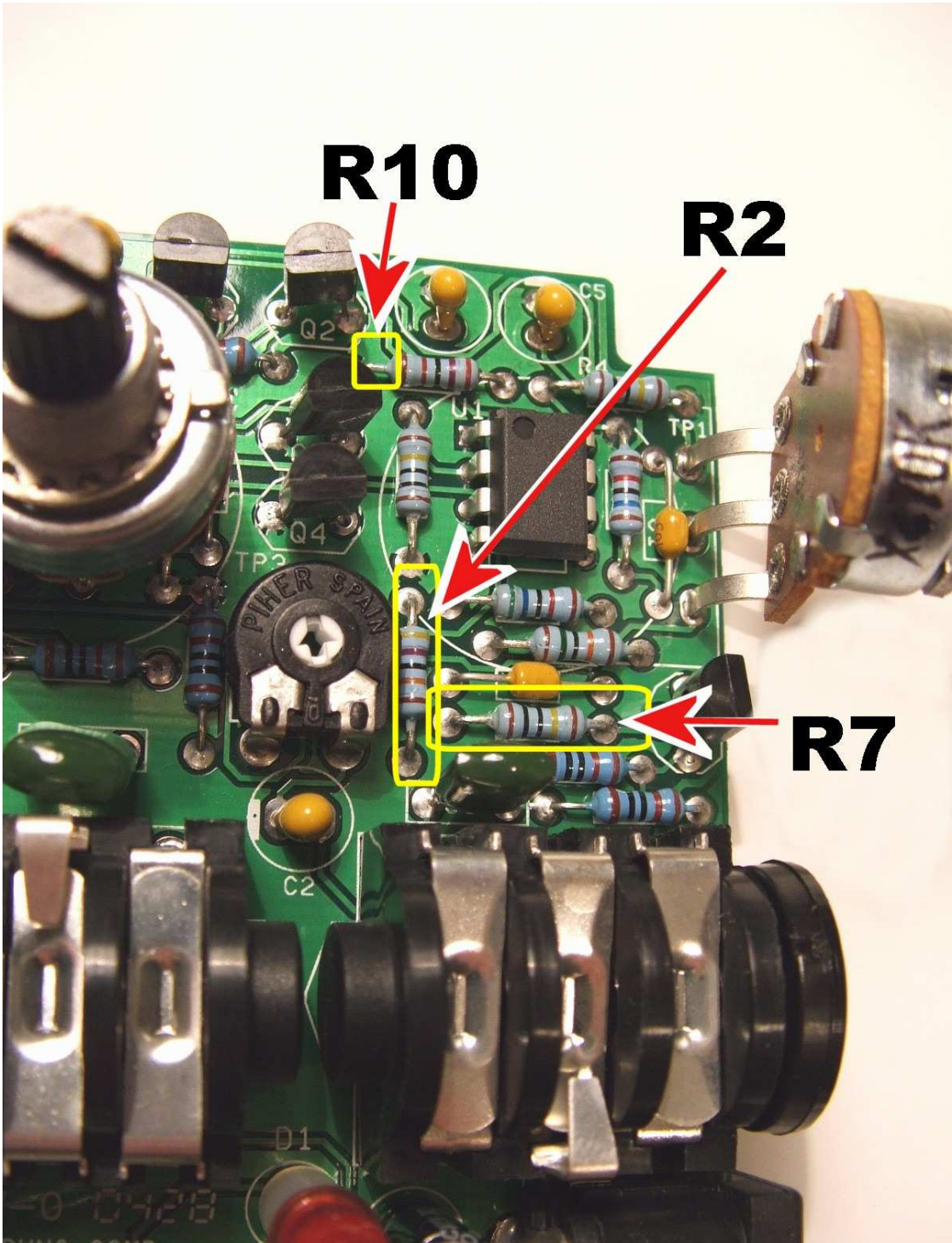


MXR PHASE 90 MODS

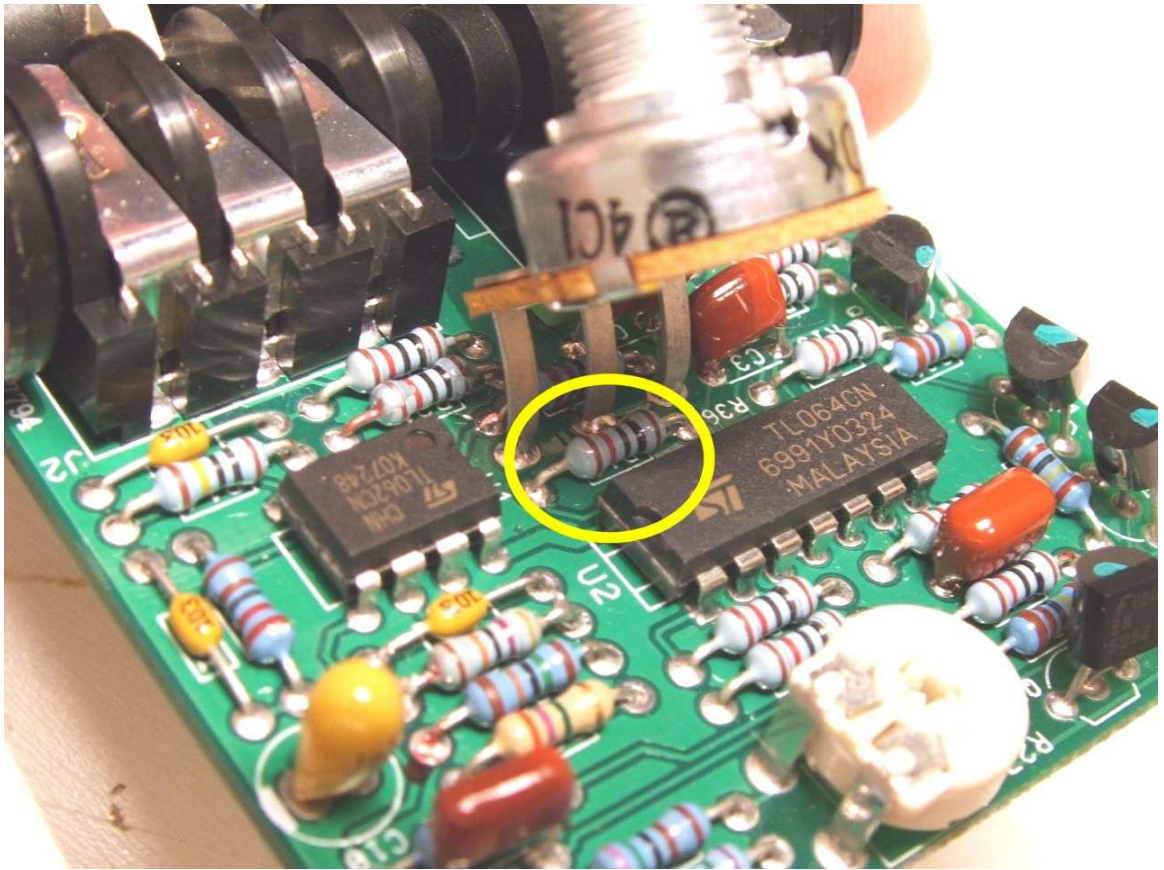

For faster speeds, replace the resistor shown above with a 470 ohm resistor

WAVE FORM MOD

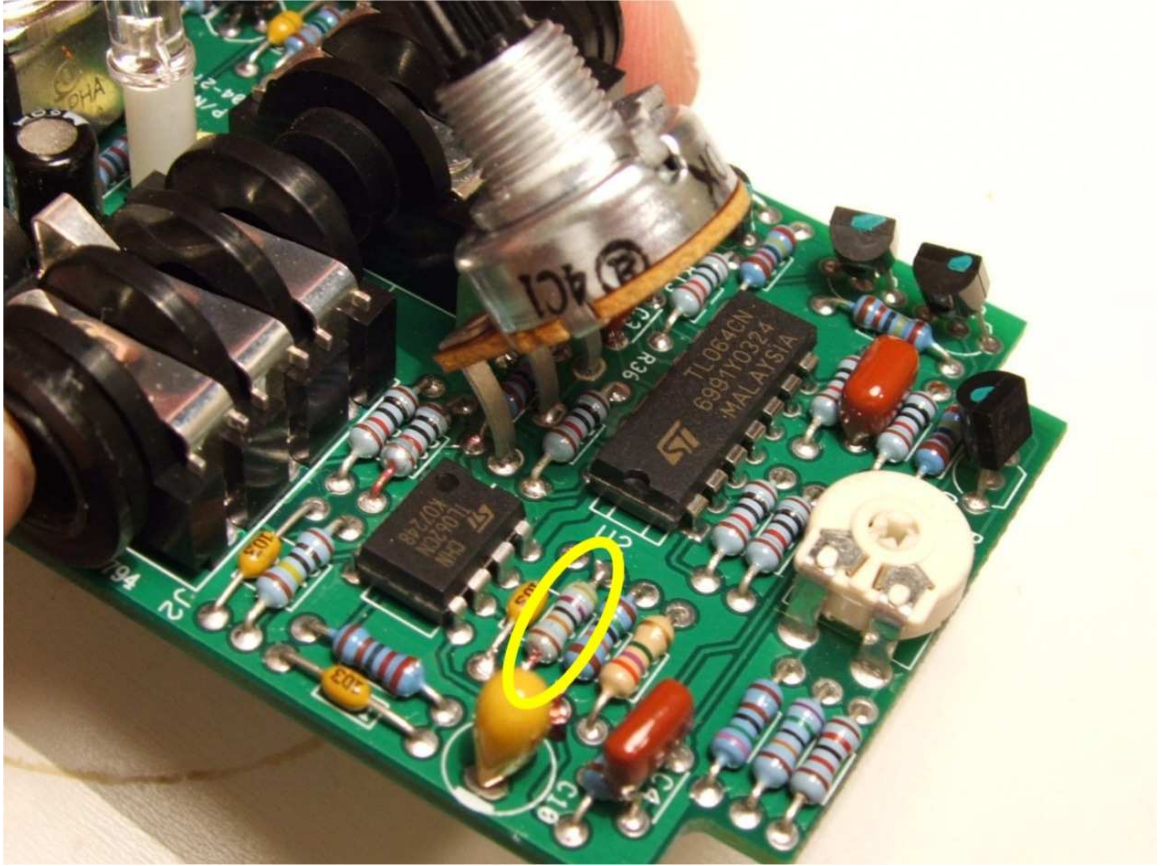


For changes in waveform of phasing, replace this resistor with a 10k resistor

UNIVIBE MOD

Replace Caps as shown

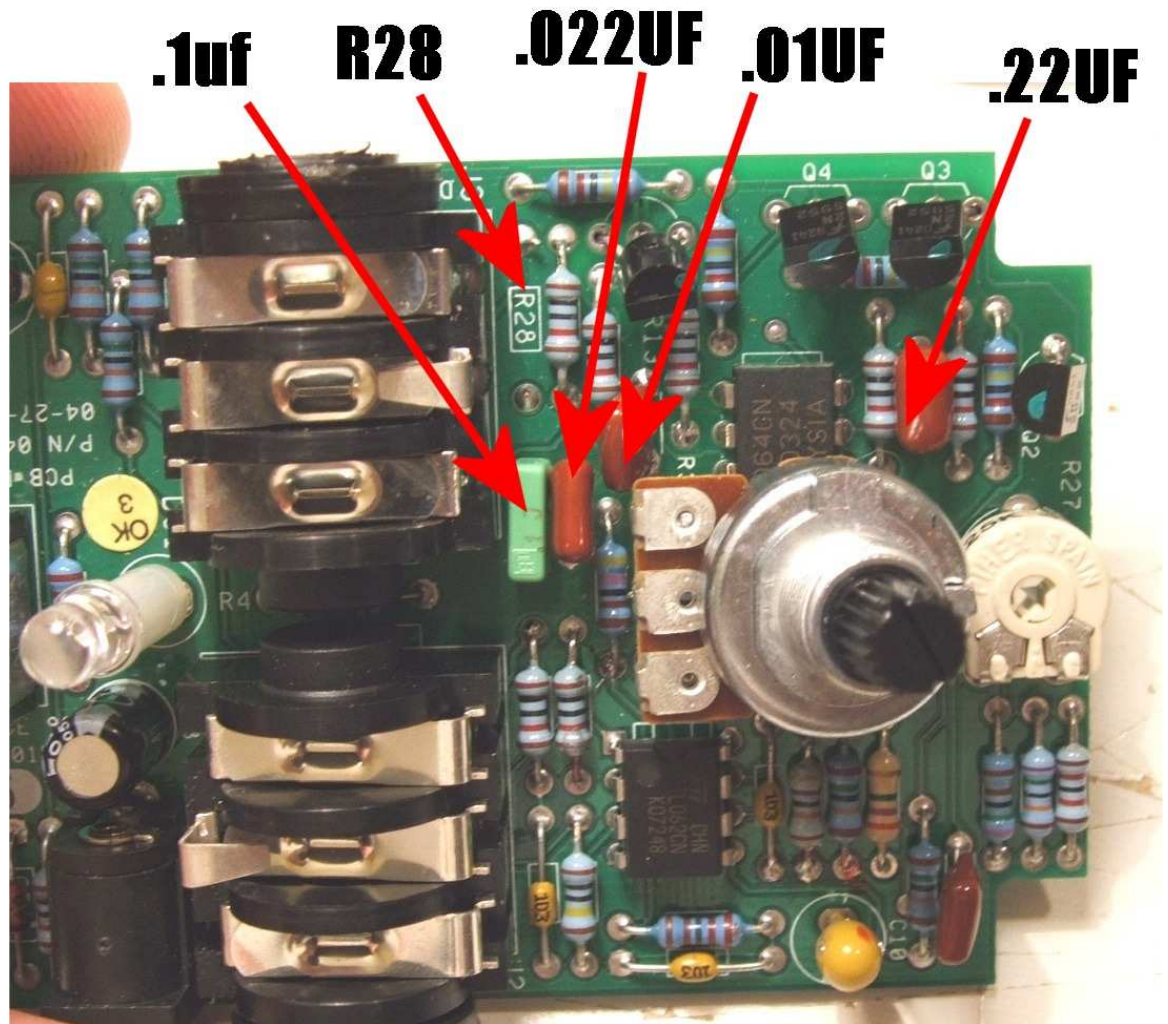
Remove R28 totally. (don't replace with anything)



"R28" SCRIPT MOD


- remove R28 totally, do not replace with anything.
- remove C11 totally, do not replace with anything.

"R28" SCRIPT MOD

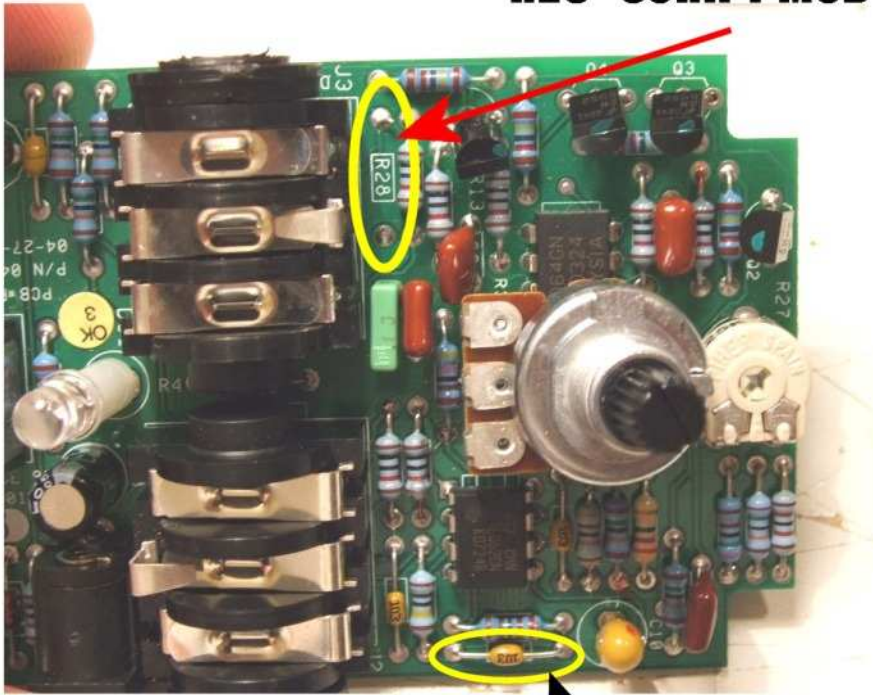

remove C11 totally (don't jumper)

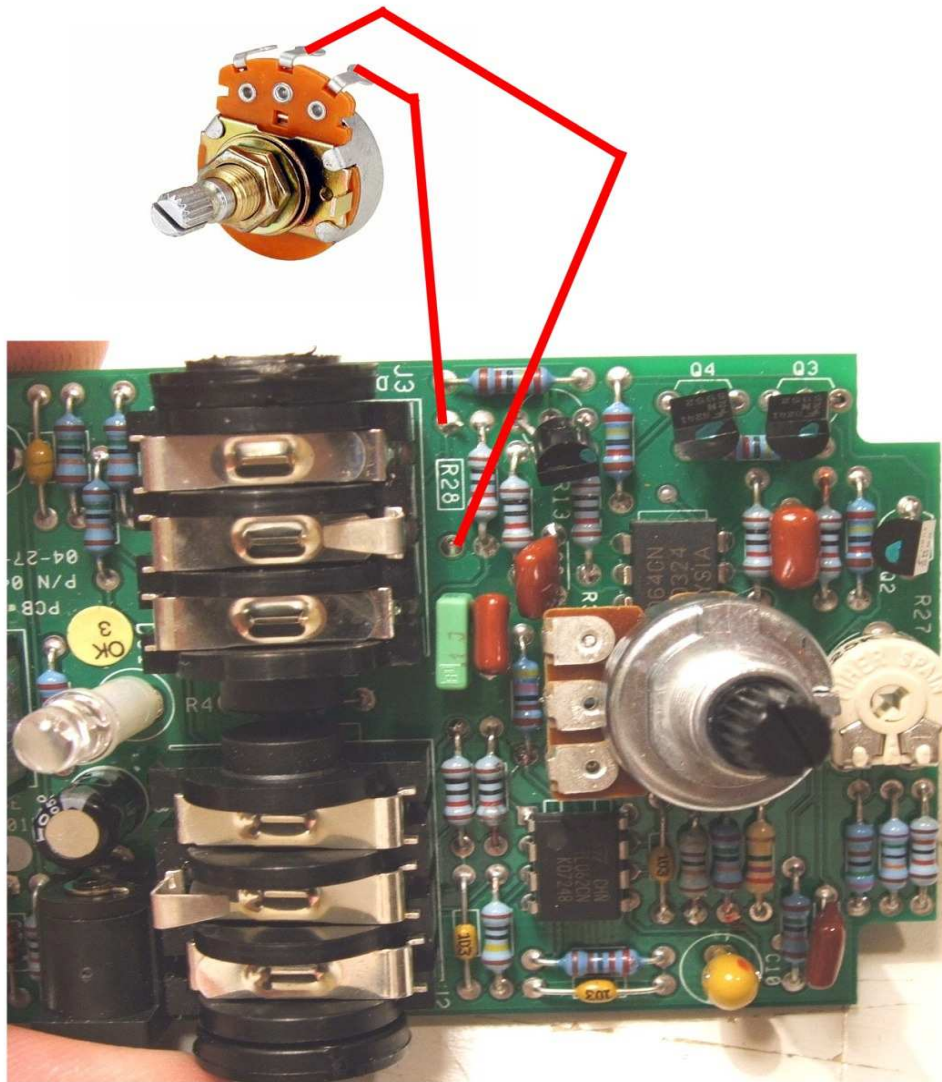Add Depth control to phase 90
-use a 47k pot or 100k pot if 47k is not available
-connect as shown




Tremelo Mod


Connect .1uf cap to the points shown below on the picture.

For standard Tremelo mod, do not change C3.

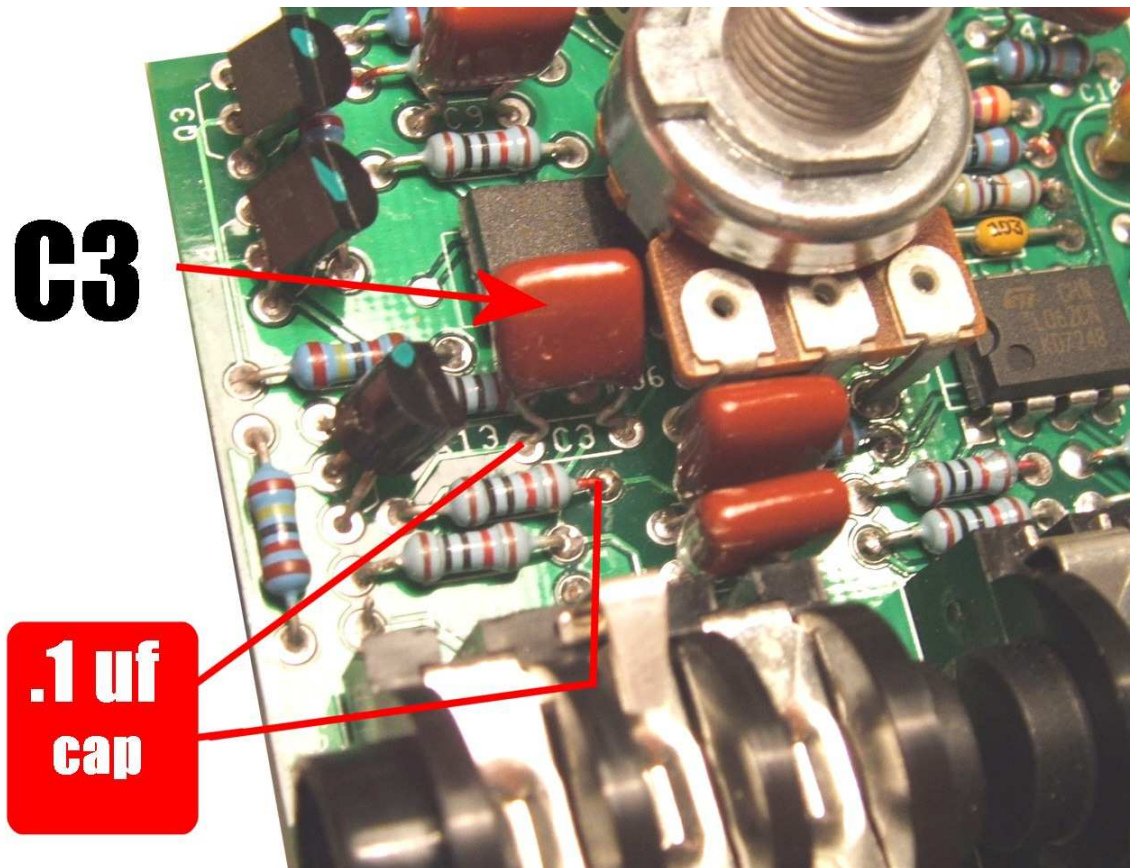For 'Dirty Tremelo' mod, change C3 to .068uf in addition to the change above.




Optional change of pedal's eq:

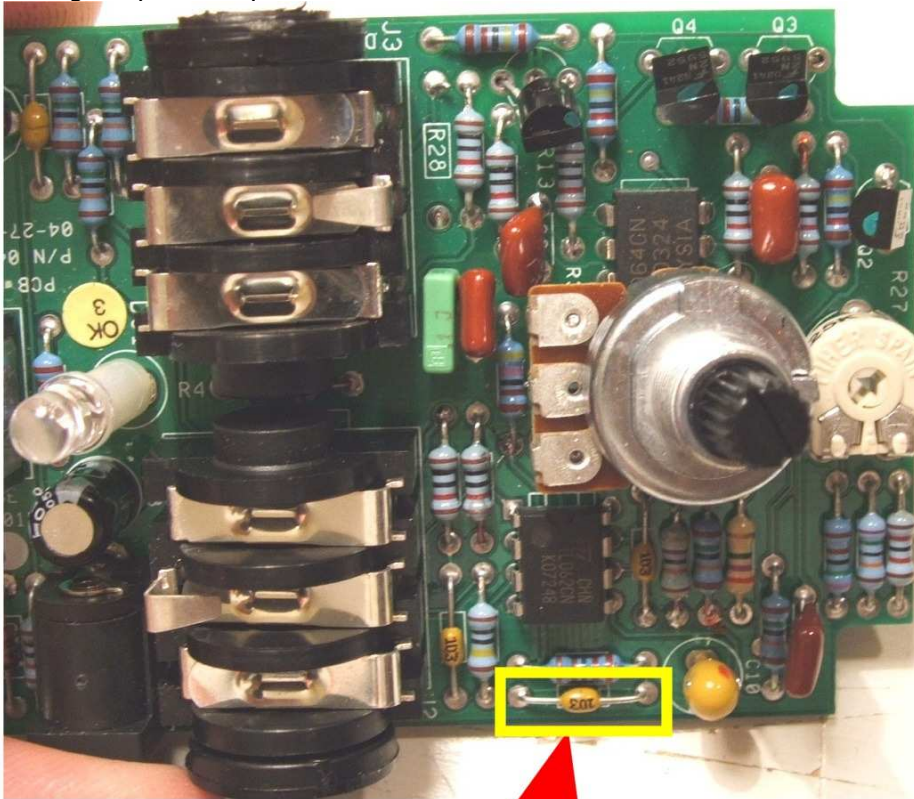

increase value for more highs
(try .015uf, .022uf, .033uf)

For a big volume boost,
and mid shift, change to
a .22uf

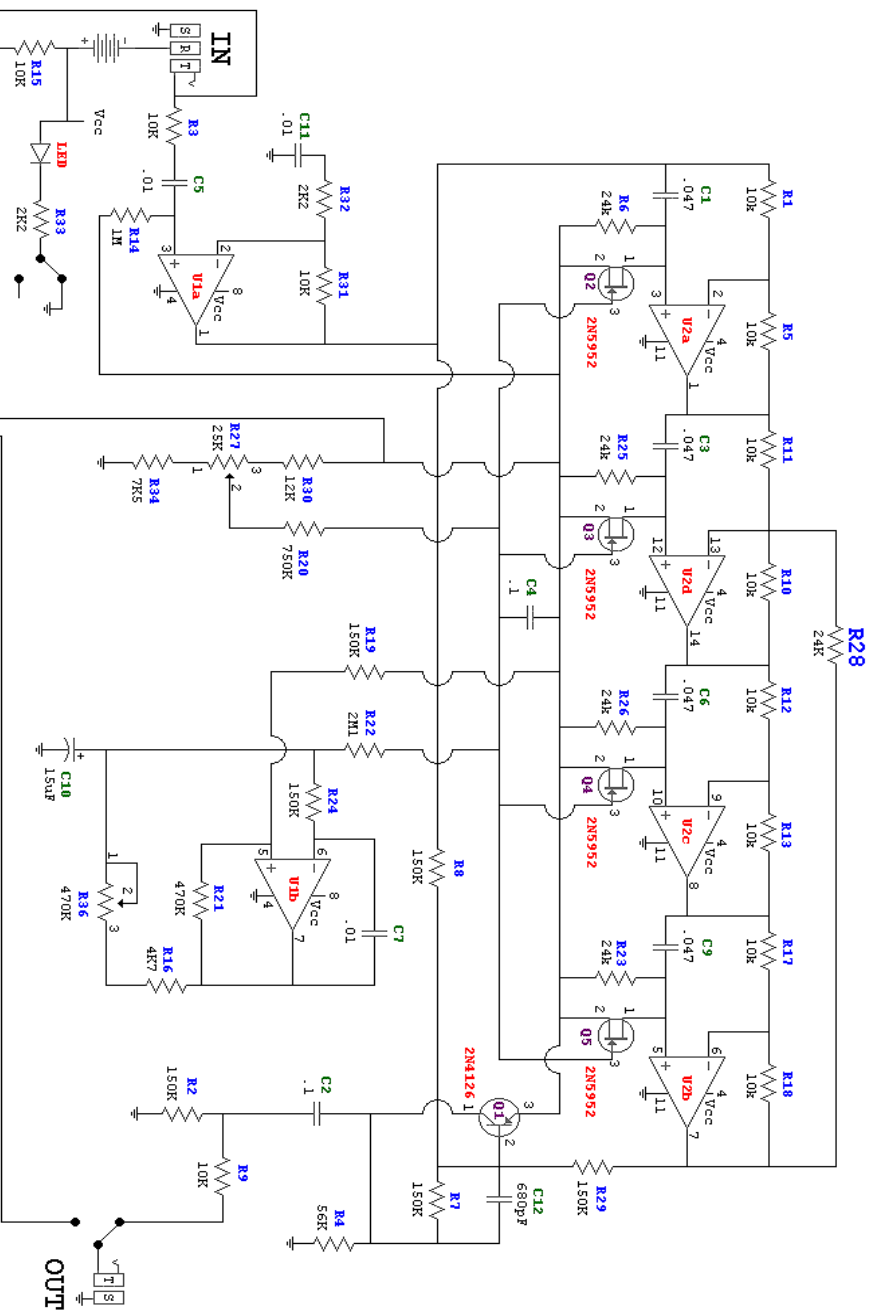

PHASE 90

(Reissue)

Nero F. Rox


www.jeanhatesjohnmusic.com
 www.mySPACE.com/jeanhatesjohn
 netofjeanhatesjohnmusic.com

*** Capacitors in uF unless noted
 *** DC Jack Wiring not Shown



Nobels ODR-1 Overdrive

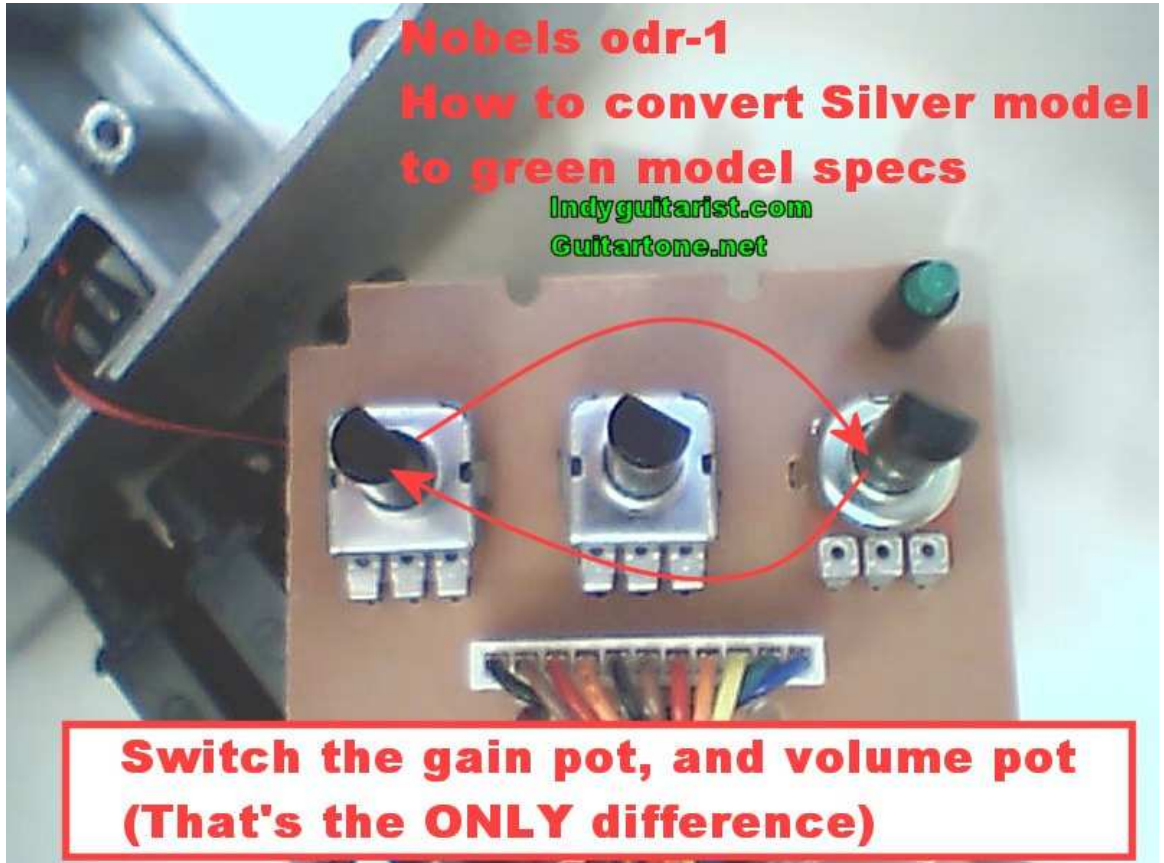How to convert silver model to green model specs, on the first version of the silver model. The newest versions are already fixed and are EXACTLY the same as the green nobels.



Nobels odr-1 modification

Location	Stock value	Mod value	What it effects
C34	.082 uf	.047uf / .068uf / .1uf / .15uf / .22uf / 1uf for bass guitar	Lower value for less bass, more value for more bass
R27	10k	4.7k	Adds highs
D4		LED and 1n4148 in series	Will add fullness, dynamics, becomes more responsive
D2		LED and 1n4148 in series	Will add fullness, dynamics, becomes more responsive

Hi Brian,

following our discussion re: Nobels ODR-1, the new version having the gain and vol pots reversed, i've done that and it sounds FAB !.

Also made these changes (after lots of trial 'n error) so thought you may appreciate the info for a "mod" @ indyguitarist

This apply's to the "Green" and the new "Silver" versions :

I didn't use diode "numbers" as they are blurred on the board !!
from those that I can read, these would seem to be D1/D2 and D3/D4.
Check the schematic to be sure of the numbers, from www.nobels.com

First "pair" of diodes near the "Flat inline op-amp" next to input/output jacks---- remove both 1N914's and use a single 3mm red LED.

A pair of 3mm red LED's also works but was to "Metal distortion" for me !

Second "pair" of diodes near the other "flat inline op-amp" middle of board --- remove both 1N914's and use a single Ge diode (1N34A)

This results in increased "volume" and a "tube" sounding sweet overdrive.

The 120pf cap around the first diode pair (tiny brown ceramic marked 121) can be increased to 150 or 180 to "roll off" a bit of the top end ---- result is smoother.

The 2.7nf cap around the second pair (C21) can be reduced to a 1.5nf to let some more "high mid/top end" come through.


Voicing is a personal thing, give it a try ?

The large 2.2uf input cap (C1) can be reduced to a 1uf and lets less bass through the circuit ---- result is a more "tube screamer" middle sounding pedal 😊

Hope you like this, most is obvious but worth the time

Regards,

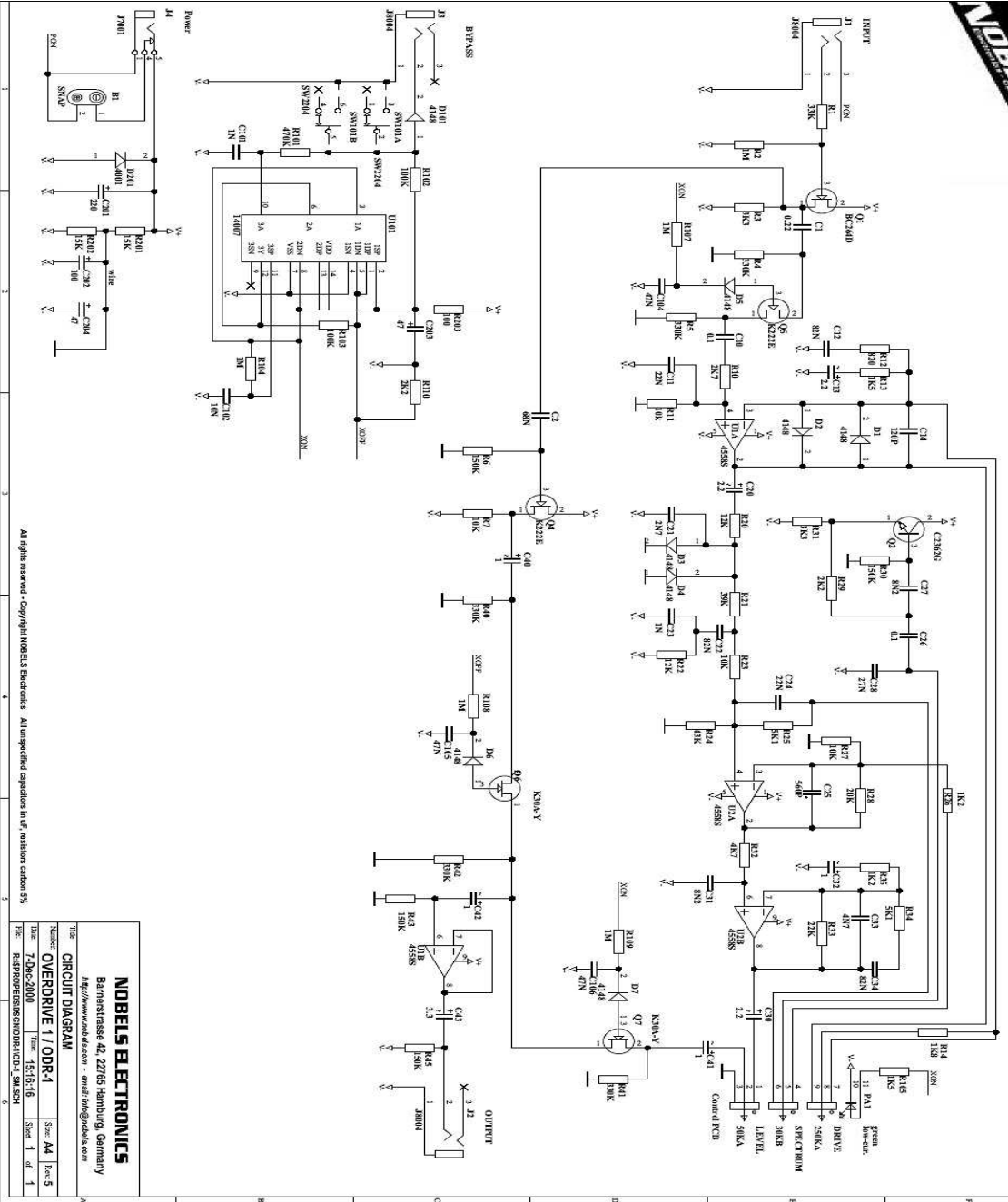
Marty from the messageboard at <http://www.diystompboxes.com/smfforum/>



Nobels DT-1

Most feel that the downfall of the dt-1 is that it is noisy and feedbacks easy. These are fairly easy fixes. The mod below will fix it.


Location	Mod value	Notes
R12	1K	
R14	220K	Lower value until feedback and noise stops
C11	1uf	
R11	2.2K	
C15	500pf	

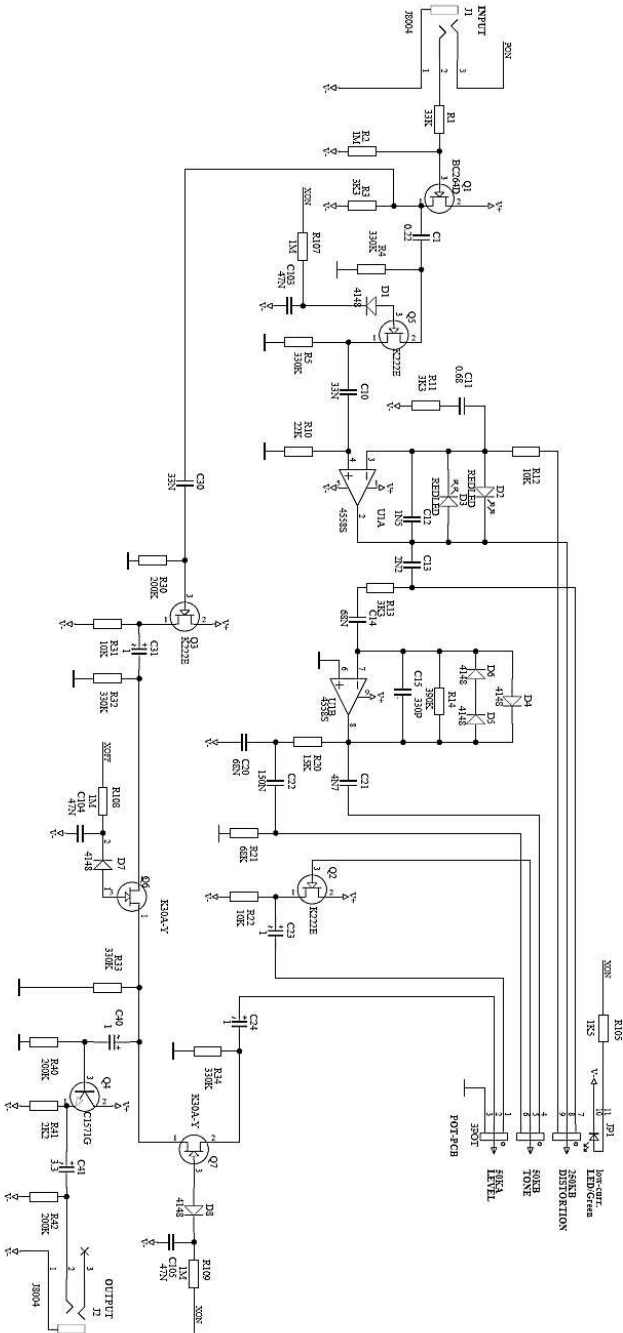

Nobels ODR-B

Most feel that the downfall of the ODR-b is that it is too compressed and too muddy. The mod below will fix that.

Location	Mod value	Notes
D1	Red led	
D2	Red led	
C21	.001uf	
R21	22k	
C25	220pf	
C33	100pf	

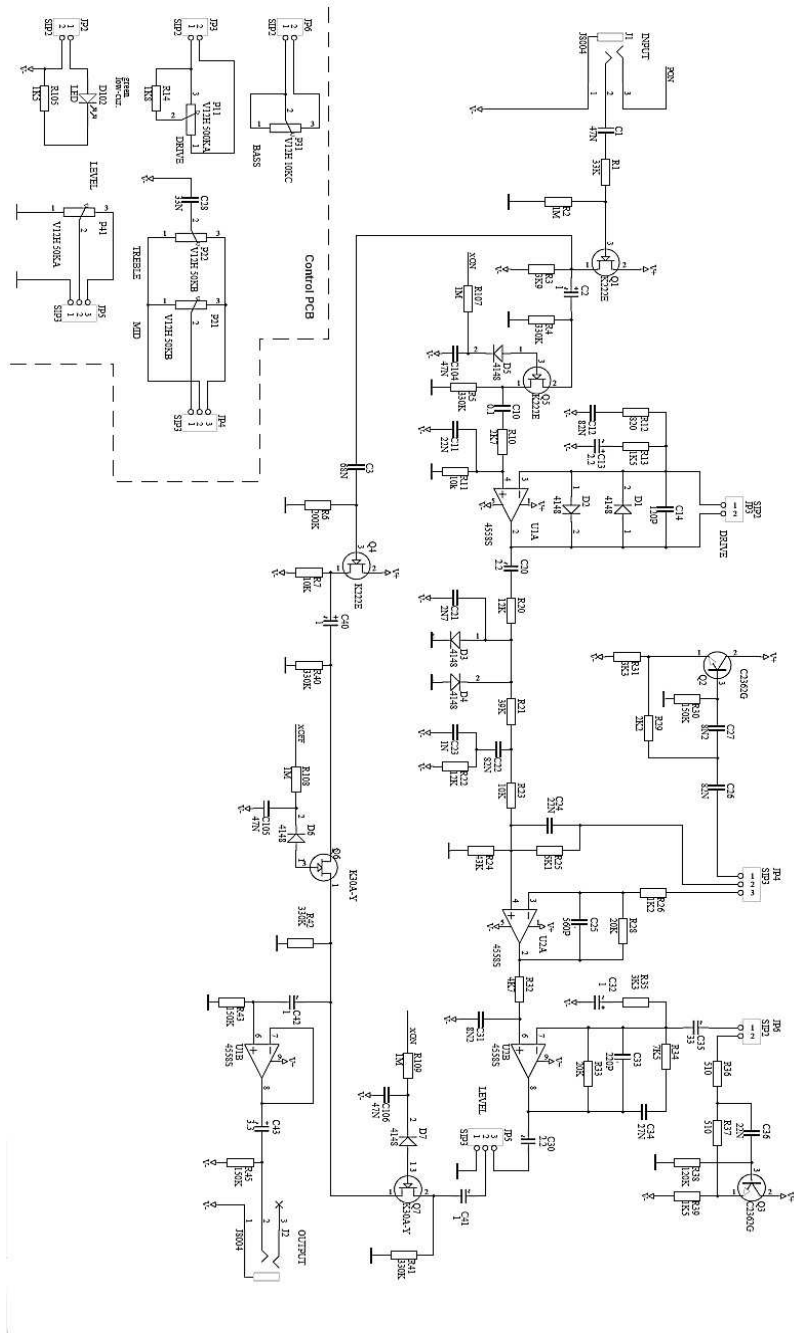

Nobels ODR-S

Thicker, warmer overdrive


Location	Mod value	Notes
D1	1n4148 + 1n4148 in series	
D4	1n4148 + 1n4148 in series	
C21	.0022uf	
R23	10k-33k	for more mids, 33k, for less mids, 10k

For more distortion

Location	Mod value	Notes
R12	470 ohm	
C11	1uf	

For more volume

Location	Mod value	Notes
R37	22k-47k	Adjust to taste

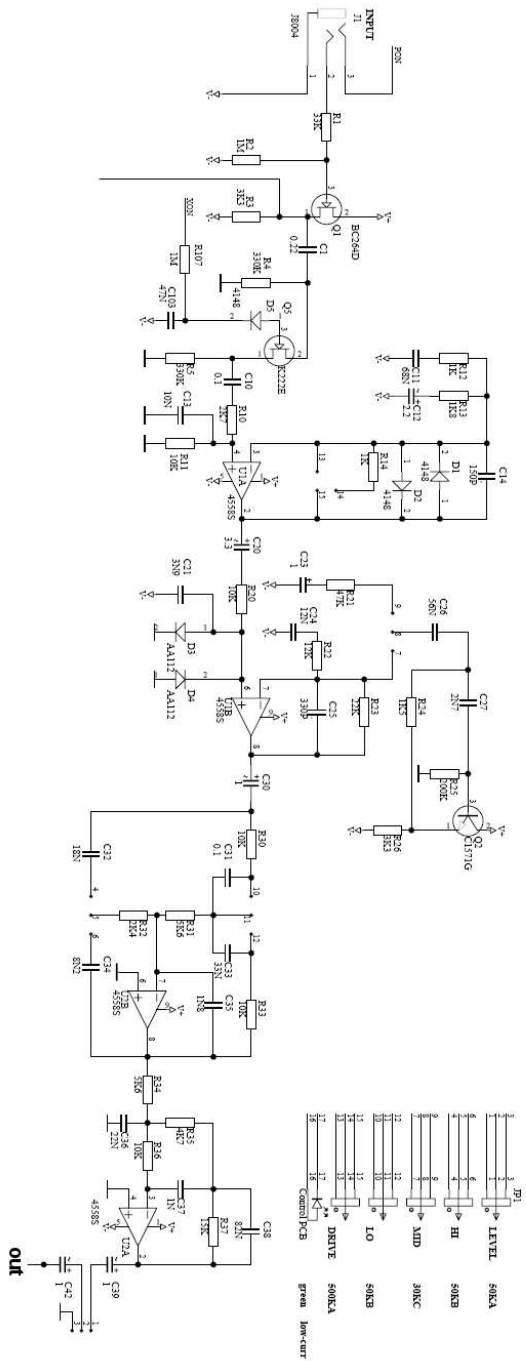

Proco Rat

Original Rat and Rat2 mods


Warning! The newest Rat pedals have potentiometers that many have had a hard time with. Apparently, when you pull the knobs off the shaft comes off with it and makes it very hard to put back together. If you've purchased a new rat since 2007, I would avoid these mods unless you are comfortable replacing the pots.

The original rat and rat2 circuits are very similar, nearly identical.



Here is a page that explains all the different version and the small difference between them:

http://happybob.com/rstrand/rat/rat_versions.htm

Original

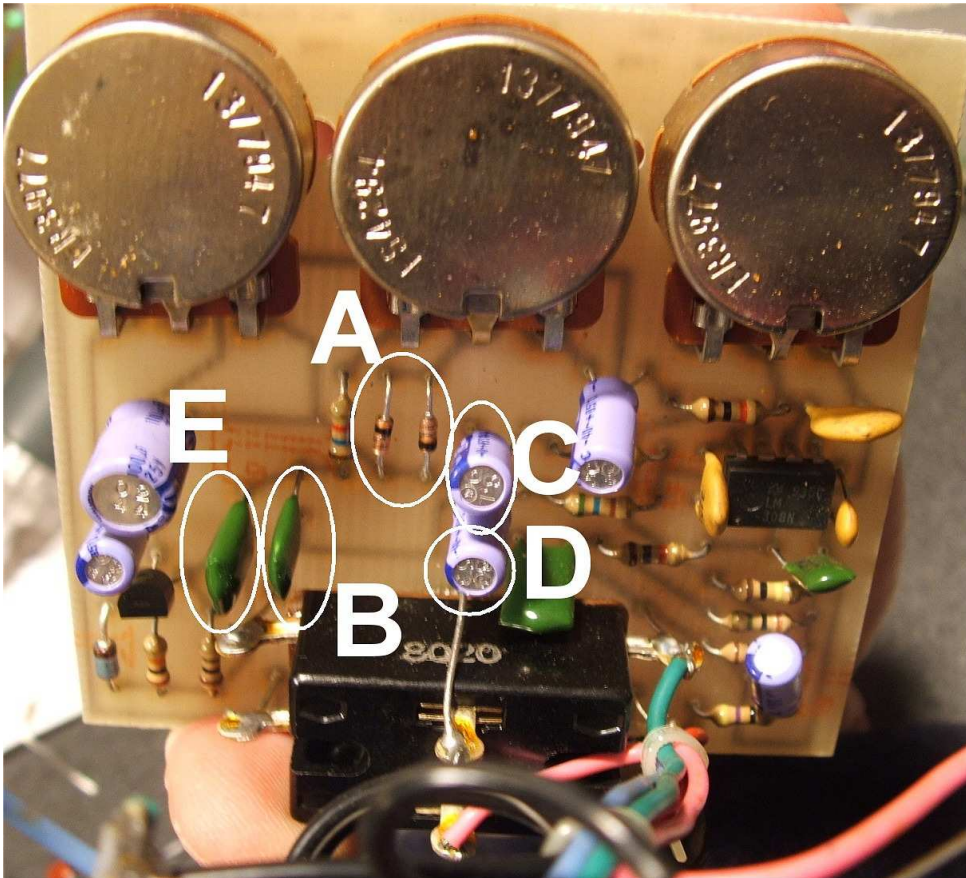


RAT 2

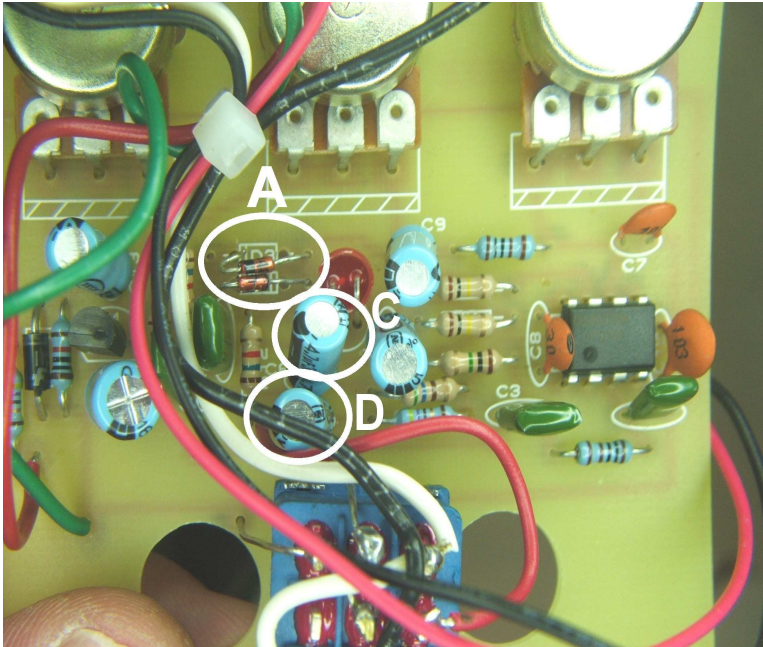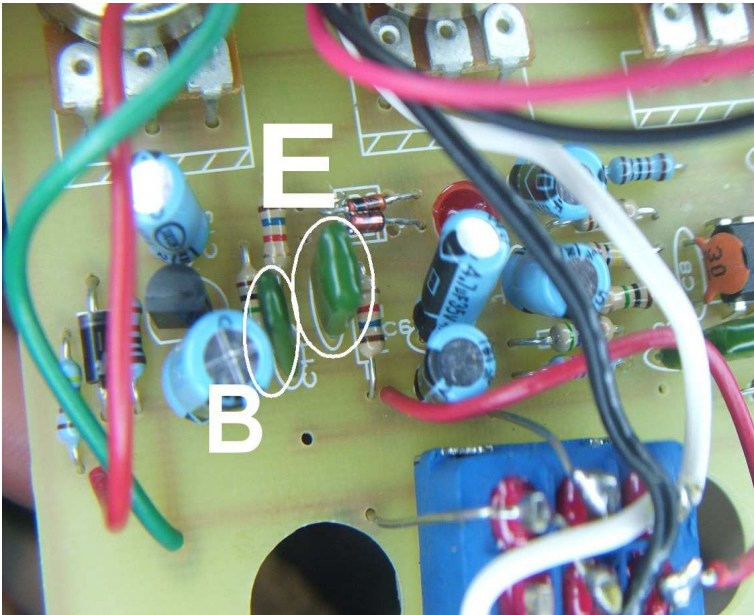


Location	Stock	Mod	Effect
A	1N4148 DIODES	2 – 1N4148 IN SERIES	REMOVE ONE OF THE DIODES. IN ITS PLACE, INSTALL 2 1N4148 DIODES CONNECTED IN SERIES. FOR SMOOTHER DISTORTION, INSTALL 1N34A GERMANIUM DIODES IN PLACE OF BOTH OF THE STOCK DIODES FOR CRUNCHIER DISTORTION (LIKE THE 'TURBO' RAT PEDALS), CHANGE THE STOCK DIODES TO RED 3MM LED'S ALSO TRY JUST CHANGING ONE OF THE DIODES TO A DIFFERENT TYPE... GERMANIUM 1N34A, LED, 1N4001 ETC.
B	.0033uF	.0047uF, OR .0068uF	CHANGE THIS CAP IF YOU FIND THE STOCK PEDAL TO HAVE TOO MUCH TREBLE.
C	4.7UF	10uF	CHANGE THIS CAP FOR MORE BASS CONTENT
D	2.2UF	4.7uF	CHANGE THIS CAP FOR MORE BASS CONTENT
E	.022uF	1uF	CHANGE THIS CAP FOR MORE BASS CONTENT


Options:

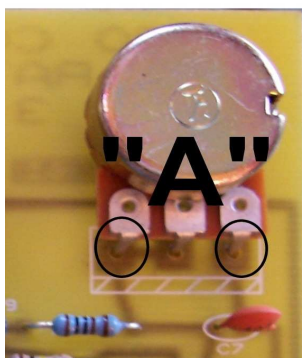For a more compressed, smoother tone, install 2 diodes (experiment with type!) in parallel, but facing opposite directions, solder directly to lugs 1 and 3 (the outside lugs) of the gain pot. For a "smooth/compression" adjustment, install a 2nd potentiometer, possibly a 50k or so, in SERIES with these diodes. +




Another Circuitboard version:

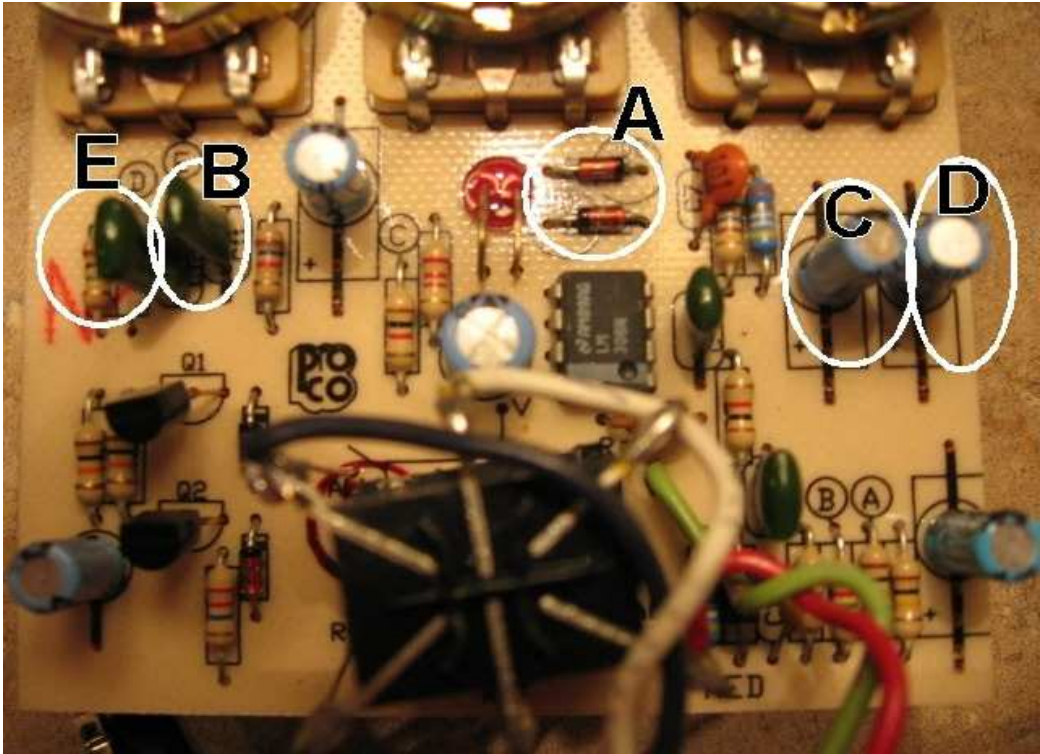

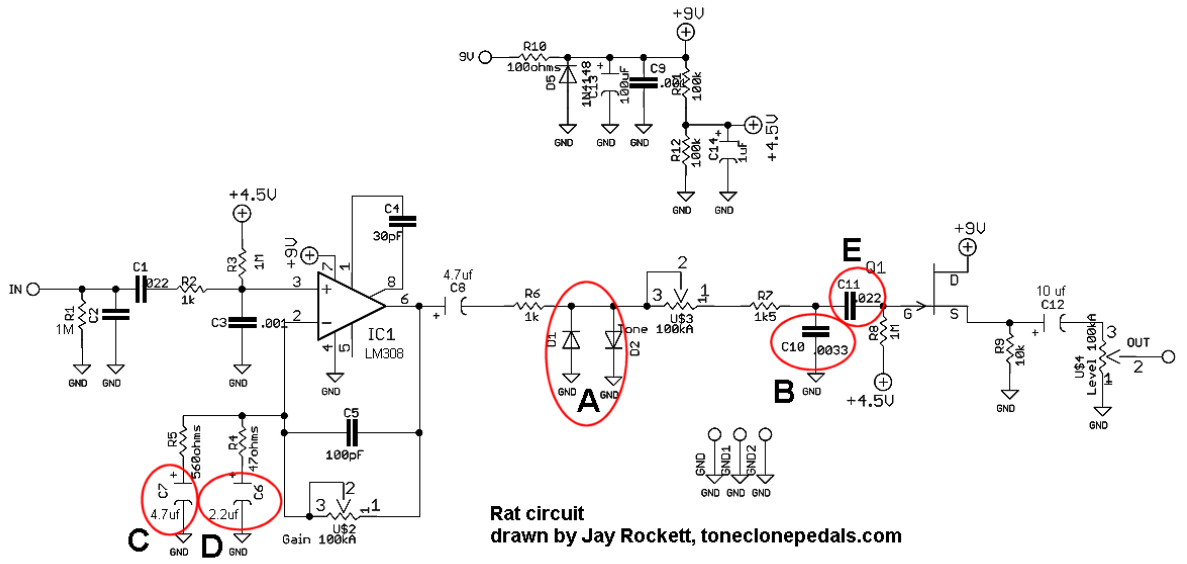

Rocktron Sonic Glory Overdrive

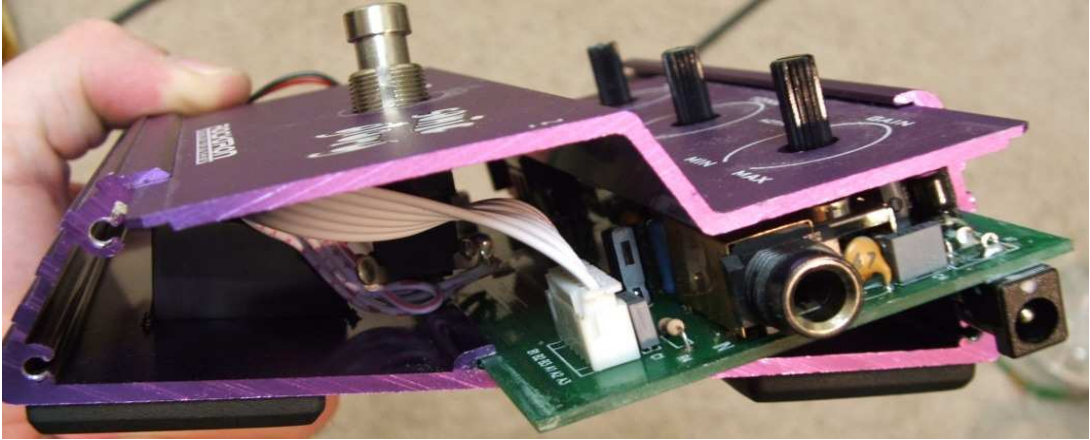To disassemble, take off the nuts connected to the jacks, and unscrew the screws on the sides.



Also, make sure you unscrew the switch, take off the knobs, and slide the bottom out and away from the top piece and then drop out the circuitboard from the top piece.



Circuit-wise, the sonic glory is almost an exact tubescreamer clone.

BSM (Brent Mason) MOD

Location	Mod value	What it affects
R13	1K RESISTOR	This mod will make the pedal fuller, more responsive, and dynamic. This is the same mod that Brent Mason uses on his TS9.
C4	.22UF x 2 in parallel CAP	
R12	10K RES	
D1	1N4001	
D2	1n4001 + 1n4001 SERIES	
C3	.15 uf or .047 + .1 uf in parallel (results in the same thing)	

316 MOD


Location	Mod value
R13	1K RESISTOR
C4	.22UF
R12	10K RESISTOR
D1	LED
D2	LED + 4148 in SERIES


standard Mod

Location	Stock value	Mod value	What it affects
C4	.047 uf	.1 uf	Adds bottom end. For more, go .22 uf
D1	1n4148	LED & germanium 1n34a in series	Adds fullness, depth, and dynamics
D2	1n4148	1N4001	
R13	4.7k	3.3k	The lower the value, the more distortion available.

Explanations

Location	Mod Value	What it affects
R12	10k	Will allow pedal to clean up when gain knob is turned down
C3	Raise value - .44uf, .1 uf	Raising value will decrease the highs. Alternatively, lessen the value to bring more highs in (.15uf, .1 uf)
C4	Raise value for more bass	.1, .22, .44, .1 uf - works in conjunction with # 6 resistor
D1, D2	Clipping diodes	Experiment—it will shape the tone and overdrive considerably!
R13	Gain resistor	Lower value for more gain, and clarity. 2.2k, 1k, works in conjunction with #4.
EXTRA		
R1	10K-22K	Adds volume and lows.
C5	.47uf and 1k resistor connected in series	Reduces the mids quite a bit.

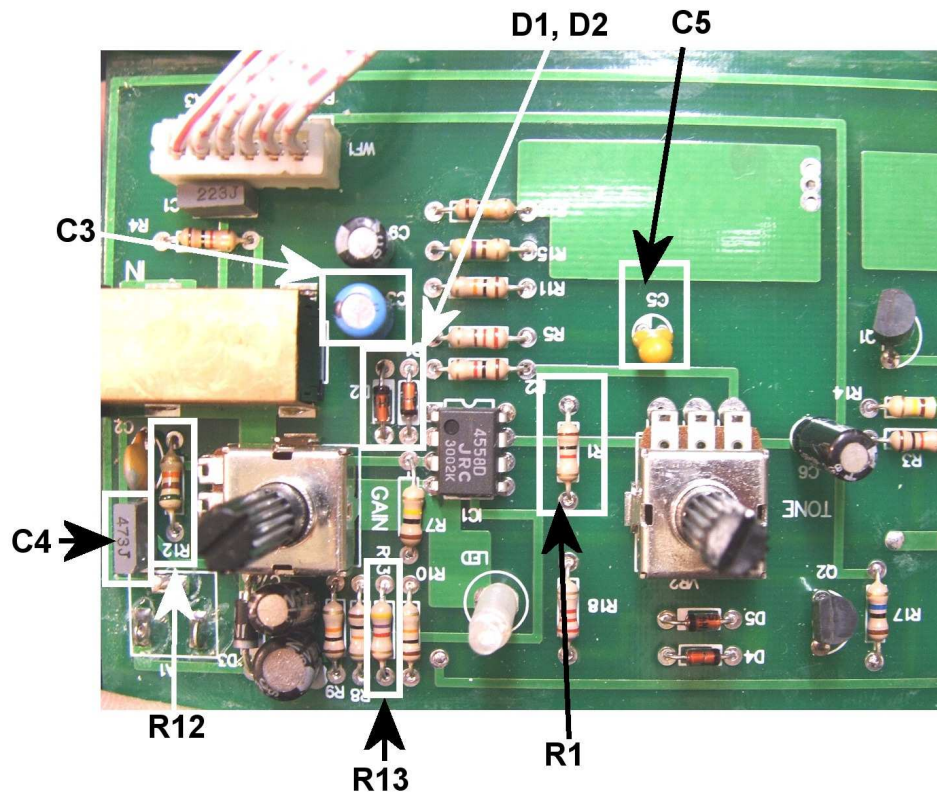

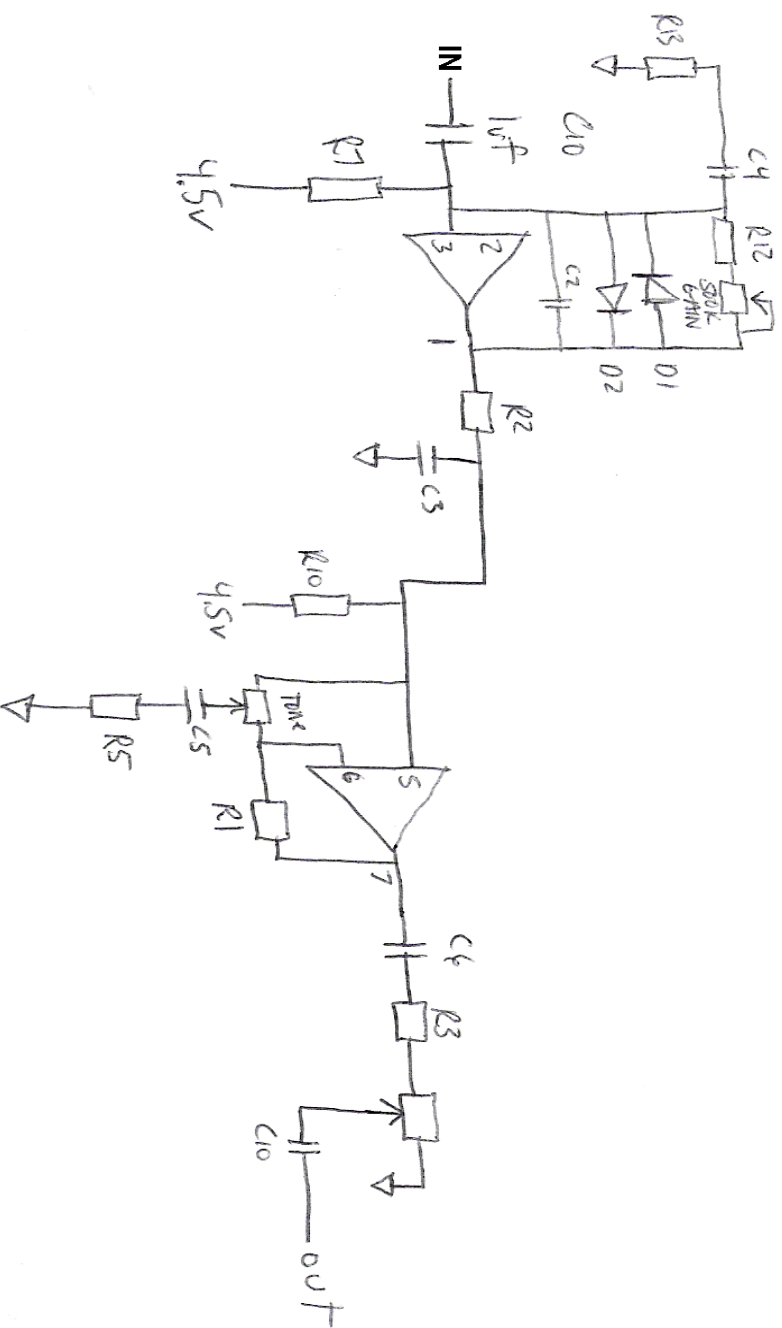

ROCKTRON SONIC GLORY OVERDRIVE
(C) 2006 BRIAN WAMPLER, INDYGUITARIST.COM

VooDoo Lab Sparkle Drive

BSM (Brent Mason) MOD

Location	Mod value
R4	1K RESISTOR
C4	.22UF x 2 in parallel CAP
R5	10K RES
D1	1N4001
D2	1n4001 + 1n4001 SERIES
C5	.15 uf or .047 + .1 uf in parallel (results in the same thing)

316 MOD

Location	Mod value
R4	1K RESISTOR
C4	.22UF
R5	10K RESISTOR
D1	LED
D2	LED + 4148 in SERIES


Standard Mod


Location	Stock value	Mod value	What it affects
C4	.047 uf	.1 uf	Adds bottom end. For more, go .22 uf
D1	1n4148	LED & germanium 1n34a in series	Adds fullness, depth, and dynamics
D2	1n4148	1N4001	
R4	4.7k	3.3k	The lower the value, the more distortion available.
R5	51K	22K	Allows the pedal to get much cleaner with the gain knob down low.

Extra's


Location	Mod Value	What it affects
R5	10k	Will allow pedal to clean up when gain knob is turned down
C5	Raise value - .44uf, .1 uf	Raising value will decrease the highs. Alternatively, lessen the value to bring more highs in (.15uf, .1 uf)
C4	Raise value for more bass	.1, .22, .44, .1 uf – works in conjunction with # 6 resistor
D1, D2	Clipping diodes	Experiment—it will shape the tone and overdrive considerably!

R4	Gain resistor	Lower value for more gain, and clarity. 2.2k, 1k, works in conjunction with #4.
----	---------------	---

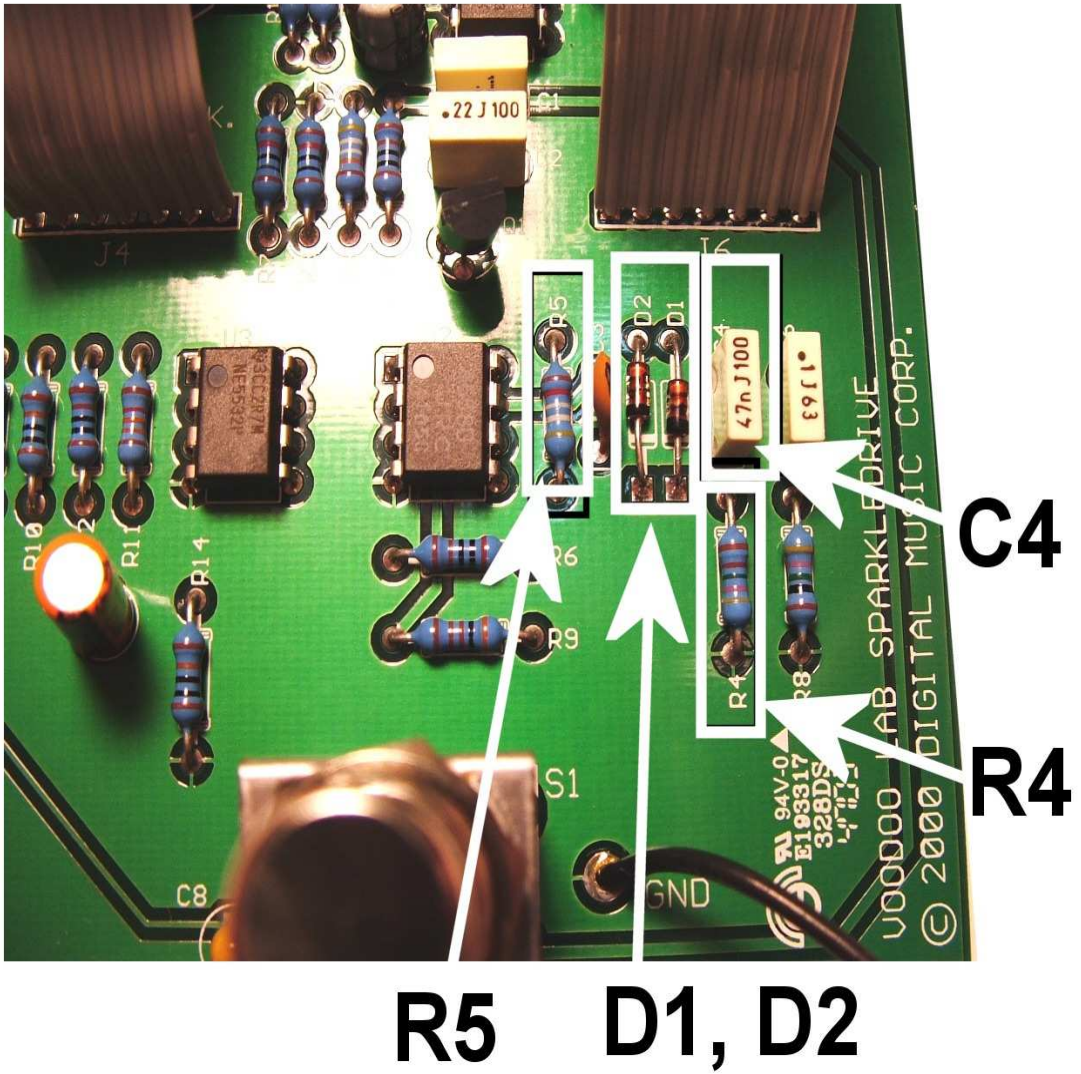

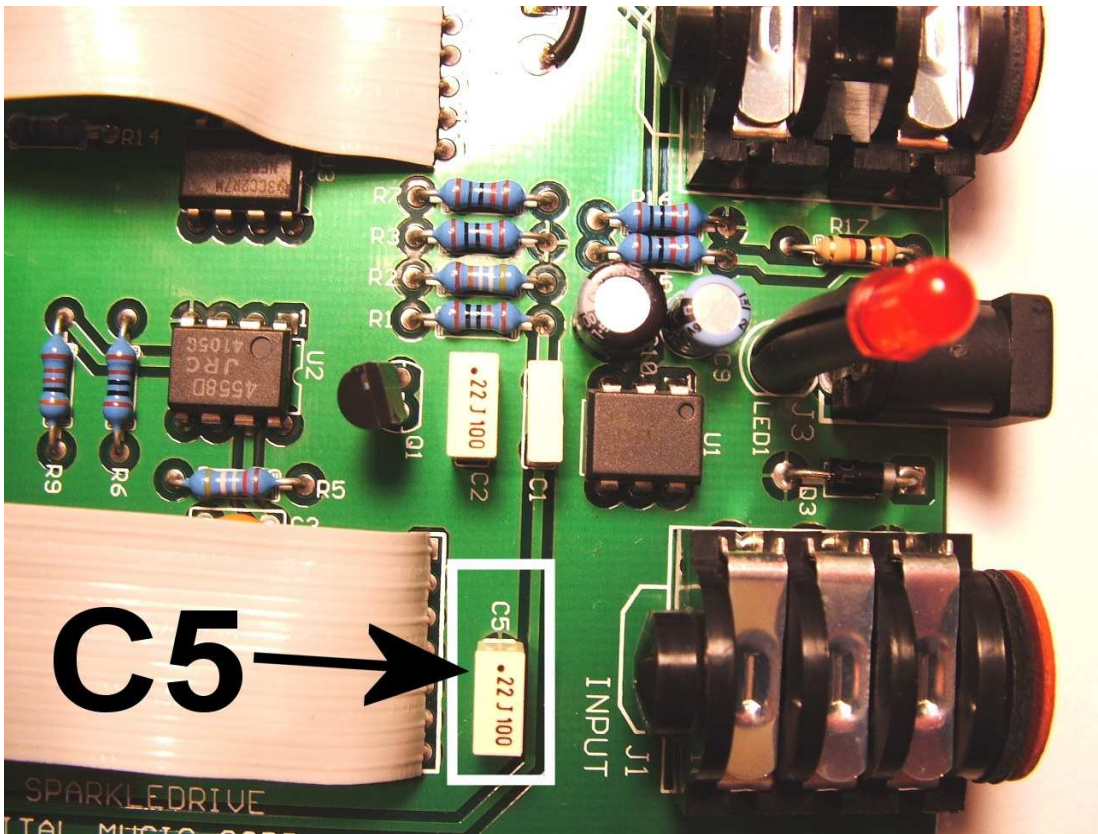


FOUND ON WEB

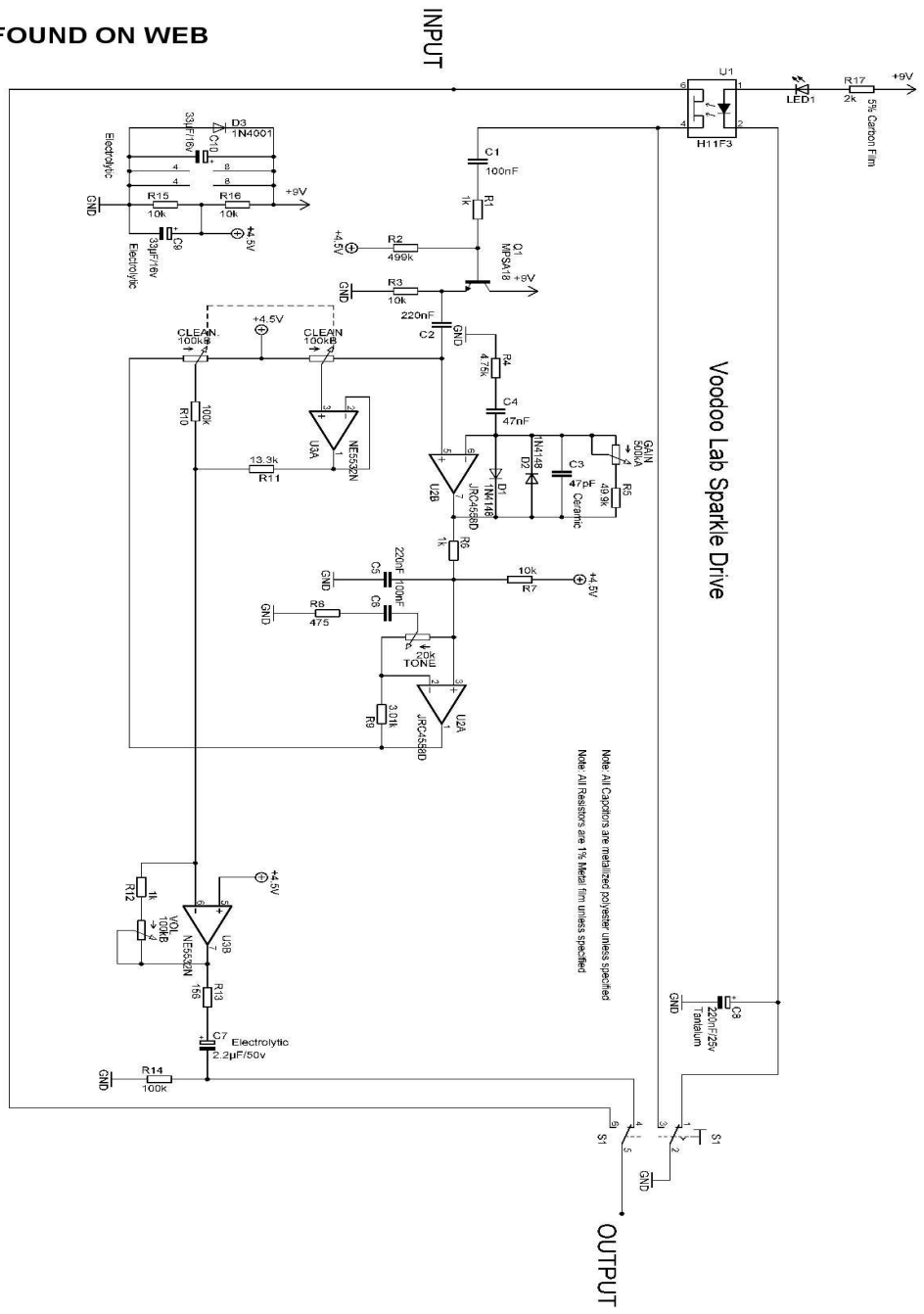




VooDoo Labs Microvibe

Location	Stock value	Mod value	What it effects
R2	3.3k	Jumper	Adds fullness, increases speed potential
R8	47k	39k	Lower value for more volume if needed
R15	47k	33k	Will give tremolo effect instead of rotating speaker

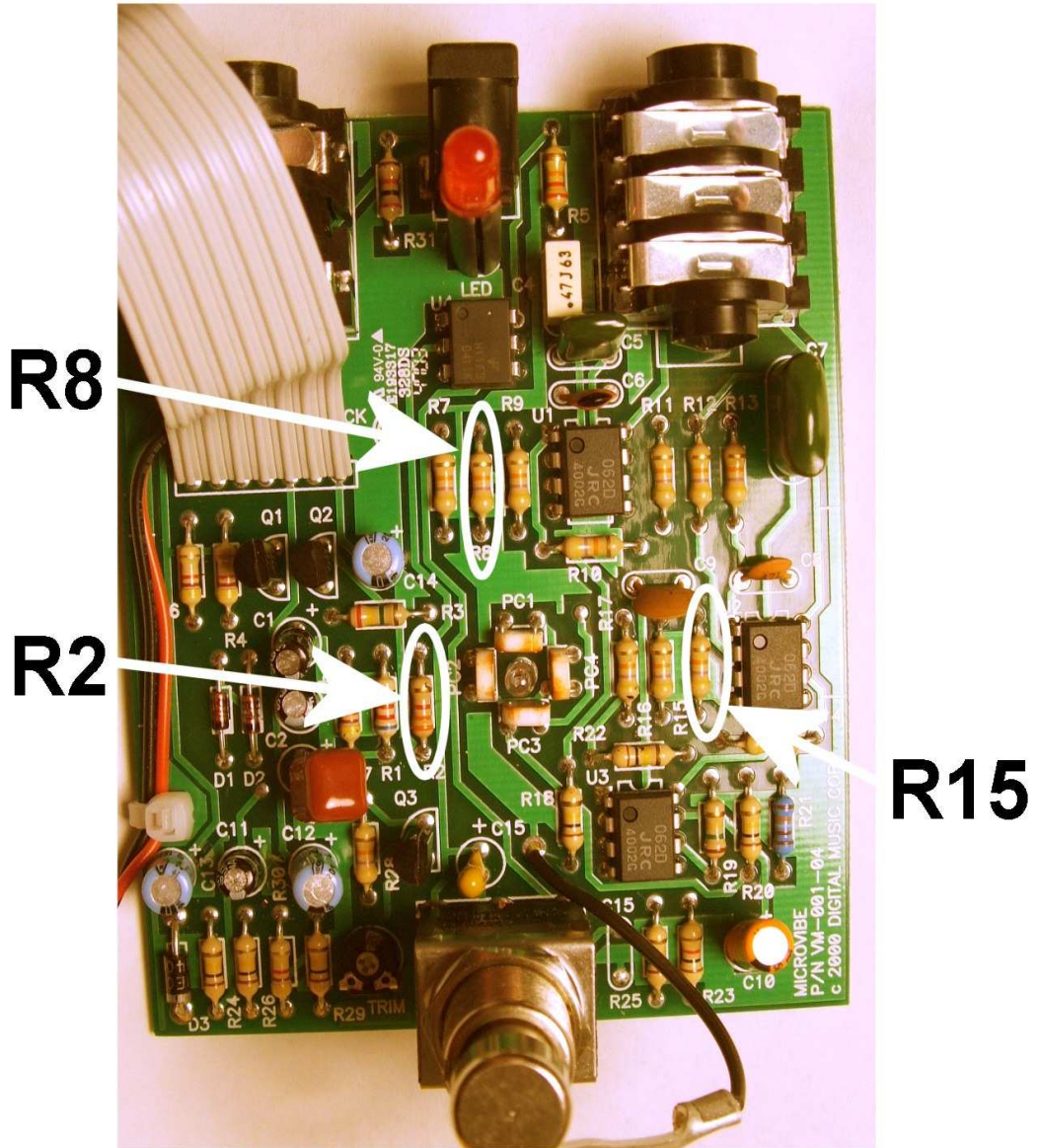

Tube Driver – 3 knob version

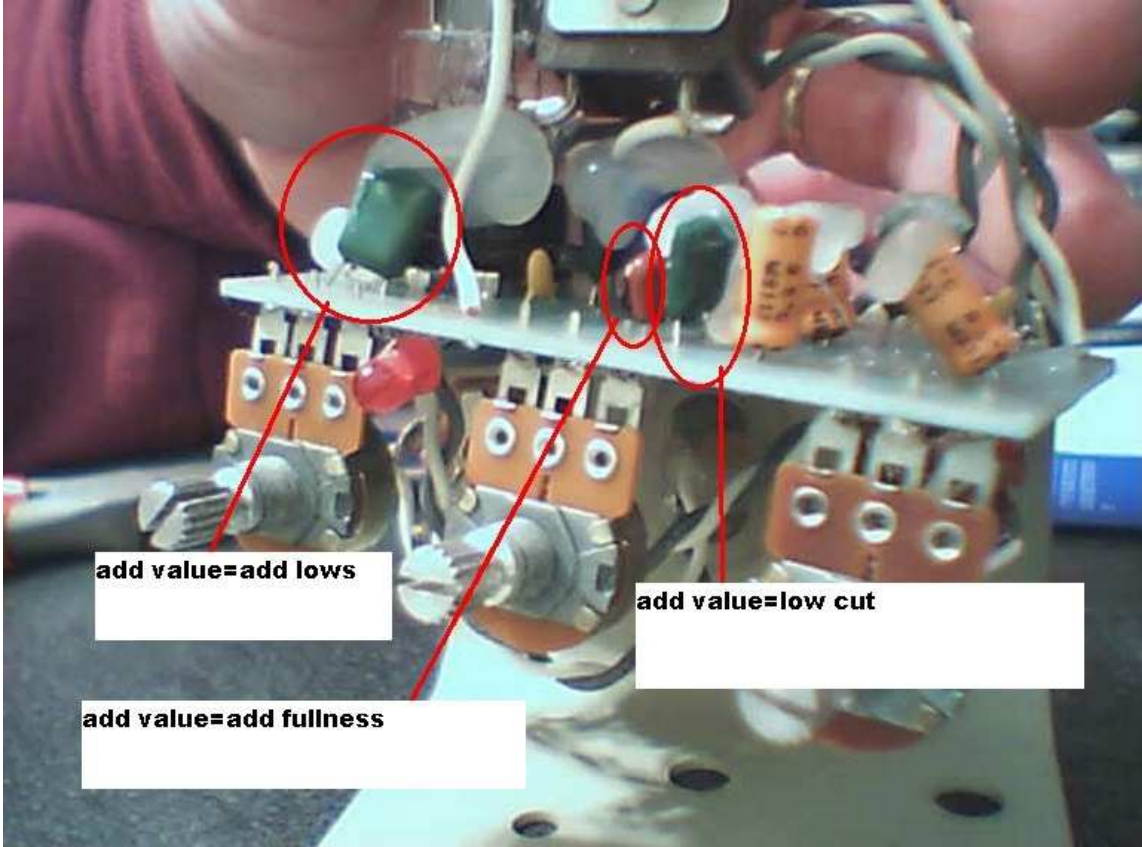

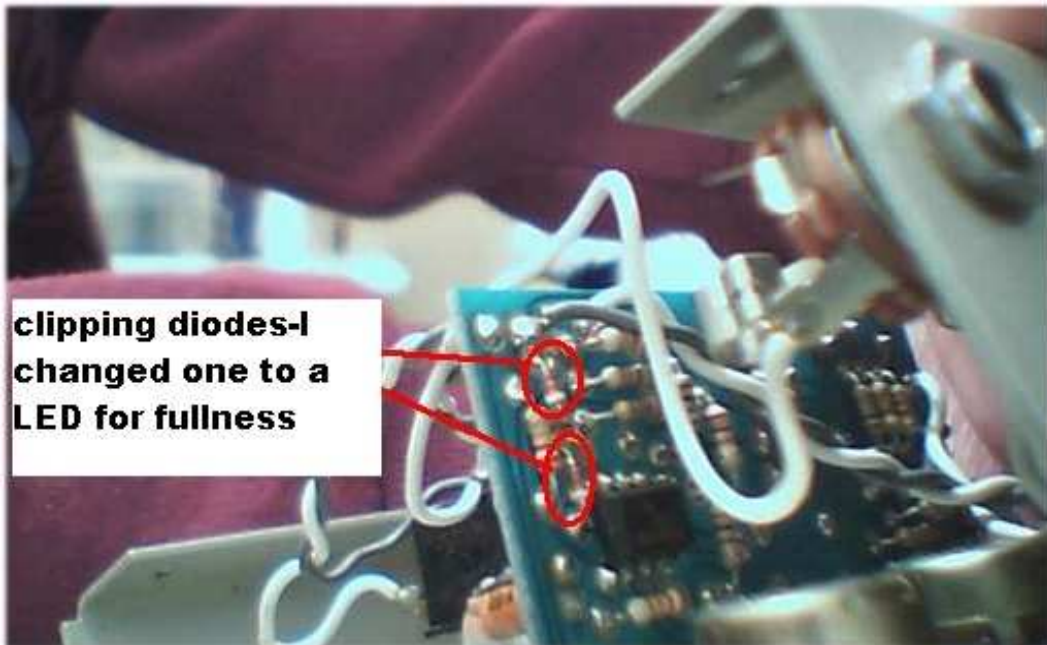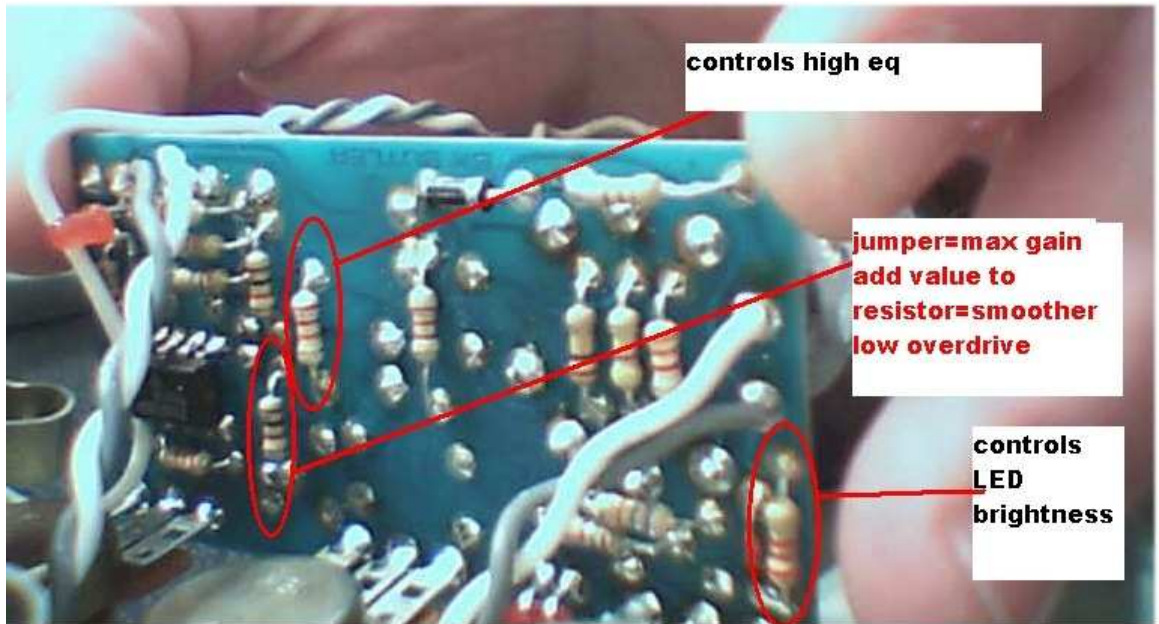

4 knob version of older chandler type tube drivers:


The stock tube drivers come with clipping diodes in the circuit board that generate most of the gain from about 9:00 to 'all the way up'. To get more tube gain, there is a 22uf cap wired the left side of the tube (when your looking at the tube itself). remove the 22uf and replace with a 47uf.

More tube gain instantly, and when you max the gain knob-it has an UNREAL amount of distortion.


replace the mediocre stock 12AX7 with a 12ax7 from <http://www.eurotubes.com> - Tell Bob I sent ya!

Visual Sound Quick How-to Guide

remove nuts, washers, knobs

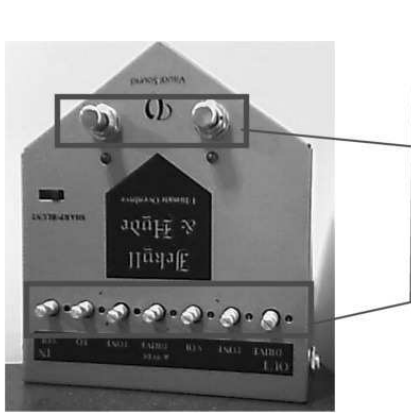


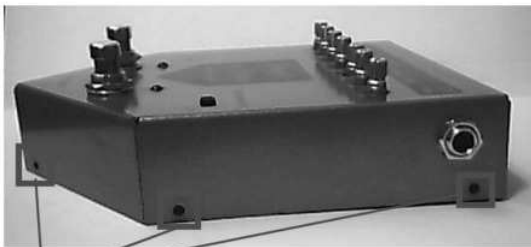**gently work the pots
and switches out of the case**



remove screws on perimeter



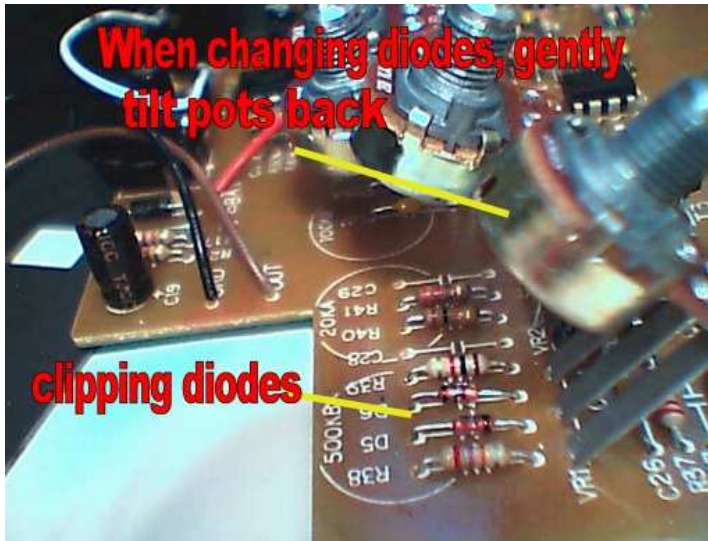

Note:
If your pedal looks like this, these modification do not apply:




Route 66


Location	Stock value	Mod value	What it effects
Overdrive side:			
C28	.22 uf elec cap	.15 uf film cap	Makes the pedal have less mids
C25	1 uf elec cap	1 uf film cap	Clearer, more hi-fi tone
C10 (may be marked incorrectly, but see picture below for location)	1 uf elec cap	1 uf film cap	
D5	4148's	1n4001	Makes the tone louder and fuller
D6	4148	1n4148 + 1n4148 in series	
R38	33k	4.7k	Allows the pedal to clean up better
Compression side:			
C23	.22 uf elec cap	.22 uf film cap	Clearer, more hi-fi tone
R10	100k	220k trim pot	Change the resistor to a 220k trim pot (lugs 1 and 2) to adjust the attack on the compressor.

Circuit explanation:


Basically, the route 66 is a tubescreamer type circuit, combined with a ross type compression circuit with a tone control that is similar to the tubescreamer tone control.

C28
R37
R61
C27
C23
C25

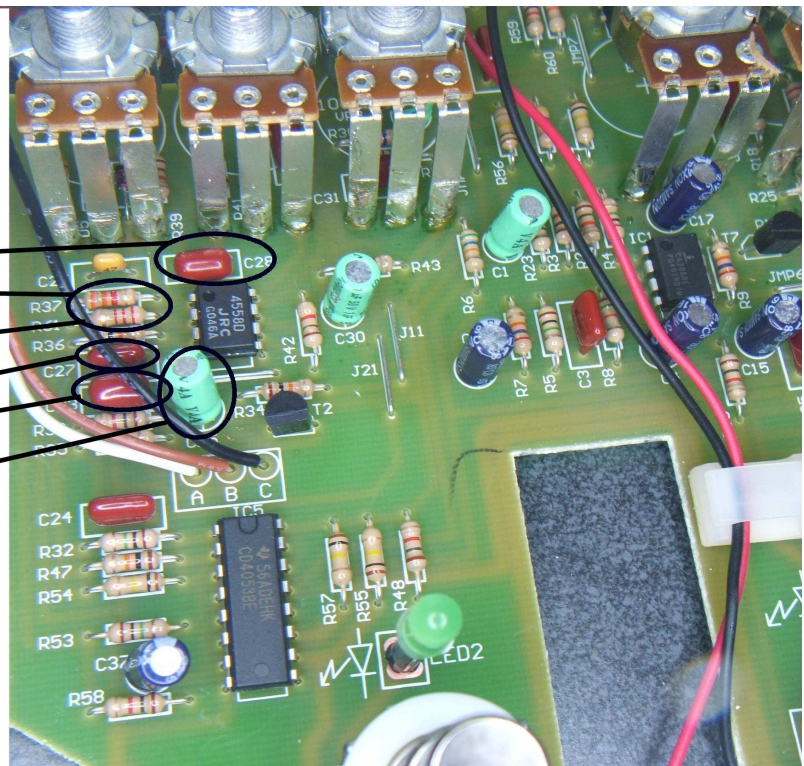

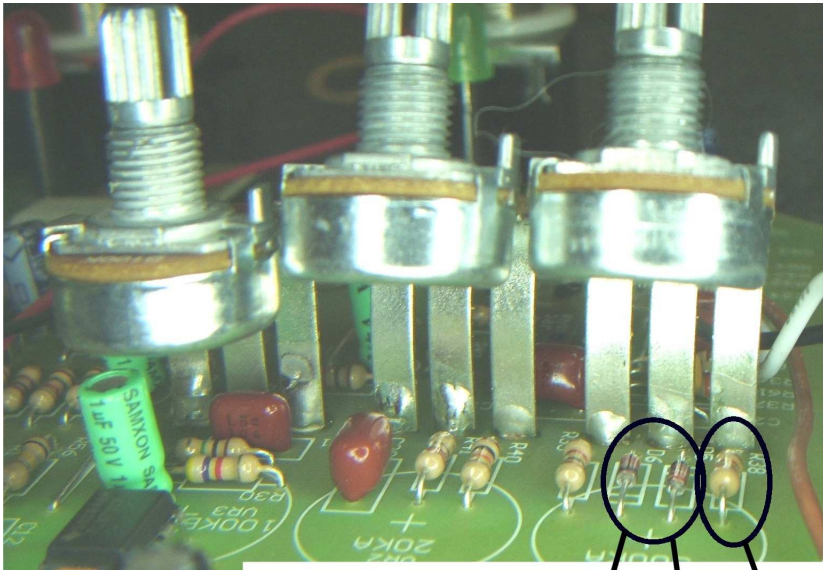


D5 D6 R38

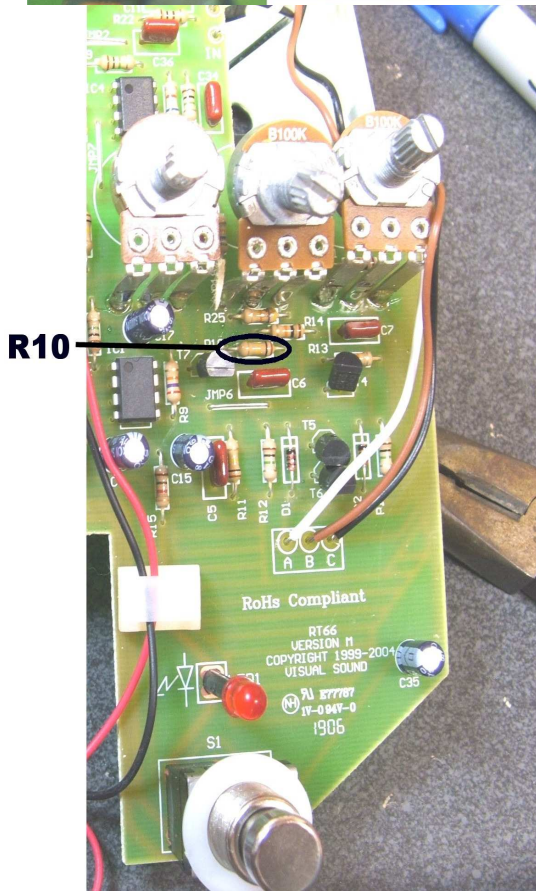

Jekyll & hyde (gray box version) mod

Location	Mod value	Part
Jekyll		
D5	1n4001	
D6	4148 + 1n4148 in series	
C27	.22uf or .44uf for more bass	The bigger the capacitor, the more bass is added to the overdrive side
R37	1k	Adds more gain potential, and adds clarity
R38	10k	Adds ability to be much cleaner when gain knob is turned down
C28a	.15uf	Adds fullness, less mid hump
Hyde		
R18	33k, or 22k	Lowers bass boominess
R1-stock 47k (optional)	1k-22k?	Lower value—adds mids
D3	1n4001 + 1n4001 in series	

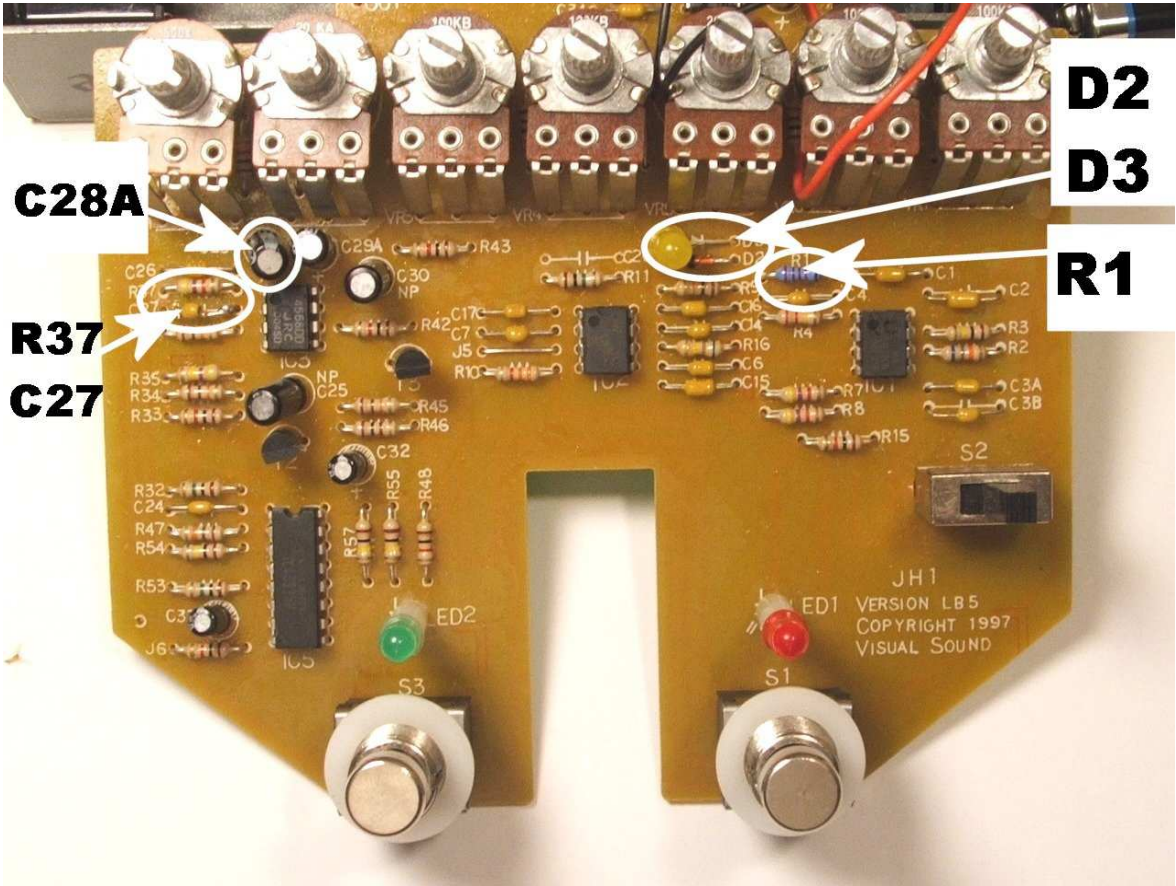

C28A


R37


C27

D2

D3

R1

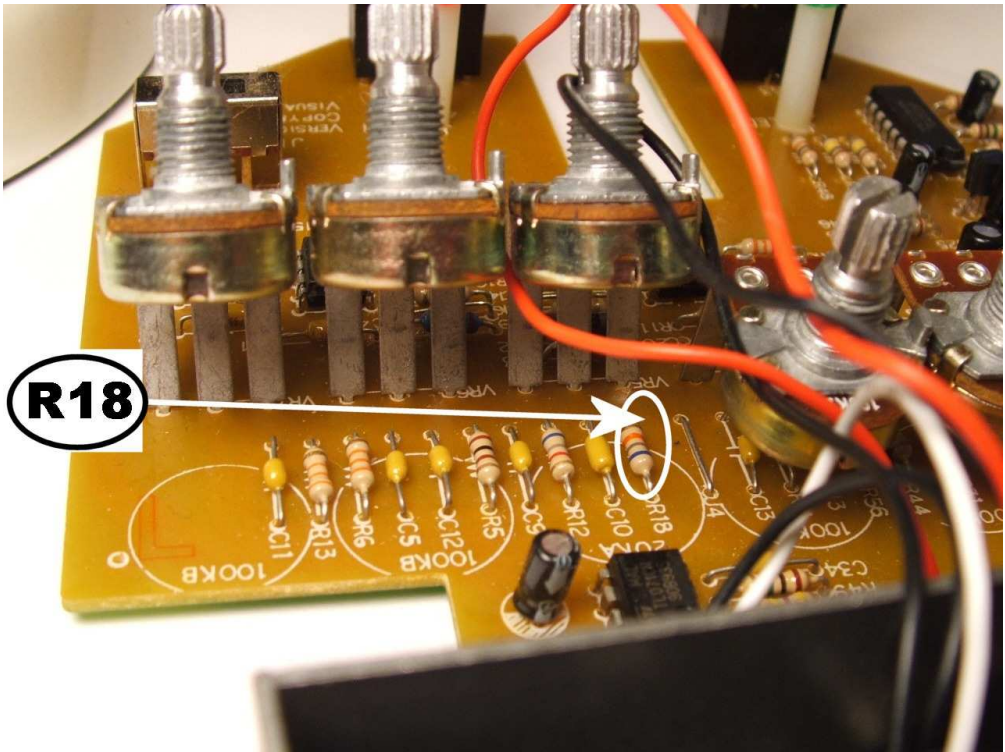

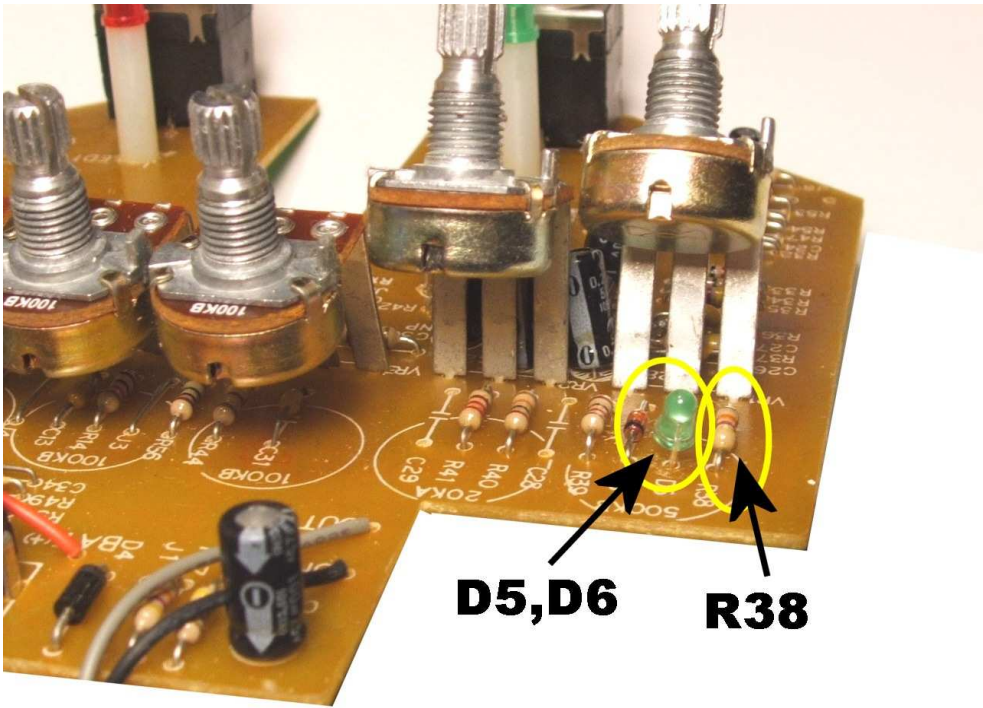

Red Version (newer version)next page.

Jekyll & hyde (Red Box version) mod

Location	Mod value
Jekyll	
D5	1n4001
D6	1n4001 + 1n4001 in series
C27 (option a: sub for R61)	.4 uf
R37 (option a: sub for C23)	1k
C28	.15 uf
R38	10k
Hyde	
R12	4.7k
IC2 and IC3	Change to a JRC4580 or LM1458
C5	Optional: Change the mid contour frequency by changing C5 to a .0015 or .002uf cap
C3b	330pf or for less highs 500pf

If you want to lower maximum volume (it's a loud pedal!), here is what Bob Weil of Visual Sound suggests:

The easiest way to lower the maximum volume on the new J&H is as follows:

For Jekyll, lower R21 from 6.8k to about 5.6k

For Hyde, raise R2 from 22k to about 47k.

All the best,
 Bob Weil
 Visual Sound LLC

Vox 847 wah

Location	Stock value	Mod value	What it effects
A	33k resistor	47k, 68k, 100k, If you use a 100k pot, you can custom tailor the 'vocal' effect *	Gives a cool 'vocal' wah type effect
B (optional)	1.5k resistor	2k, or 2.2k resistor	Controls amount of midrange present
C (optional)	.01 uf	.015 uf cap	Controls the sweep range

*See "how to replace a resistor with a potentiometer elsewhere in this book.


Diagram for '60's-'80's Vox, Crybaby, Dunlop: <http://www.fulltone.com/vox6080.html>

Text for '60's-'80's Vox, Crybaby, Dunlop: <http://www.fulltone.com/vox6080copy.html>

Diagram for Reissue Vox V847: <http://www.fulltone.com/v847.html>

Text for Reissue Vox V847: <http://www.fulltone.com/V847copy.html>

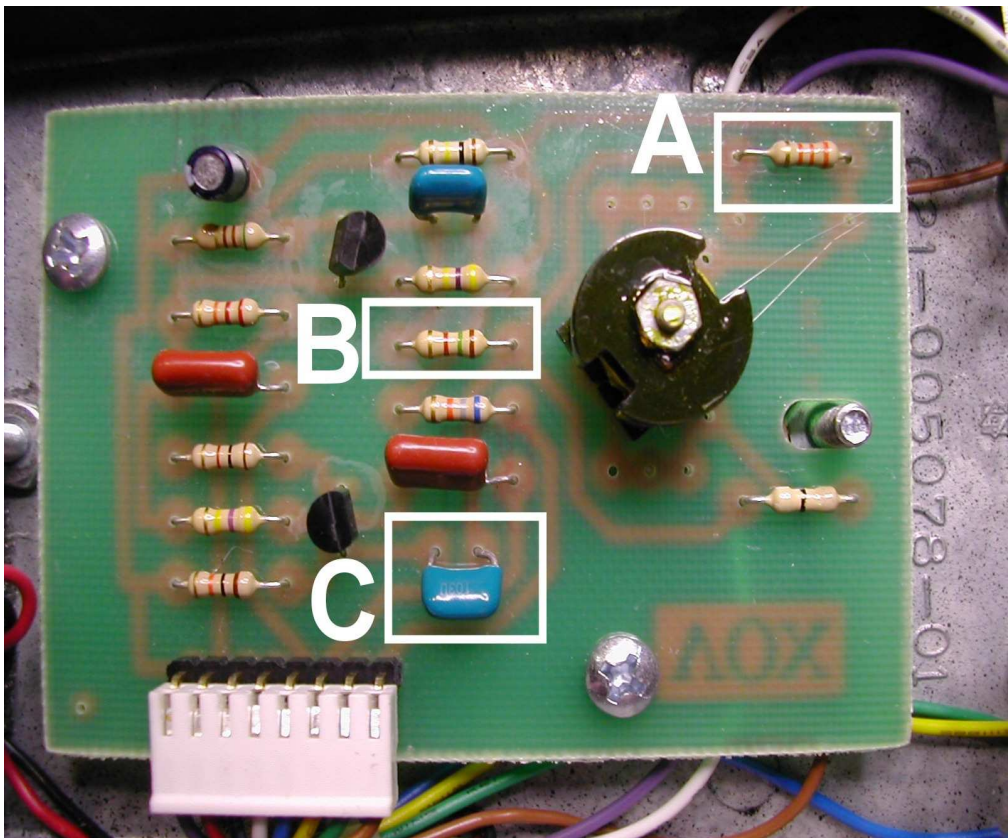70's/80's Thomas/Dunlop wah: <http://www.fulltone.com/ThomasCrybaby.jpg>



H & K Warp factor

"Fat tone" Mod


Location	Stock value	Mod value	What it effects
D1	1n4148	1n4001	Much warmer, better dynamically. Responds much better.
D2	1n4148	LED	
R39		ADD 1uf in parallel with stock resistor	Adds juicy midrange
R19	120k	JUMPER	Adds high mids around 1k or 1.5k hz or so. Connect a mini-pot to use as a mid adjustment.
R18	47k	10k	Adds more mids...almost into tubescreamer territory. Connect a 47k mini-pot (trimmer) and you will have a mid control.
R24	18k	10k, 4.7k, 2.2k	(Lower value for more highs)
C13	.0068UF	.22uf (optional)	Adds low bass


H & K Warp factor 'Rollins Mod'

Location	Stock value	Mod value	What it effects
D1	1n4148	1n4001	Much warmer, better dynamically. Responds much better.
D2	1n4148	LED	
C20	.01uf	.047uf	Raise value=more mids/low mids
C41	.22uf	Remove	Adds a little bit more highs

OPTIONS:

Location	Stock value	Mod value	What it effects
Options:			
R35		1k resistor	Adds a ton of volume, and headroom.
C20	.01uf	.047/.1/.22/.47 uf	Raise value=more mids/low mids
C21	.01uf	047/.1/.22/.47 uf	
C41	.22uf	.15 / .1 / .047 / .01 uf	Subtract value, will add clarity, and gain.
R18		10k	Adds more mids...almost into tubescreamer territory

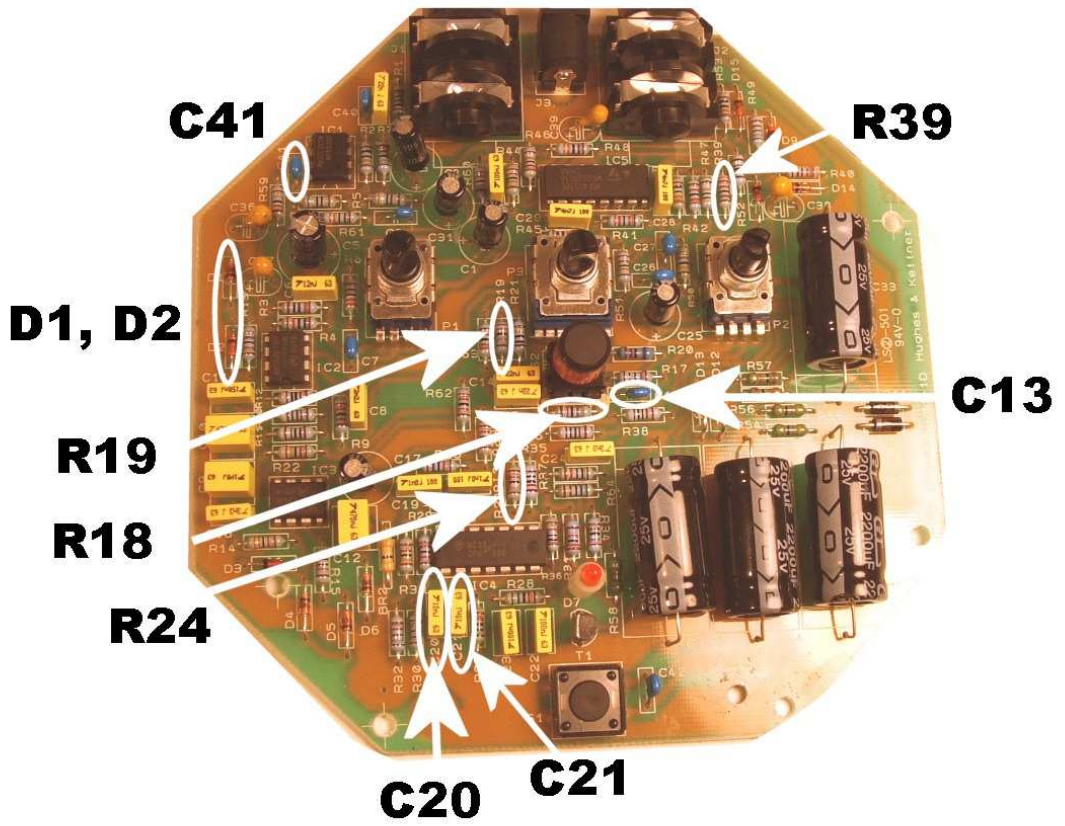

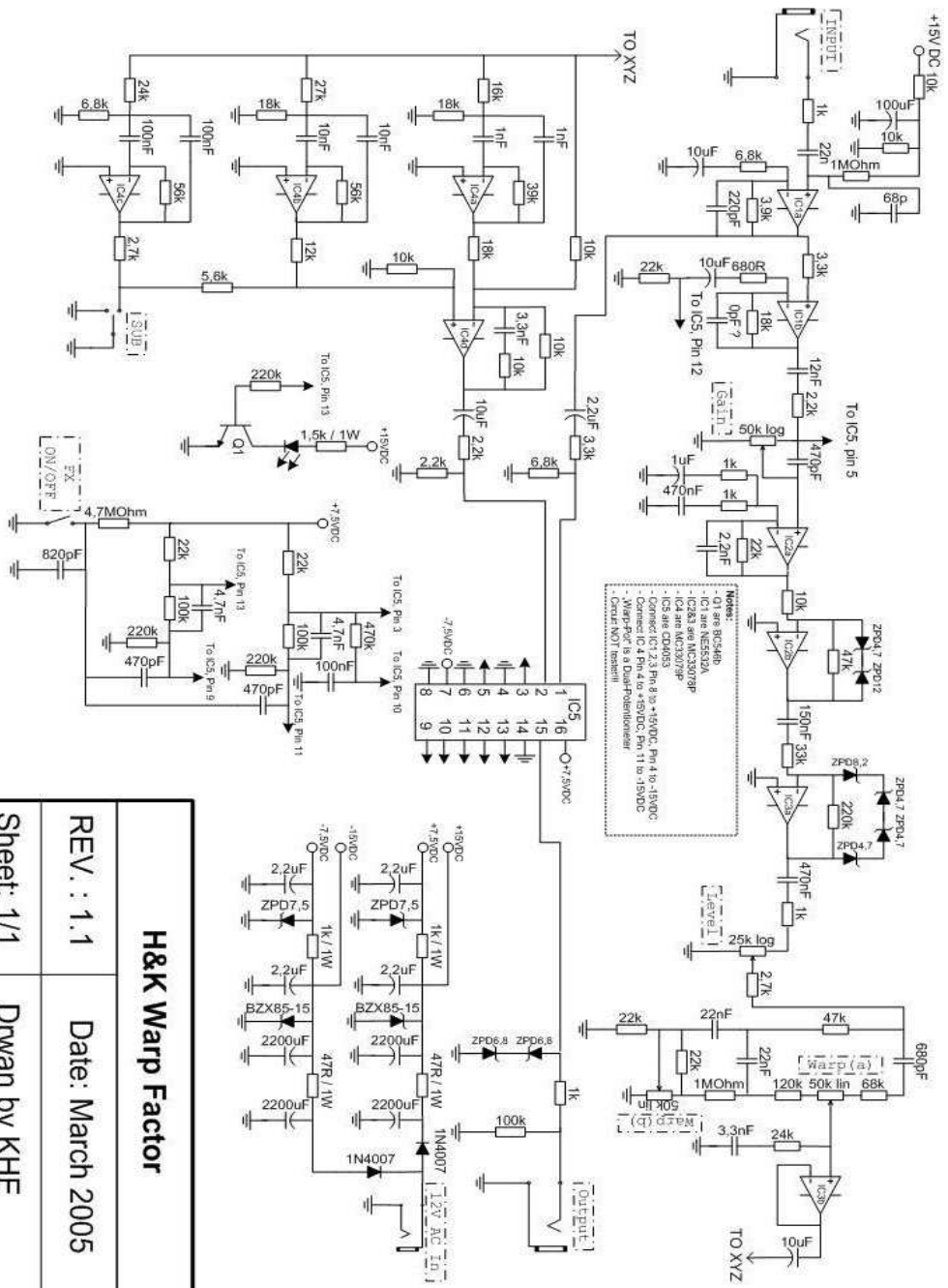

H&K Warp Factor	
REV. : 1.1	Date: March 2005
Sheet: 1/1	Drawn by KHE

In Closing...

Building and modifying effects is a seriously addicting hobby...one that many enjoy for years and years. It definitely is a lifetime journey. This is by means NOT everything that can be done, but it should be the guide to help you on your journey to build some of the best effects you've ever heard. Please realize that every pedal will sound a little different, even if they are the exact same circuit. Every part has a + or - tolerance, and when added up as a whole, one circuit can sound much better compared to the other. This is very evident in the earlier fuzz pedals, tubescreamers, and most of the old vintage equipment.

The 'key' to optimal happiness and enjoyment in this hobby is just the desire and willingness to experiment – there are many times when you just 'try' this or that just to 'see what happens'. This is by far the best way to learn. Getting an electronics engineering degree won't do this totally, but it will tell you the theories behind why it does or does not work. Mike Fuller of Fulltone is a prime example of this. Not schooled in electronics originally, he built his first pedals by tweaking them by ear (much like I did). Mike has an AMAZING sense of tone and an excellent ear. As a result, he's built one of the prime 'boutique' pedal companies around today.

A great sense of marketing helped him out a bit as well. ;))

I hope this book has inspired you to open up your guitar pedals, and start tinkering – there is SERIOUS tone hiding in there!! :)

I must insist, however, that you follow each step in this book very carefully – and do NOT use this guide to work on amplifiers, or multieffects, or ANYTHING except for the pedals I have listed in this book. After you become more familiar with electronics and working on pedals, you may want to try your hand at building your own. For that I recommend you check out our other books, "How to build effect pedals...(for beginners)", and "How to build effect pedals...(for advanced DIY'ers.)" Also, if you want to learn how to tweak your guitar amp, you may be interested in our new DIY amp modification series... see www.DIYampmods.htm for more info.

Thanks for your interest in the DIY effect pedal scene – keep in touch with me and let me know how you are coming along! : -)

Take care,
Brian Wampler
Author, and avid stompbox nut!!

Contact Information

<http://www.guitartone.net> – DIY modifications and “how to build effects” books

<http://www.ToneClonePedals.com> – Build your own pedal kits and instructions

<http://www.indyguitarist.com/> - if you would rather not do your own mods, check out <http://www.indyguitarist.com/> --indyguitarist.com developed the mods originally, and is the only company with permission to do the mods under the “IndyGuitarist” name at this time. You MAY, however, perform modifications designated as ‘similar to indyguitarist.com,’ or ‘using guitartone.net templates’.

Email: brian@wamplerpedals.com

*No part of this book may be reproduced in whole or part for profit or non-profit without the exclusive written permission of Brian Wampler. As such, this document and the information within it is copyright © 2004-2009 Indyguitarist.com, Brian Wampler.